 



AstroPix v4

Nicolas Striebig*, Richard Leys, Ivan Peric
**striebig@kit.edu*



Introduction – HV-CMOS


- Charged particles or photons generate electron-hole pairs in depletion region of the sensing diode formed by deep n-well and p-substrate
- Separated by strong electric field
- Electrons drift to charge-collecting deep n-well
- Deep n-well contains shallow wells for electronics
- **High-Voltage CMOS Active Pixel Sensor (HVMAPS)**

 

AstroPix4: Analogue Part

Pixel contains:

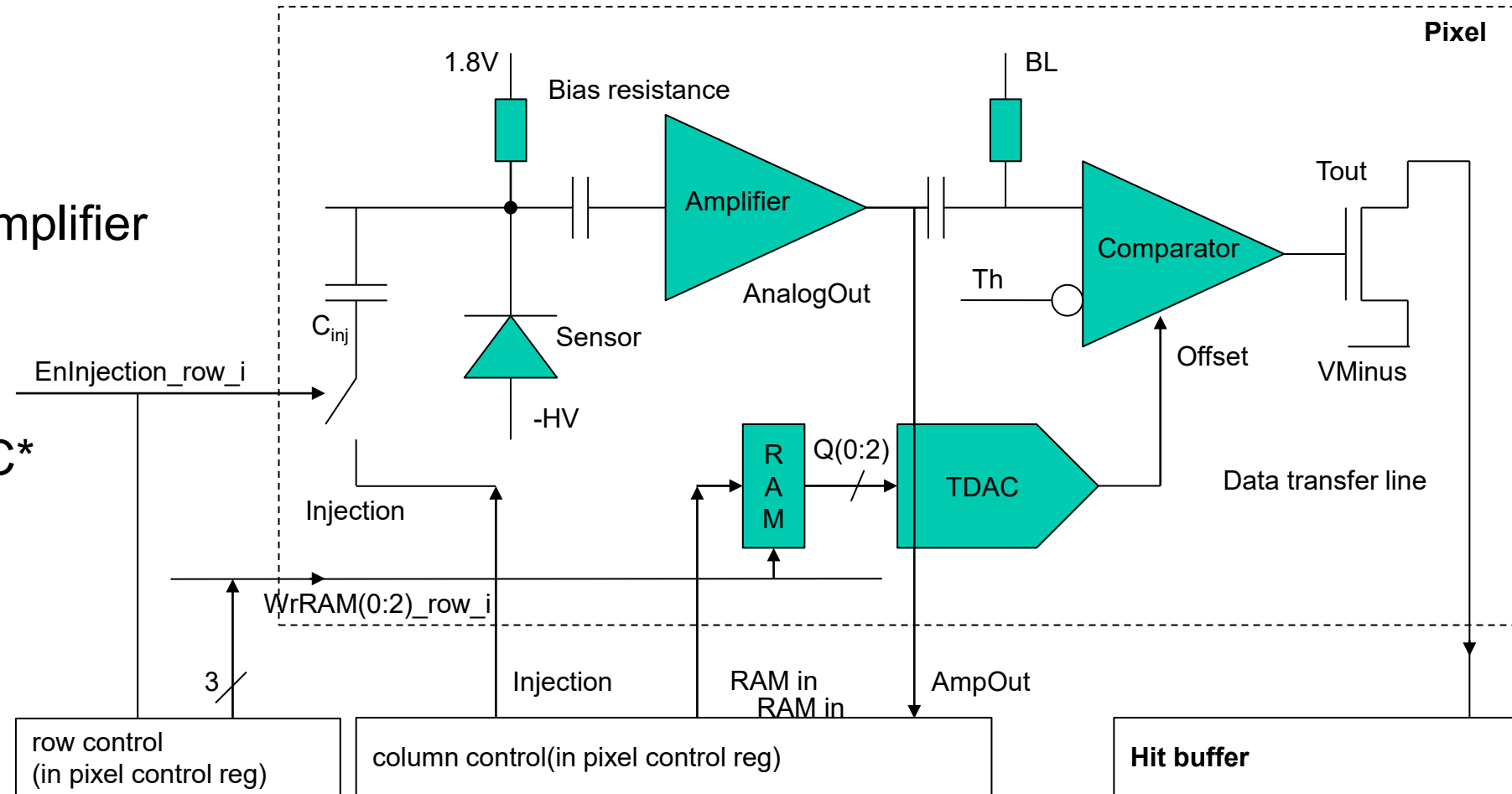- Sensor diode
- Charge Sensitive Amplifier (CSA)
- Comparator
- Threshold tune DAC*
- RAM for tune bits*




*placed in the periphery

Source: Ivan Perić

AstroPix4 : Analogue Part

Working principle:

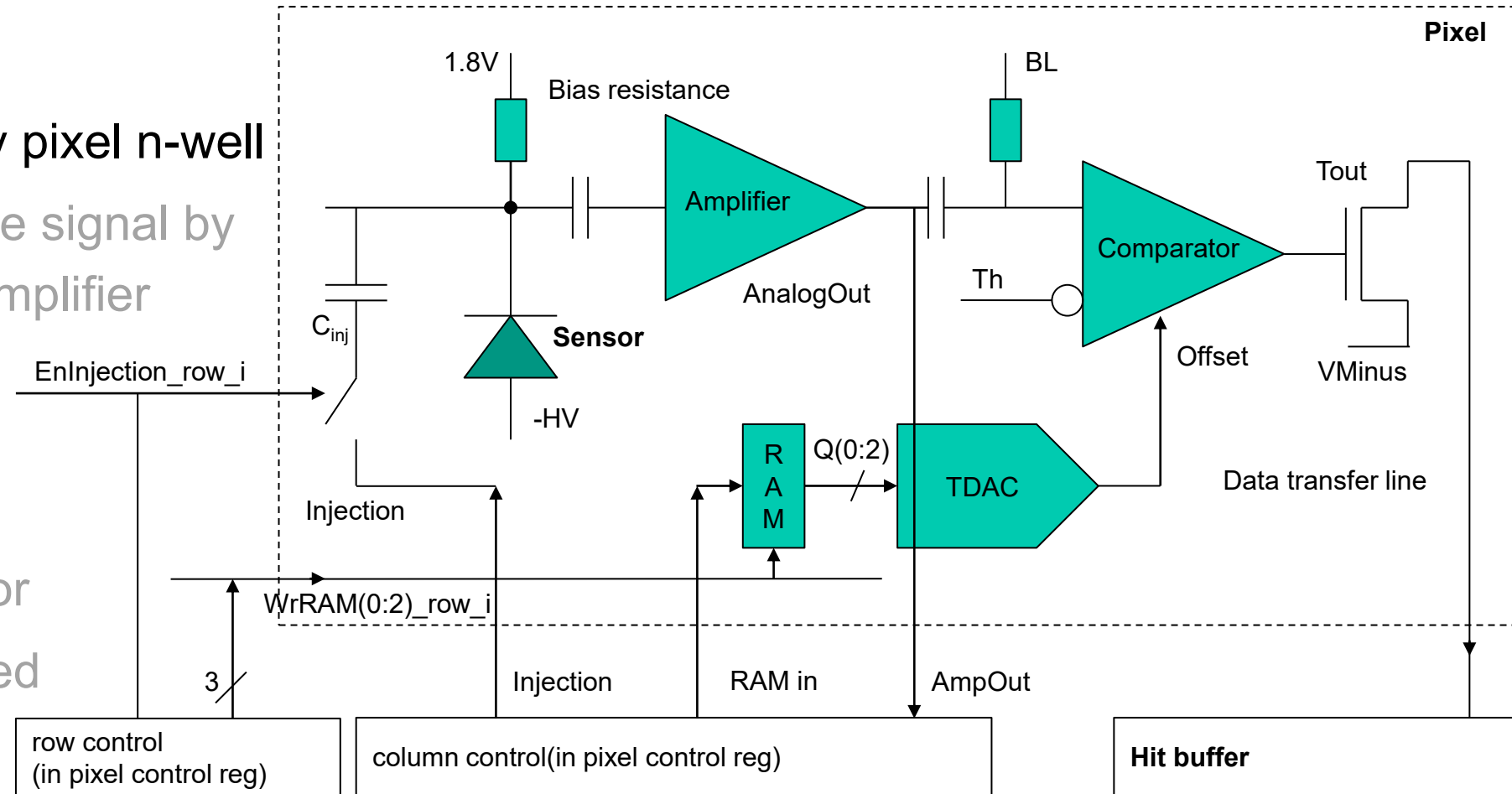1. Charge collected by pixel n-well
2. Converted to voltage signal by Charge Sensitive Amplifier
3. Analog voltage pulse shaped and converted to digital signal by comparator
4. Hit information stored in hit buffer




Source: Ivan Perić

AstroPix4 : Analogue Part

Working principle:

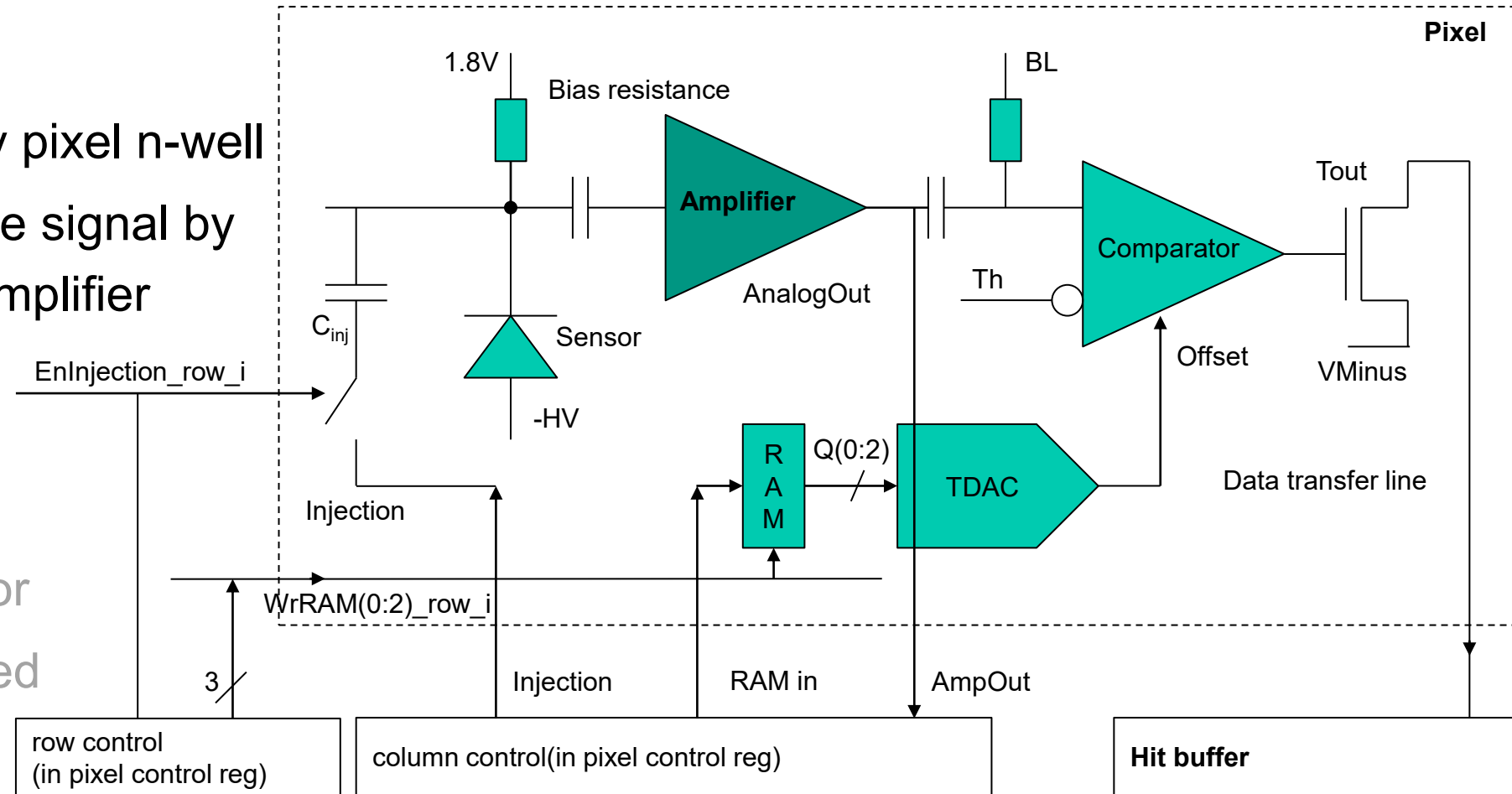1. Charge collected by pixel n-well
2. Converted to voltage signal by Charge Sensitive Amplifier
3. Analog voltage pulse shaped and converted to digital signal by comparator
4. Hit information stored in hit buffer




Source: Ivan Perić

AstroPix4 : Analogue Part

Working principle:

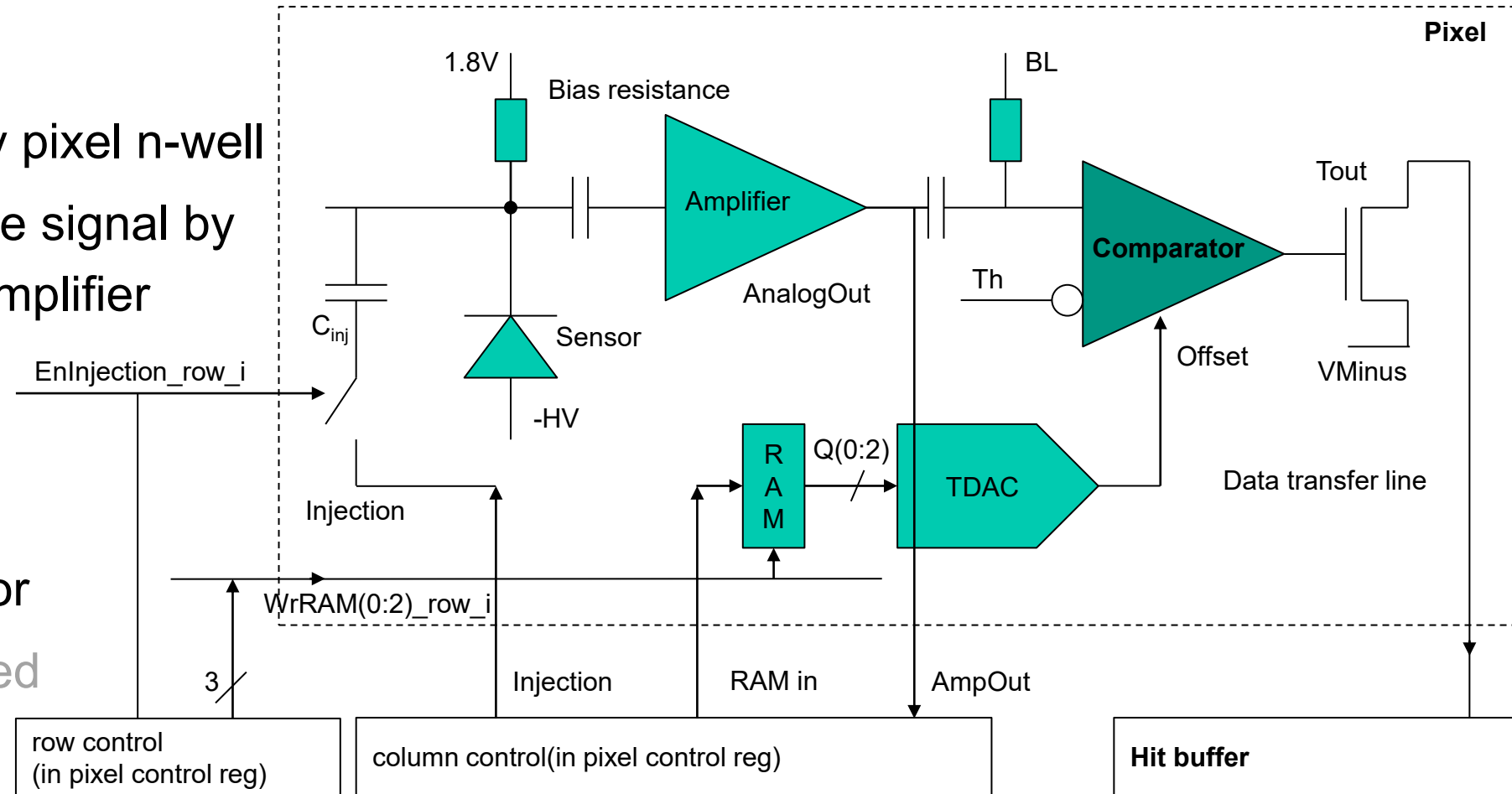1. Charge collected by pixel n-well
2. Converted to voltage signal by Charge Sensitive Amplifier
3. Analog voltage pulse shaped and converted to digital signal by comparator
4. Hit information stored in hit buffer




Source: Ivan Perić

AstroPix4 : Analogue Part

Working principle:

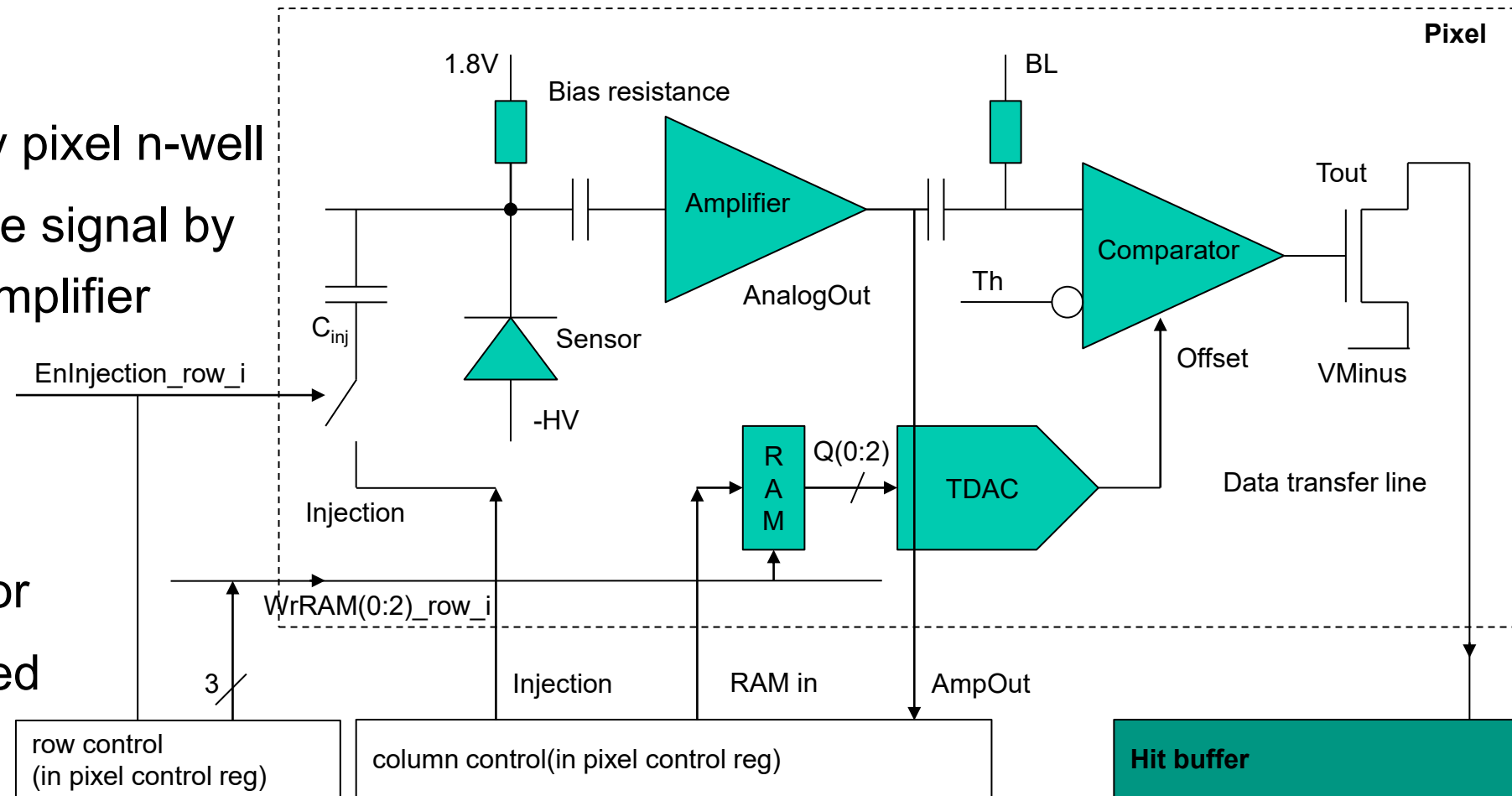
1. Charge collected by pixel n-well
2. Converted to voltage signal by Charge Sensitive Amplifier
3. Analog voltage pulse shaped and converted to digital signal by comparator
4. Hit information stored in hit buffer



Source: Ivan Perić

Specifications for TSI May 2023 run

 - Size: 1 cm x 1 cm
- Matrix: 16 x 13 pixels
- Pixel size: 300 μm x 300 μm
- Pixel pitch: 500 μm
- Interfaces: QSPI Daisychain, SR
- Integrated voltage DACs
- Integrated injection switch
- Integrated temperature sensors
- **Improvements over v3:**
 - TuneDACs
 - Hitbuffers + FlashTDC measurement
 - Reduced pixel capacitance
274 fF vs 391 fF @100 μm t_{dep}




AstroPix4 I/O

- Clocks: 2.5 MHz timestamp clock (used as refclk for PLL)
- Digital Interfaces:
 - QSPI max. 5 MB/s: Configuration, Readout
 - Shiftregister Interface: Configuration fallback
- Interrupt, Hold
- Analog output: monitor amplifier output in Row0
- Hitbus: monitor comparator outputs
- Cal: Injection pulse
- Power:
 - Analog 1.8 V + 1.2V
 - Digital 1.8 V
 - Vminuspix 0 – 0.9 V
 - HV

TuneDACs

 - 3 SRAM cells per pixel to control current DAC
- Number of bits can be increased if needed
- Placed in periphery
 - would add capacitance if placed in pixel
- Used to tune comparator branch currents to compensate threshold dispersion




(b) The threshold dispersion before (red) and after (blue) tuning for the full MuPix10 matrix with an equivalent signal of $3000 e^-$.

Source: <https://arxiv.org/pdf/2012.05868.pdf>

Astropix v1 - v3: Or'd Rows and Columns

 - Or'd Rows and Columns
- Advantages:
 - Low number of channels
- Disadvantages:
 - Identification problems with multiple hits in Row/Col
 - High bus capacitance → limits time resolution




Astropix v4: Individual Hitbuffers

- Hits from every pixel are saved individually
- 16 x 13 pixel matrix -> 208 hitbuffers
- Similar to ATLASpix design
- Advantages:
 - No identification problems with multiple hits in Row/Col
- Disadvantages:
 - Occupies larger chip area




AstroPix Hitbuffer

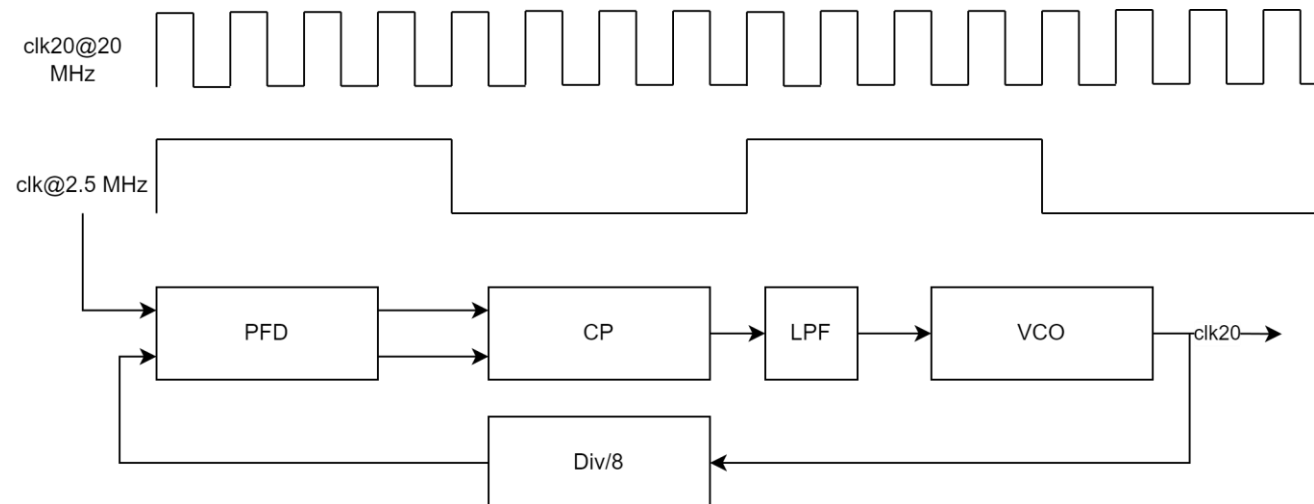- Logic + DRAM cells
- TS gets saved on positive and negative edge of a hit:
 - 20 MHz from PLL with 2.5 MHz reference -> 17bit@50ns
 - Covers 6.55 ms




AstroPix Hitbuffer

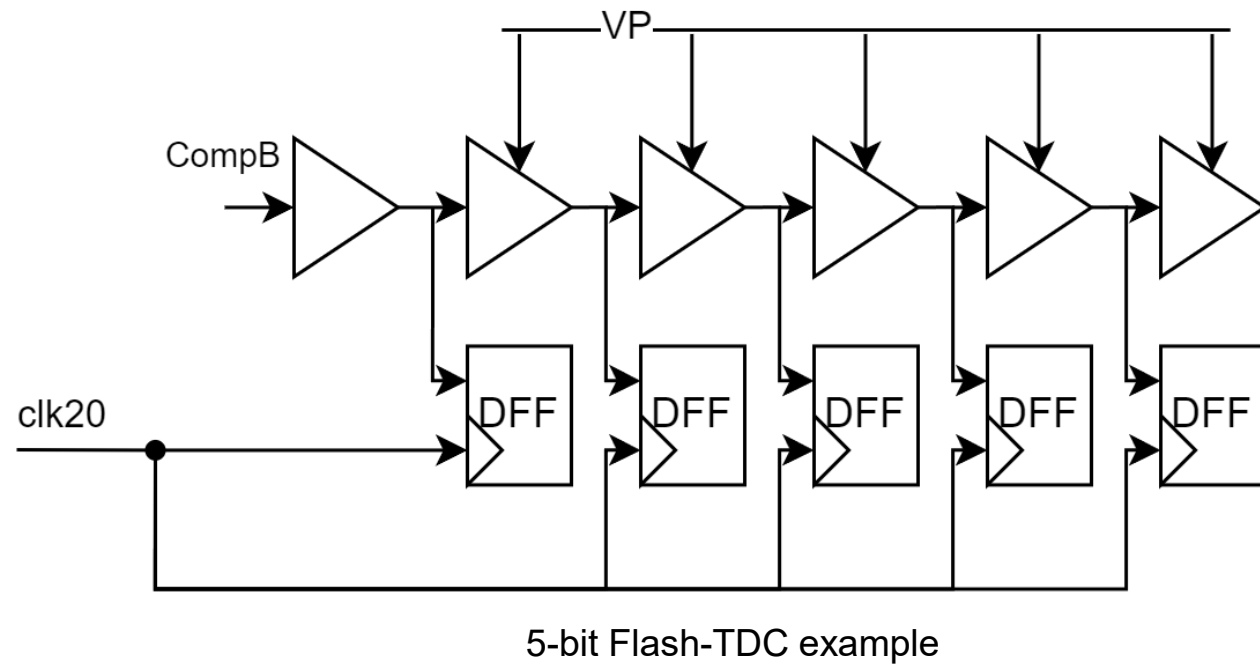- FineTS:
 - Flash TDC with 16 delay elements (32 current starved inverters)
 - Resolution of 2.94 ns



AstroPix Hitbuffer TDC

 - **Problem:** Flash TDC is very susceptible to process and temperature variation
- Without calibration:
 - Nominal delay should be 50 ns
 - Mismatch: +/- 3.7 LSB
 - Temperature variation (10 to 50 °C): ~5.4 LSB
- 1225 Flash TDCs have to be calibrated for mismatch/process and temperature ☹️



AstroPix Hitbuffer TDC


- **Solution:** TDC delay elements are stabilized by global DLL (1 per chip)
- Without calibration:
 - Mismatch: +/- 0.5 LSB
 - Temperature variation (10 to 50 °C): < 0.17 LSB
- Can be improved with automatic calibration
 - After each measurement, automatic measurement of a fixed time period, i.e. 1 clock cycle

```
stddev(cross(clip(VT("/Out<0:34>") 0 3.1u) 0.9 1 "rising" nil nil nil)-cross(clip(VT("/Compln") 0 3.1u) 0.9 1 "rising" nil nil nil))
```

1


Name

 ...ln") 0 3.1u) 0.9 1 "rising" nil nil nil)



Readout logic

- Controlled by state-machine (FSM)
- Working principle:
 - Priority Logic: Data from highest active Hitbuffers in every column are loaded into EoCs
 - FSM goes through all loaded columns and writes the data into async FIFO
 - If FIFO is not empty, interrupt goes low
 - DAQ toggles the SPI clock, which initiates FIFO readout via QSPI Interface
 - From the outside perspective i.e. the DAQ, no difference to older AstroPix version, same protocol just different payload size

 


AstroPix QSPI

- AstroPix2 digital: 2x5 Byte
 - Each per Col/Row
 - 8b Header
 - 8b col/row
 - 8b TS
 - 16b ToT

- AstroPix4+: 1x8 Bytes
 - 8b Header (5 bit ChipID, 3 bit Payload)
 - 6b Row
 - 6b Col
 - 2x 18b TS
 - 2x 4b TDC

Commands

 

BIT	FIELD	DESCRIPTION
[4:0]	Address	Requires 20 single addresses <ul style="list-style-type: none"> - 0x00 - 0x14 : Single addresses - 0x15 - 0x1F : Reserved - 0x1D: Invalid - 0x1E: Broadcast
[7:5]	Command	8 Commands: <ul style="list-style-type: none"> - 0x01 - <u>NOCMD</u> / IDLE - 0x02 - Routing: dispatch addresses - 0x03 - Shift Register Config

Readout

- Wait for interrupt signal low
- Toggle SPI clk to read out

AstroPix4: Requirements for ePIC

- **Dynamic range 20 keV - 3 MeV**
 - Much larger than Amego-x requirement → Amplifier redesign?
 - Wafer: Resistivity and thickness?
- **Radiation tolerance 1 rad/year and 10^8 neutrons/cm²/year**
 - Low TID important for HiRes wafer effectiveness
- **10 ns bunch crossing**
 - Which time resolution is actually needed?
 - 4σ would be **~1.25 ns** → not easy with large pixels
 - Amego-x requirement is only 666 ns
 - Off-chip timewalk correction is needed (~20 ns for $V_{th} = 6 \cdot V_{noise_rms}$ 6 keV vs. 60 keV)
- **Power consumption**
 - Better timing → higher amplifier and comparator current needed
 - Power budget? 1.5 mW/cm² is very optimistic

Documentation

- From Google Doc → nice Overleaf document
- Contents:
 - Explanations
 - I/O List with descriptions
 - Drawings with pad locations
 - Quickstart guide for measurements
- Started working on it
- Takes a bit of time 😊

2.1 Pixel electronics

A simplified schematic of the pixel electronics is shown in Fig. 2.1. The sensing element is the photo-diode formed by the p-n-junction and the deep n-well of the pixel. By applying a high reverse bias, a thick depletion region is created. Electrons generated by charged particles or photons in the depletion region are quickly transported to the collection well by drift, due to the strong electric field.

A charge sensitive amplifier (CSA) is capacitively coupled to the collection well, it is implemented as a cascode amplifier with a cascode load and an offset input device. The feedback capacitance of around 50fF is formed by the parasitic drain junction capacitance of the load cascode pMOS. An output signal is produced dependent on the input charge and this capacitance:

$$v_{out} \propto \frac{Q}{C_{FB}}$$

A second, much larger 15pF feedback capacitance C_{FB} is connected from the amplifier input to the voltage node between the load transistors. If the cascode transistor is in saturation, the impedance from the output to this node is high, but if there is a large input signal, the cascode transistors go into the linear region and there is a connection from the output to this node. Therefore for a large input signal the two capacitors appear to be in parallel resulting in a reduced closed loop gain of:

$$v_{out} \propto \frac{Q}{C_{FB} + C_{J02}}$$

The feedback capacitance is continuously discharged by a constant current source VBIAS, this results in a linear decay of the pulse. The amplifier input de-saturating point is set by source-follower SP1. The other source-follower SP2 acts as a low pass filter. The rising edge is fast, but the falling is slow because the load current source INFOL2 is biased with a low current. A higher current increases the low pass filter bandwidth, resulting in a steeper slope i.e. shorter Td but also higher noise. From the output of SP2 the signal is capacitively coupled through a Metal-Insulator-Metal (MIM)

7

capacitor to AmpOutAC.

 


Figure 2.1: Simplified schematic of signal path from sensing diode, amplifier and band-pass stage

The signal path from the comparator input is shown in Fig. 2.2. The analog voltage pulse goes into the comparator and gets compared to the threshold voltage V_{th} . The comparator bias current is set by the digital-to-analog converter (DAC) VSCOMP. The output is a positive voltage pulse with T_{low} and V_{th} high LVT. Due to mismatch the differential amplifier in the comparator is not totally symmetric. This results in a threshold mismatch to the value set by V_{th} . A compensation mechanism is implemented in AutoPret. It consists of a 30fF current DAC which can be tuned to make the tail current in the differential stage equal.

The following stage is an open drain offset. This offset converts the positive pulse to a negative pulse. The source of the offset is connected to Voutneg (normally 0.7 - 1V), which reduces the signal amplitude to 0.6 - 1.1V. In the tail of every pixel, the signal is converted back to the full amplitude, with a pass common source amplifier. The output signal is a positive pulse with a fast rise time and a fall time which is determined by the discharge current VBIAS2. This circuit also incorporates the pull-up current source VBIAS2.

AstroPix4 Summary

- No identification problems with multiple hits in same row/col
- Improved timestamp resolution
- Threshold tuning
- Lower digital power
 - Chip level: Async ToT measurement with low duty cycle due to low rates
 - System level: No fast clocks needed anymore, no highspeed clock distribution
- Documentation

- Some ideas for v5:
 - Self tuning
 - ADC to digitize analog temperature sensor
 - Passive matrix for e-TCT


AstroPix4: Time Walk and ToT

■ Time walk:

- Rise time same for all signals
- Difference in time at which threshold is crossed is called time walk
- Time walk ~ 20 ns
 - can be corrected with ToT information

■ Time over Threshold:

- $1 \mu\text{s}$ to $30 \mu\text{s}$

 

Schematic description of time walk, rise time, and time over threshold

Power consumption TDC + PLL + DLL

- Hitbuffer with TDC
 - Active: ~700 μ W
 - Idle: 50-100 nW
- 20 MHz PLL + DLL: ~240 μ W
- Based on hitrate studies:
 - Average 0.008 Hits/s per 500 μ m Pixel
 - For 35x35 Pixel **2cmx2cm Chip**: 35*35*0.008 Hits/s **~10 Hits/s**
- Implications on duty cycle
 - TDC duty cycle D for max. $\frac{10}{1s} \cdot 2 \cdot 50 \text{ ns} = \frac{1000 \text{ ns}}{1s} = 10^{-6}$
- **Avg. power per Chip for ToT: $\frac{0.7 \text{ mW} \cdot 1 \text{ } \mu\text{s} + 35 \cdot 35 \cdot 100 \text{ nW} \cdot 999.999 \text{ ms}}{1s} = 121 \text{ } \mu\text{W}$ i.e. 360 μ W incl. PLL and DLL**
- **For comparison LVDS-Receiver in v2/v3 for 200 MHz clock alone consumes 1 mW!**