

Basics of serial powering

L. Gonella

ePIC SVT workfest



ANL, 9 January 2024

Introduction

- In the following slides (2 to 4) a module is the detector's active element, that is the sensor with its readout electronics.
- It can be an hybrid pixel detector where sensor and readout electronics are two separate entities bump bonded together, or a MAPS detector where sensor and readout electronics are integrated in the same substrate.
- Serial powering is used to power the readout electronics, not to bias the sensor.
- Power to the readout electronics is typically called “low voltage”.
- The choice of serial powering for the low voltage distribution impacts the data transmission scheme and the sensor bias scheme.



Serial powering basics

- Serial powering is a **current based powering scheme**, where modules are powered in series by a constant current.
- **The current to voltage conversion is done by regulators close to/on module.**
- In a serial powering chain made of n modules, the transmitted current is only the current needed by one module, I .
- For n modules powered in series, the **current is reduced of a factor n with respect to a direct powering scheme** → Higher power efficiency and reduced cable volume.
 - Cable cross-section and the power losses on the cables scale by the same factor.

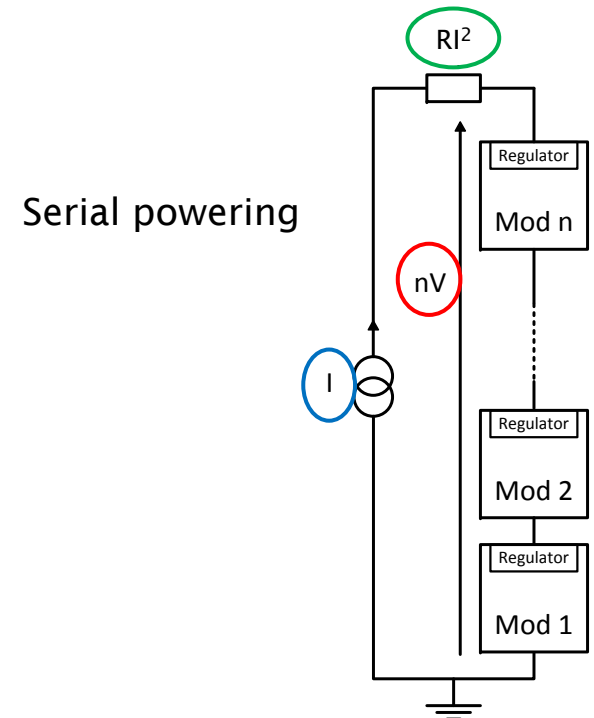 



Serial powering basics

- As the modules are powered with a constant current, V_{drop} is not constrained as in a voltage based powering scheme.
 - It can in principle be chosen only depending on the output voltage capability of the current source and of the allowed power density (i.e. cooling capability).
- Higher V_{drop} can be allowed in the active area of the detector to reduce the material budget of the cables.
 - Outside the detector the voltage drop can be reduced to lower the power losses.
- With respect to voltage based powering schemes (incl. DC-DC), serial powering allows more flexibility in the optimization of material and power efficiency.

  


Serial powering basics: data transmission

  - The voltage across the chain is nV , where V is the voltage on a module.
- Each module sits at a different ground potential.
- **AC coupled data transmission** required.
 - DC balanced data protocol (e.g. 8b10b).
 - Self biased receiver inputs to set the common mode voltage.



Sketch of a AC-coupled LVDS link

 


Serial powering basics: sensor biasing

- The voltage across the chain is nV , where V is the voltage on a module.
- Each module sits at a different ground potential.
- A group of sensors can be powered in parallel, i.e. sharing the same bias line + return, if the difference between operational voltage and breakdown voltage is larger than the total voltage drop in the chain.
- This is the case for planar sensors in hybrids pixel detectors biased to 100s volts.
- This is not the case for MAPS detectors where the sensor is biased with a few volts.
 - Direct powering of each sensor, required one floating supply channel per MAPS sensor.
 - Generate the sensor bias from the low voltage.

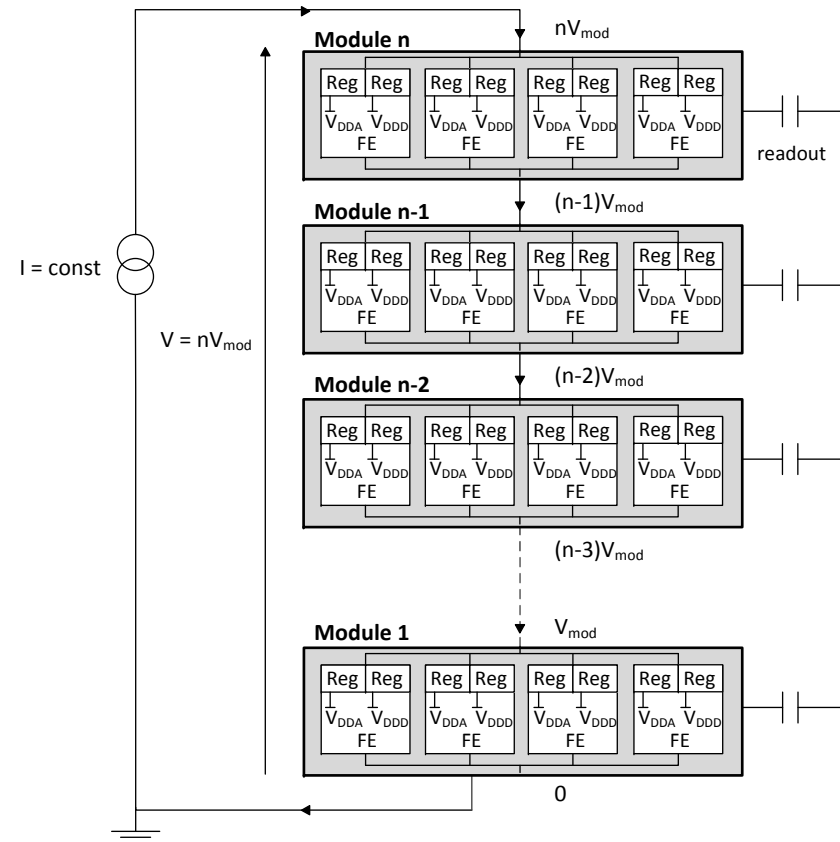
Example: ATLAS ITk detector

- The ATLAS pixel detector at the HL-LHC adopted serial powering (also the CMS pixel detector).
- Each module is made of a sensor bump bonded to a certain number of readout chips.
 - In the sketch, four readout chips per module (FE).
- The current flows in series between modules and in parallel between readout chips on a module.
- In each chip, two **shunt-LDO** regulators generate the analogue (V_{DDA}) and digital (V_{DDD}) voltages.



Shunt-LDO regulator

- For this powering scheme, on-chip regulators are needed that can:
 - Operate in parallel;
 - Generate different output voltages out of the current supply;
 - Shunt additional current in case of device failure.
- The Shunt-LDO regulator was designed to match these requirements.
 - First prototype version in the ATLAS pixel FEI4 chip (180 nm process).
 - Full SP version in the RD53 chip (65 nm process).
- It combines two regulation loops.
 - **Shunt regulation circuitry** → regulates the current to the chip.
 - **LDO (Low Drop Out) regulation loop** → generates the voltage for the chip.

 

Earlier SP regulator configurations

- Initial tests were done with the ATLAS FE-I3 pixel chip using a Shunt regulator to generate a constant voltage out of the input current and then one or two LDO to generate the V_{DDD} and V_{DDA} voltages needed by the pixel chip.
- To add redundancy to the SP chain, all shunt regulators on module are operated in parallel.
- Beneficial for voltage regulation when using shunt regulators as the input resistances are connected in parallel, lowering the total resistance and improving the voltage stabilization.

 


Figure 4.4: Schematic drawings of on-chip shunt and LDO regulators, represented respectively as a zener diode and variable resistors, to convert the input current into two stable voltages. These regulator configurations have been used with FE-I3 modules to generate $V_{DDD} = 2.0\text{ V}$ and $V_{DDA} = 1.6\text{ V}$.

Earlier SP regulator configurations

- However, this connection can be critical.
 - Due to mismatch and process variation, the shunt regulators placed in parallel can have different V_{thres} .
 - As the input characteristics of shunt regulators is very steep, the regulator with lower V_{thres} can take all current at start-up and burn.
 - This could eventually lead to a chain reaction and destroy all regulators on module.
- Safe parallel operation of shunt regulators requires to choose the value of the input series resistance according to the spread in threshold voltage values, in order to mitigate the I-V characteristics.
- The use of this resistance lowers the power efficiency and decreases the voltage stability.

 


Figure 4.4: Schematic drawings of on-chip shunt and LDO regulators, represented respectively as a zener diode and variable resistors, to convert the input current into two stable voltages. These regulator configurations have been used with FE-I3 modules to generate $V_{DDD} = 2.0\text{ V}$ and $V_{DDA} = 1.6\text{ V}$.

 


Figure 4.3: I-V characteristics of a shunt regulator integrated in the FE-I3 chip (DOVER). This regulator has $V_{thres} = 2.58\text{ V}$ and $R_{in} = 1.9\ \Omega$ [51].

New regulator concept: Shunt-LDO

- Combination of a Low Drop Out (LDO) regulator and a shunt regulator.
 - Shunt transistor is part of the LDO load.
 - R_{in} of the shunt is replaced by the LDO power transistor.

- LDO regulation loop \rightarrow constant V_{out}

$$V_{out} = 2 \cdot V_{ref}$$

- Shunt regulation circuitry \rightarrow const I_{load}

- I_{ref} set by R3, depends on V_{in} ($\rightarrow I_{in}$)
- I_{M1} mirrored and drained in M5
- I_{M1} and I_{ref} compared in A3
- M4 shunts the current not drawn by the load

$$I_{in} \approx kI_{ref} \approx k \frac{V_{in} - V_{thM6}}{R3}$$

$$R_{in} \approx \frac{V_{in}}{I_{in}} \approx \frac{R3}{k}$$


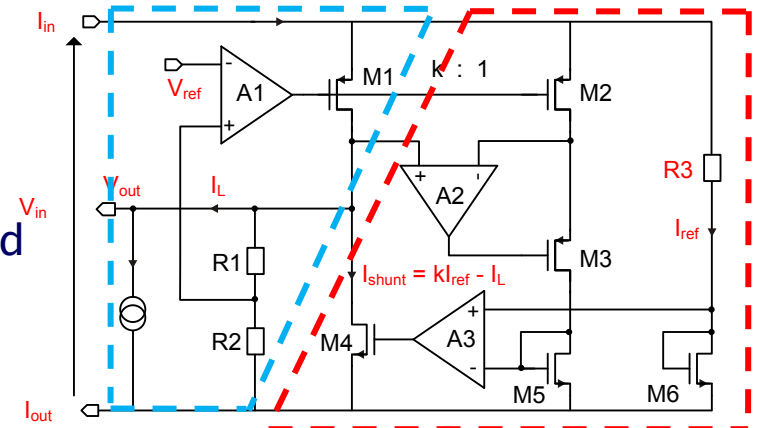
 


Figure 4.6: Simplified schematics of a Shunt-LDO regulator, explained in the text [46].


Shunt-LDO regulators in parallel

- The Shunt-LDO has an **ohmic I-V characteristics** → safe operation of Shunt-LDO regulators connected in parallel.
 - Even for different values of R_{in} , i.e. different $R3$
- More robust design against process variation and mismatch.
- Differences in the value of $R3$ lead to different shunt current values but do not destroy the regulator.
- **Shunt- LDO regulators can be placed in parallel even if they generate different output voltages:** the difference between their output voltages is compensated by the $V_{dropout}$ across the pass transistor of the LDO regulator, $M1$.
- Finally, should one of the parallelly placed regulators fail, **the extra current can be shunted by the other regulators.**

 
$$R_{in} \approx \frac{V_{in}}{I_{in}} \approx \frac{R3}{k}$$



Shunt-LDO regulators in parallel

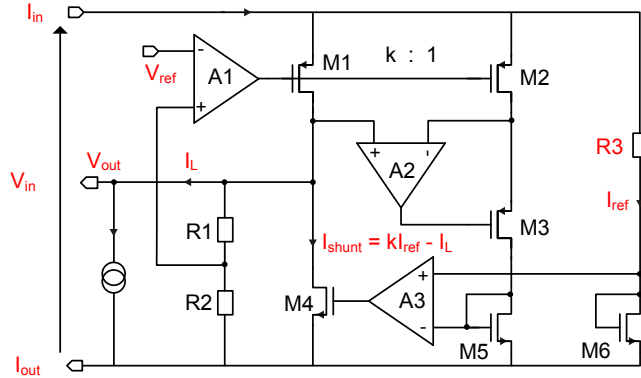

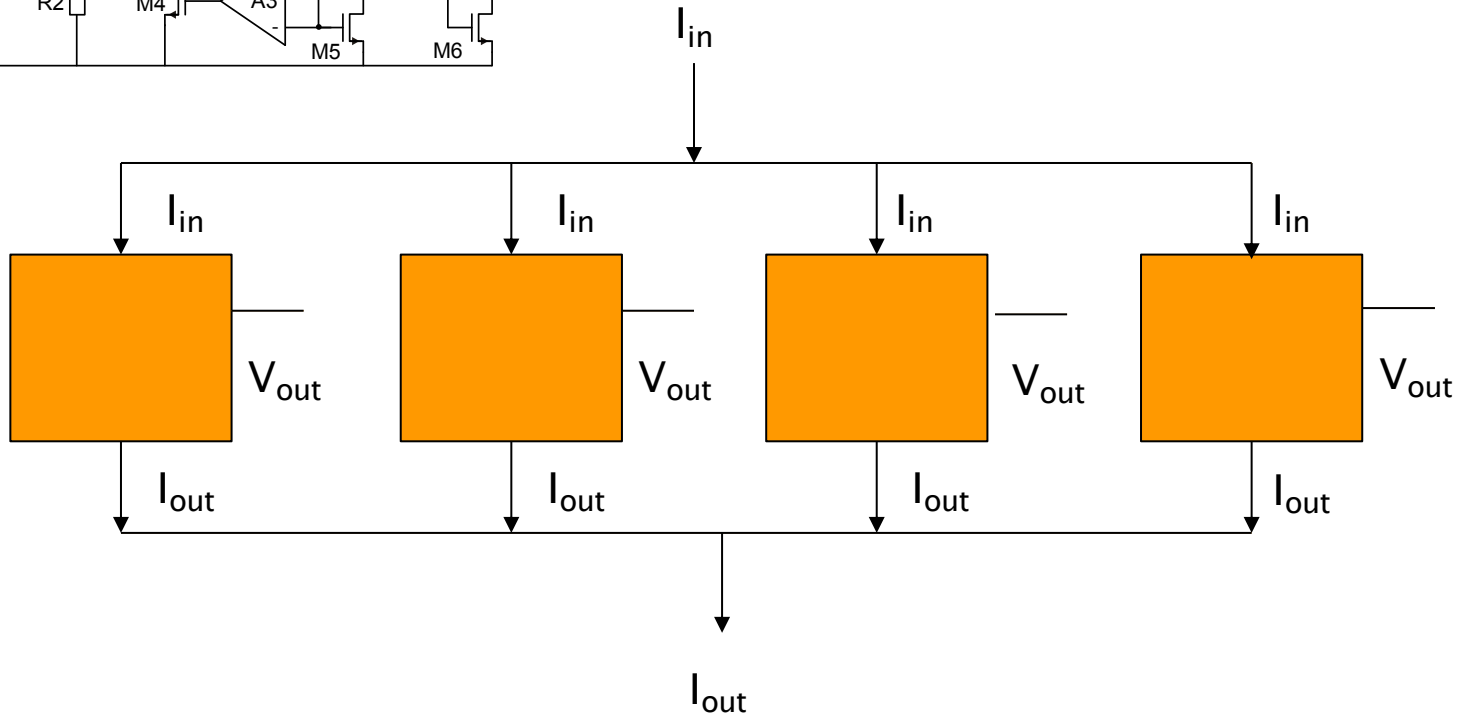- Parallel connection means that I_{in} and I_{out} are in parallel, not V_{out}



Shunt-LDO in RD53 chips

- The production version of the regulator for the ATLAS ITk pixel detector includes many protection features and addresses all possible regulator failure modes.
- The design is considered robust enough that a bypass element on each module has been deemed not necessary.
- The development time of this regulator was 7 years, with 5 designs submitted.
- More details at
 - M. Karagounis, Shunt-LDO RD53B features, talk, 2020
https://indico.cern.ch/event/879686/contributions/3706455/attachments/1975390/3287622/SLDO_RD53B_Features.pdf
 - M. Karagounis, Evolution of the SLDO Regulator, talk, 2022, (ask Laura for the slides)

Backup

Literature

- ATLAS SP Proof of concept and Shunt-LDO in 180 nm
 - L. Gonella, PhD thesis, <https://cds.cern.ch/record/1633150?ln=en>
 - L. Gonella, D. Arutinov, M. Barbero et al. **‘A serial powering scheme for the ATLAS pixel detector at sLHC’**. In: JINST 5 (2010), p. C12002. doi: 10.1088/1748-0221/5/12/C12002.
 - M. Karagounis, D. Arutinov, M. Barbero et al. **‘An Integrated Shunt-LDO Regulator for Serial Powered Systems’**. In: Proc. of the European Solid-State Device Conference, ESSCIRC 2009 (2009), pp. 276–279. doi: 10.1109/ESSCIRC.2009.5325974.
 - L. Gonella, M. Barbero, F. Huegging et al. **‘The shunt-LDO regulator to power the upgraded ATLAS pixel detector’**. In: JINST 7 (2012), p. C01034. doi: 10.1088/1748-0221/7/01/C01034.
 - L. Gonella et al. **‘Performance evaluation of a serially powered pixel detector prototype for the HL-LHC’**. In: JINST 12.03 (2017), P03004. DOI: 10.1088/1748-0221/12/03/P03004.
 - V. Filimonov et al. **‘A serial powering pixel stave prototype for the ATLAS ITk upgrade’**. In: JINST 12.03 (2017), p. C03045. DOI: 10.1088/1748-0221/12/03/C03045.

Literature

- Shunt-LDO in 65 nm
 - M. Karagounis, Shunt-LDO RD53B features, talk, 2020
https://indico.cern.ch/event/879686/contributions/3706455/attachments/1975390/3287622/SLDO_RD53B_Features.pdf
 - M. Karagounis, Evolution of the SLDO Regulator, talk, 2022, (ask Laura for the slides)
 - F. Winkler, Verification of Shunt-LDO, Master Thesis, 2019 <https://d-nb.info/1237320216/34>
 - J. Kampkötter et al. 'Stabilization and Protection of the Shunt-LDO regulator for the HL-LHC pixel detector upgrades', PoS (TWEPP2019) 067