

# Introduction to Radiation Sensors Readout ICs and Measurements

G.W. Deptuch, S. Mandal

EDIT 2023



@BrookhavenLab

# Covered:

## Part 1

- Solid-State sensors as a source of charge signal
- Short Introduction to Integrated Circuits technology
- Typical Front-End Processing chain in nuclear electronics
- Types and methods of measurement achieved with Front-End circuits
- Elements of Back-End Processing chain in nuclear electronics

## Part 2

- Introduction to Digitization and Digital Signal Processing
- Illustrations of practical realizations

# People

Grzegorz W. Deptuch [gdeptuch@bnl.gov](mailto:gdeptuch@bnl.gov)


Soumyajit Mandal [smandal@bnl.gov](mailto:smandal@bnl.gov)

Prashansa Mukim [pmukim@bnl.gov](mailto:pmukim@bnl.gov)

Md Arif Iqbal [miqbal@bnl.gov](mailto:miqbal@bnl.gov)

# Transistors + IC Technology - 1


symbolic/schematic representation

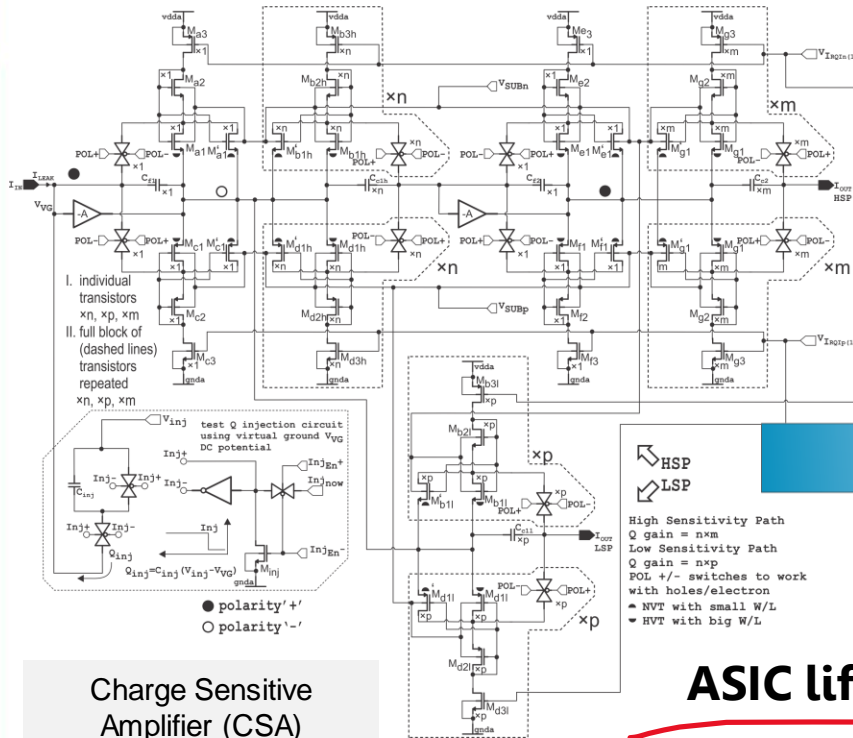

Charge Sensitive Amplifier (CSA)  
(with two sensitivity paths)

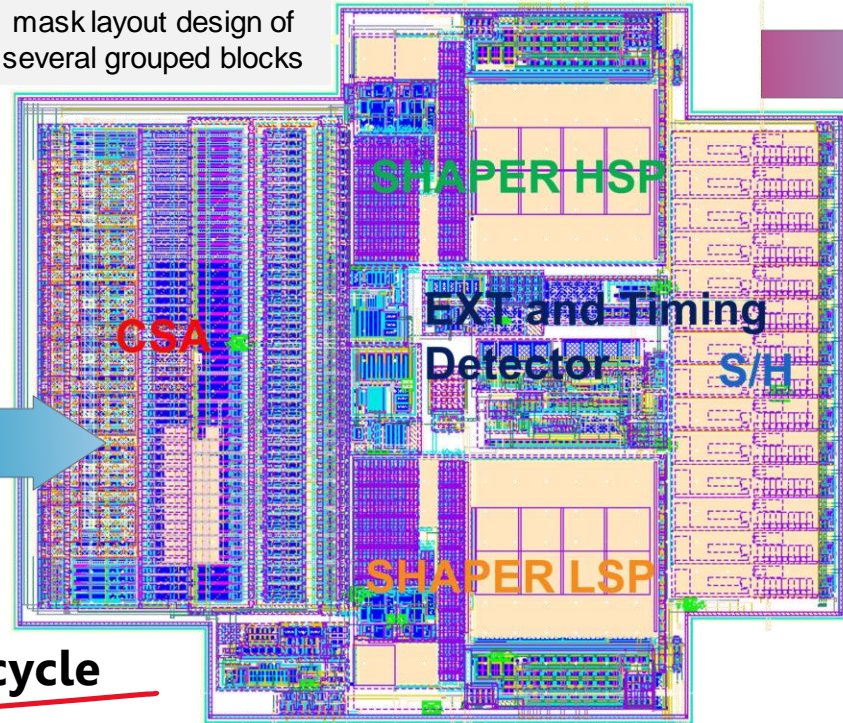
## ASIC lifecycle

mask layout design of several grouped blocks



scientific instruments  
scientific instruments

full ASIC layout

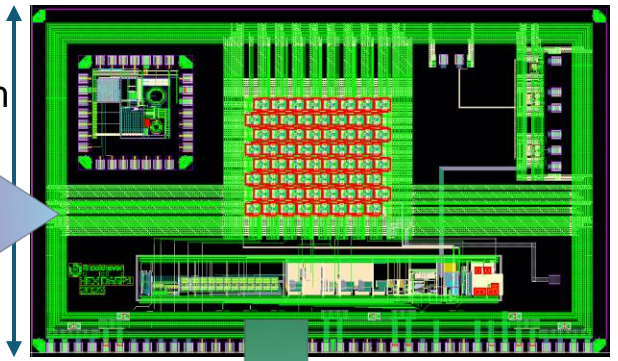


5 mm




Silicon foundry (manufacturing)



testing of ASICs

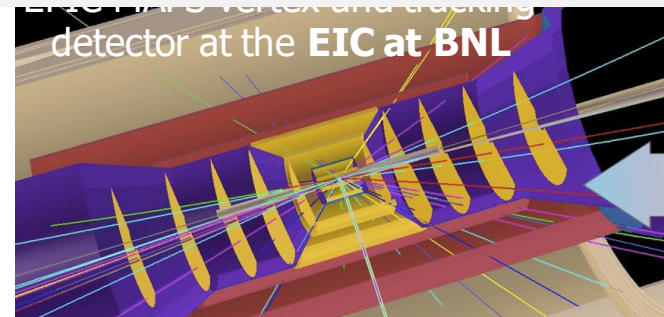


detector at the EIC at BNL

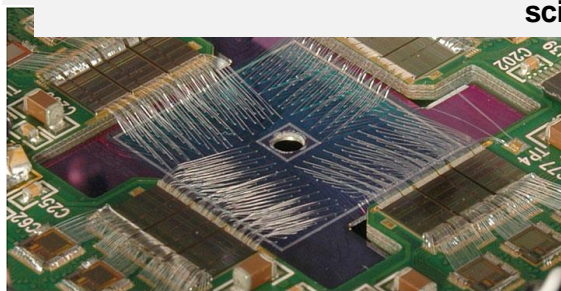

MAIA 20x20 (BNL)


# Transistors + IC Technology - 2

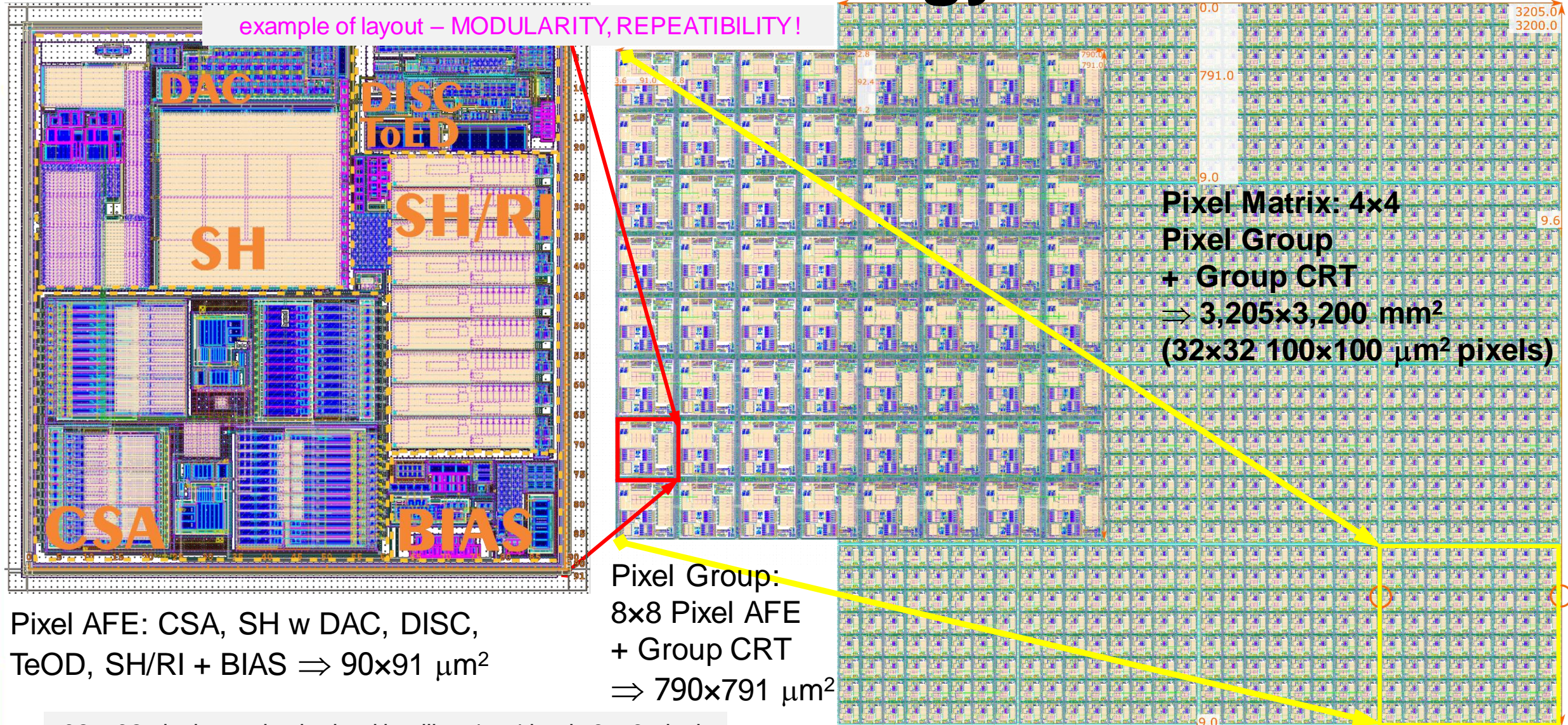

32 x 32 pixels matrix obtained by tiling 4 x 4 basic 8 x 8 pixels groups ⇒ suitable for continued tiling.

# Transistors + IC Technology - 3

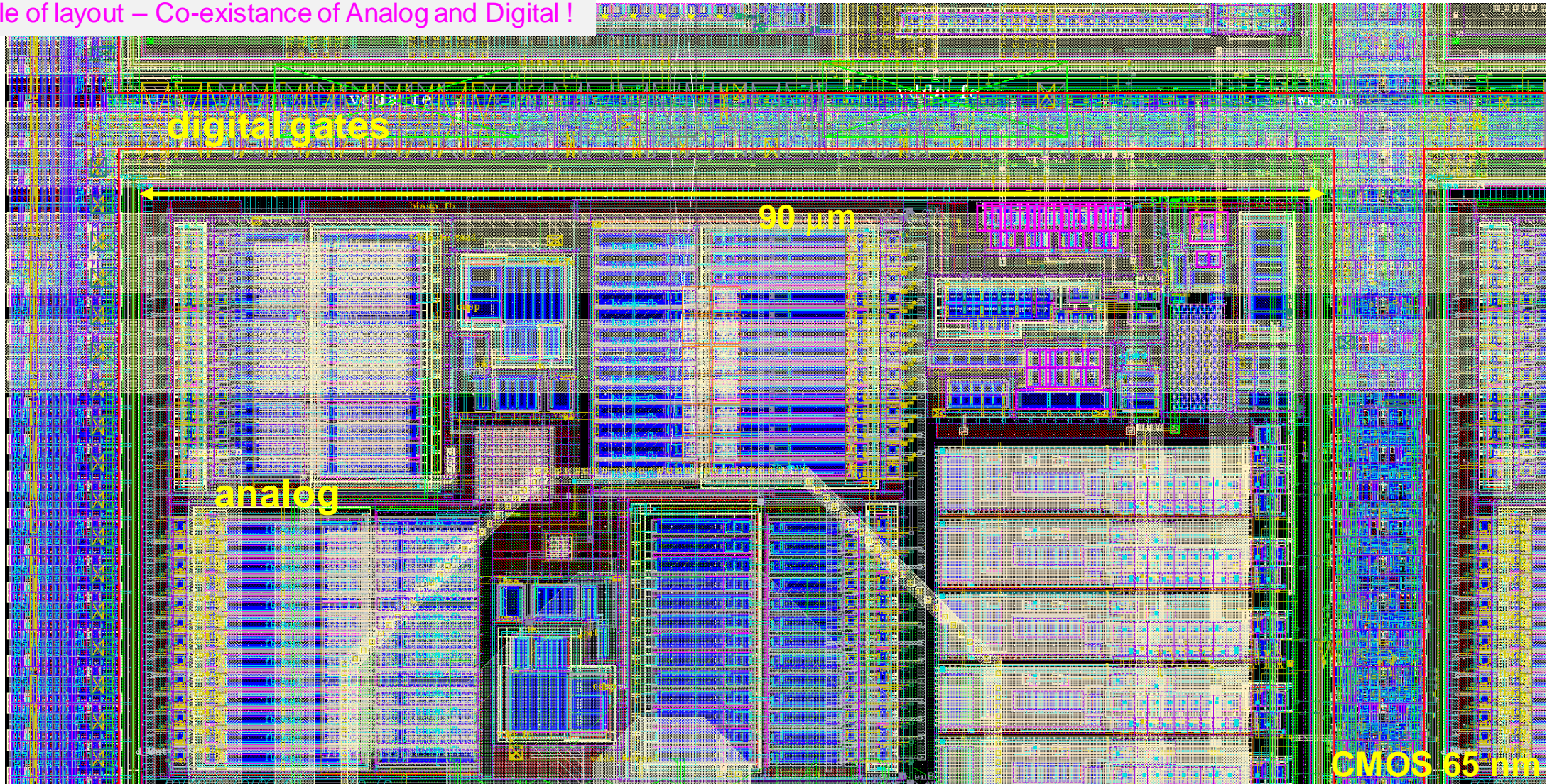example of layout – Co-existence of Analog and Digital !



# Application

## High Energy Physics

### CMS DETECTOR

Total weight : 14,000 tonnes  
 Overall diameter : 15.0 m  
 Overall length : 28.7 m  
 Magnetic field : 3.8 T

STEEL RETURN YOKE  
 12,500 tonnes

SILICON TRACKERS  
 Pixel (100x150 μm) ~1m<sup>2</sup> ~66 M ch.  
 Microstrips (80x180 μm) ~200m<sup>2</sup> ~9.6 M ch.

### SILICON TRACKERS

Pixel (100x150 mm<sup>2</sup>) ~1 m<sup>2</sup> ~66 M ch.)

Microstrips (80x180 mm<sup>2</sup>)

~200 m<sup>2</sup> ~9.6 M ch.)

SUPERCONDUCTING SOLENOID  
 Niobium titanium coil carrying ~18,000A


MUON CHAMBERS  
 Barrel: 250 Drift Tube, 480 Resistive Plate Chambers  
 Endcaps: 540 Cathode Strip, 576 Resistive Plate Chambers

PRESHOWER  
 Silicon strips ~16m<sup>2</sup> ~137,000 channels

FORWARD CALORIMETER  
 Steel + Quartz fibres ~2,000 Channels

CRYSTAL ELECTROMAGNETIC CALORIMETER (ECAL)  
 ~76,000 scintillating PbWO<sub>4</sub> crystals

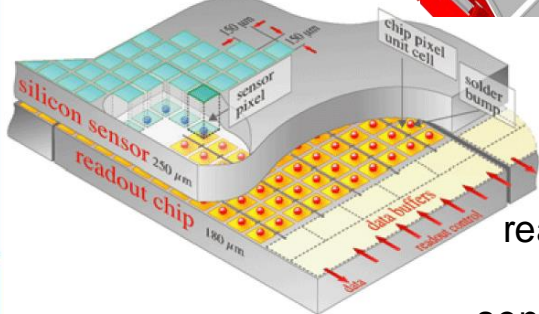HADRON CALORIMETER (HCAL)  
 Brass + Plastic scintillator ~7,000 channels




### CMS (CERN)

<https://cms.cern/detector/identifying-tracks/silicon-pixels>

readout channels are laid out in 2D matrix connected to sensor elements at same pitch



## Nuclear Physics

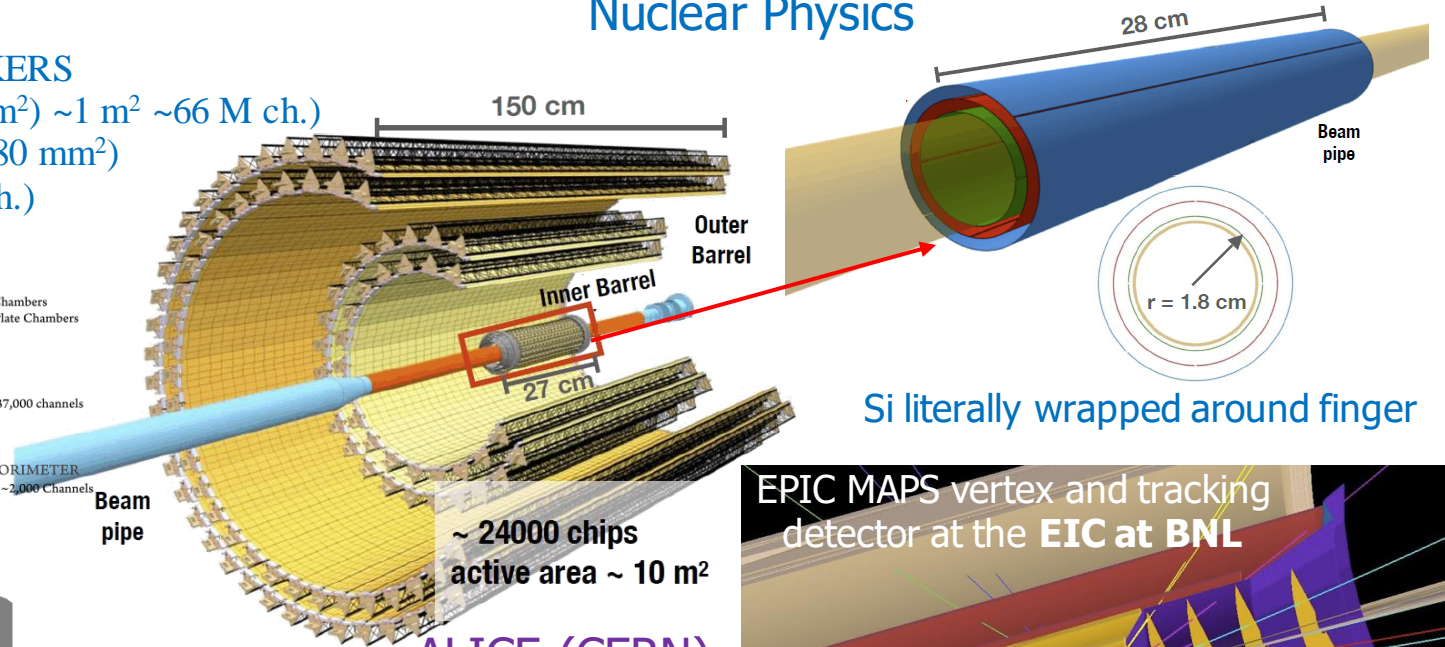



Si literally wrapped around finger

~ 24000 chips  
 active area ~ 10 m<sup>2</sup>


### ALICE (CERN)

Astrophysics,  
 Photon Science (X-ray detection)

EPIC MAPS vertex and tracking detector at the EIC at BNL

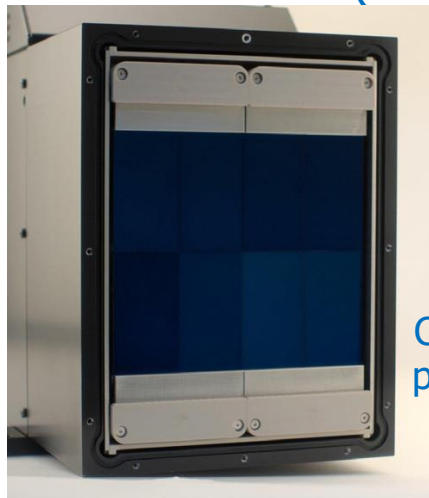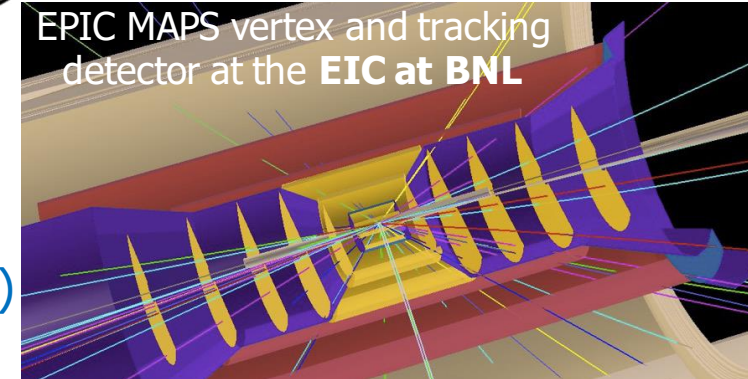

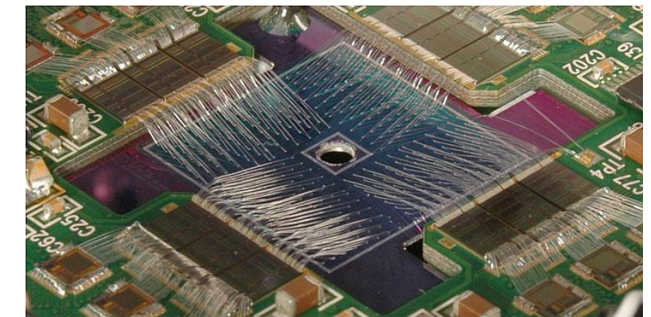CITIUS 2.2 M  
 pixel detector  
 assembly  
 (RIKEN)



MAIA 20x20 (BNL)

# Introduction to IC Technology - 1




construction of vacuum tubes was complex, their cost was high, but above all they were bulky (not good candidates for miniaturization)




tubes are still loved by audiophiles for soft, warm and highest fidelity in sound

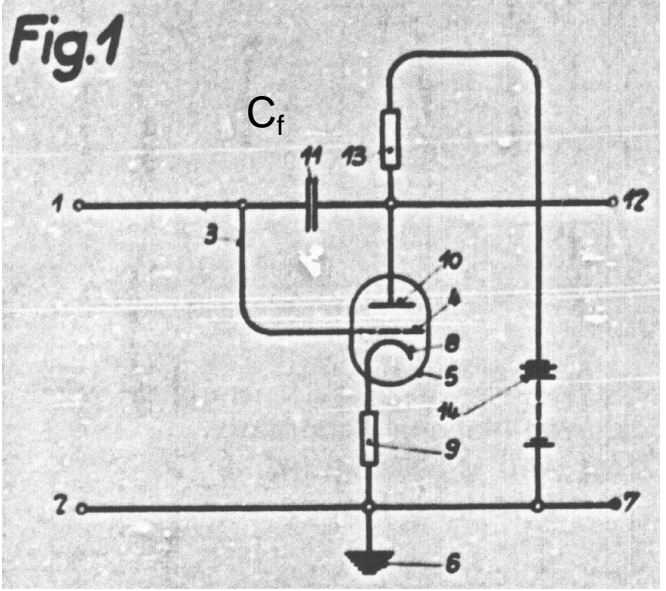first electronic components, allowing nonlinear functions were vacuum tubes




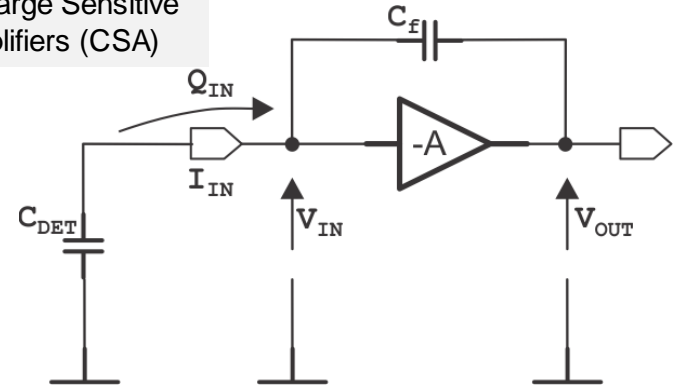Integrator circuit is basic building block of Charge Sensitive Amplifiers (CSA)







# Introduction to IC Technology - 2

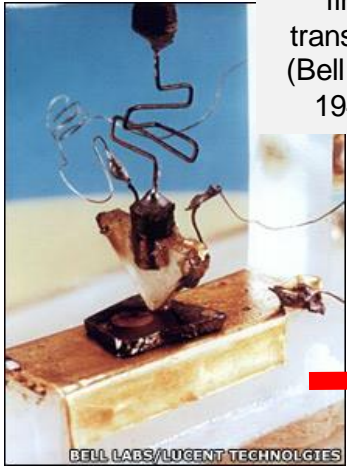


first transistor (Bell Labs 1947)

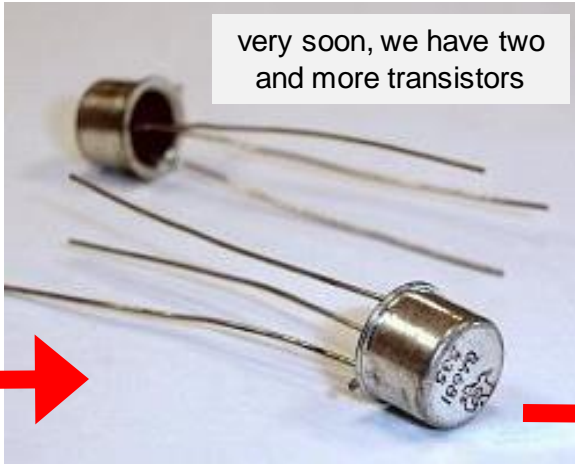

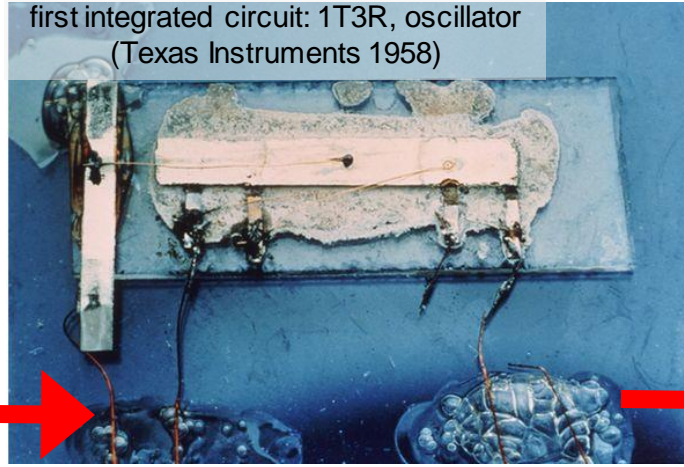very soon, we have two and more transistors



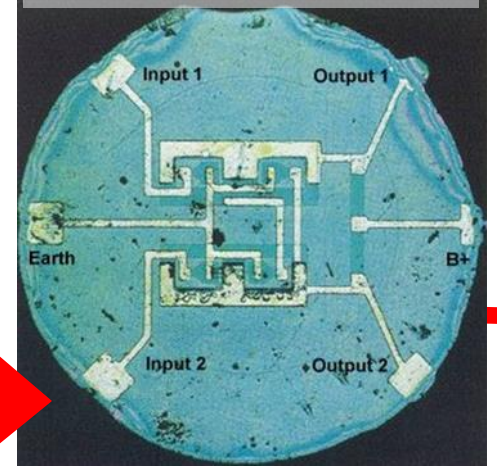
first integrated circuit: 1T3R, oscillator (Texas Instruments 1958)



first monolithic integrated circuit: logic (Fairchild 1961)




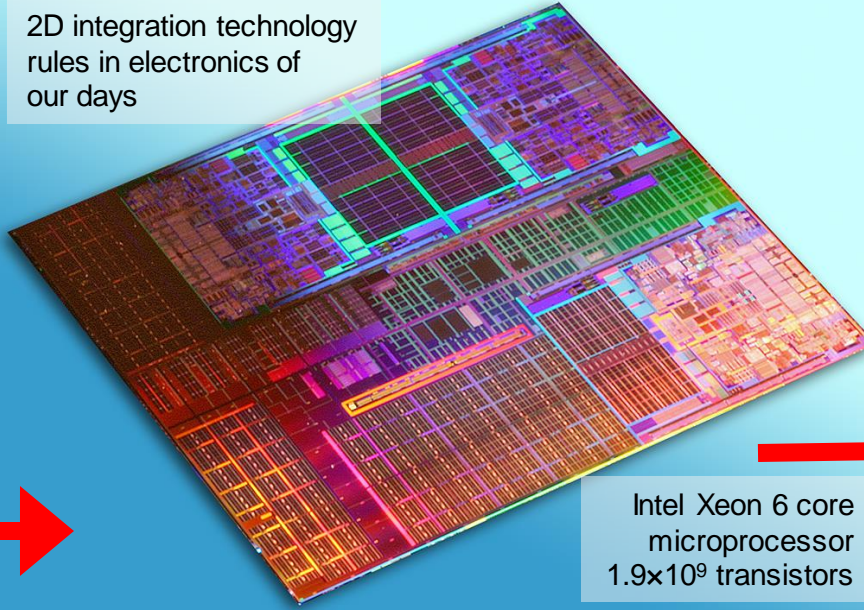more and more components, more and more functions, growing complexity



2D integration technology rules in electronics of our days

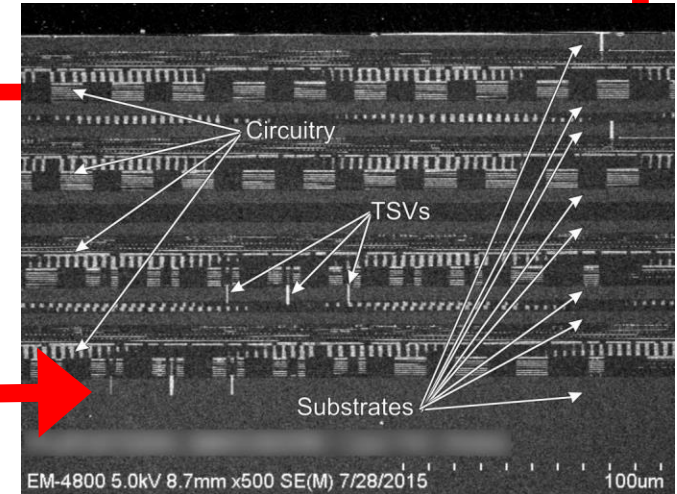
Intel Xeon 6 core microprocessor  $1.9 \times 10^9$  transistors



Integration in 2D is not enough  $\rightarrow$  3D



8-layer stack of integrated circuits interconnected vertically (Tezzaron)

# Transistors and Amplifiers - 1

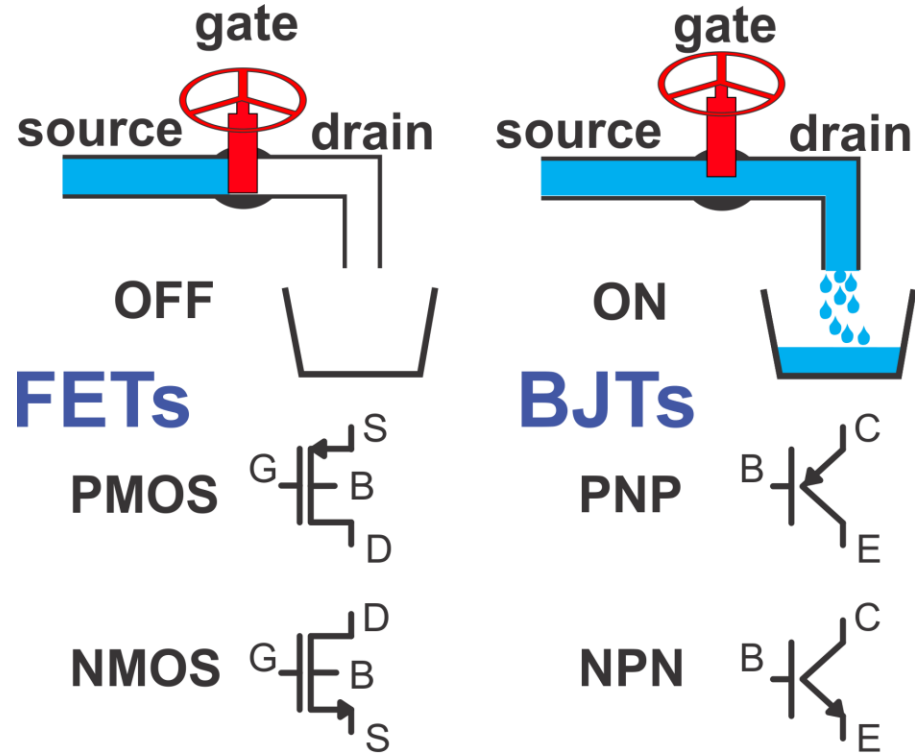


This is how we built amplifier:

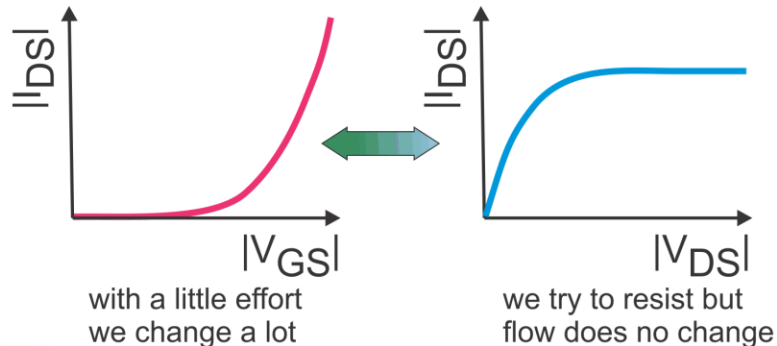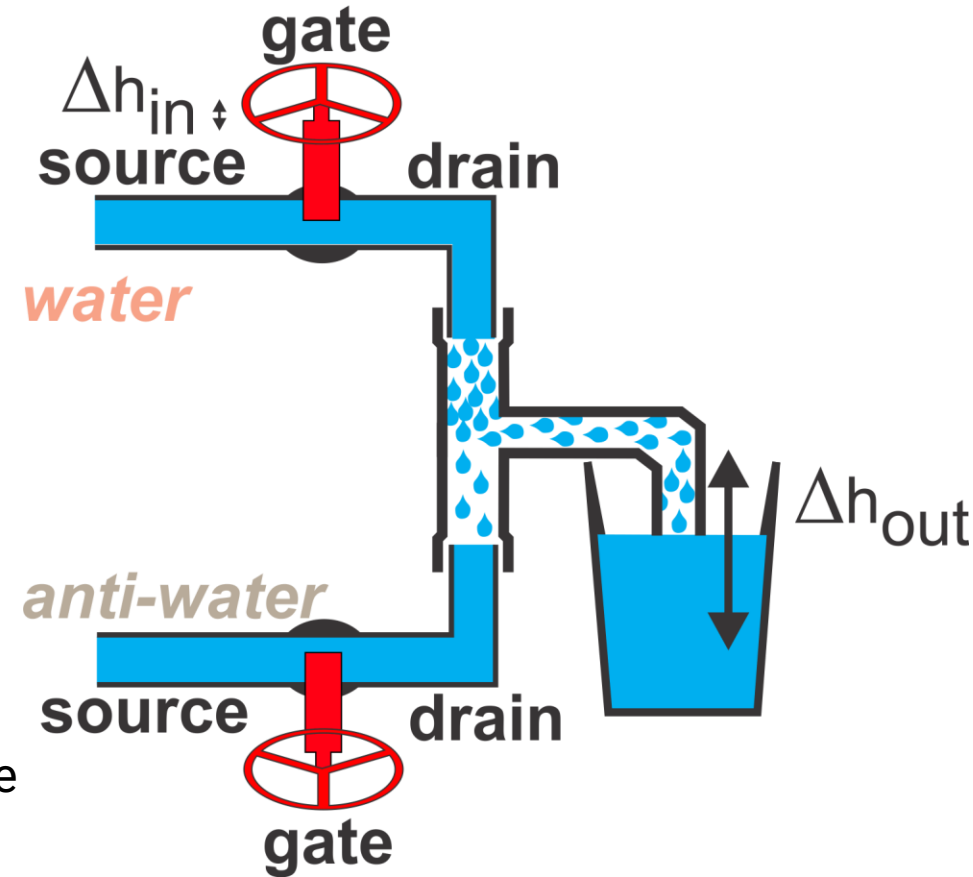- resistance of a finger loads a faucet,
- water stream, set by turning knob just a little bit, pushes measurably on our finger




# Transistors and Amplifiers - 2

Why can we amplify signals?

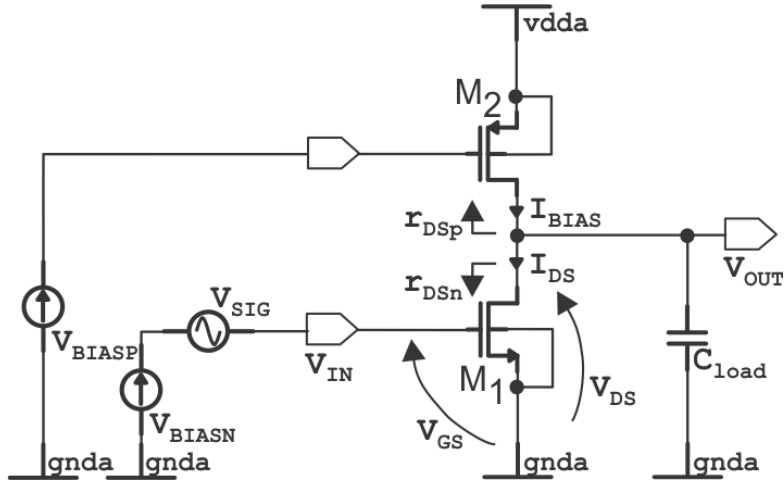


input signal applied to gate on top of bias voltage



"transfer" characteristics

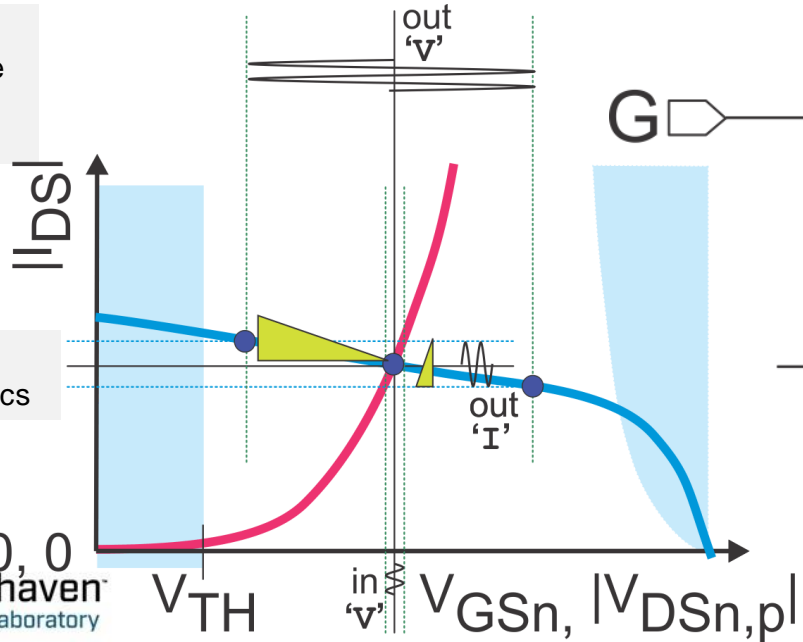

input characteristics

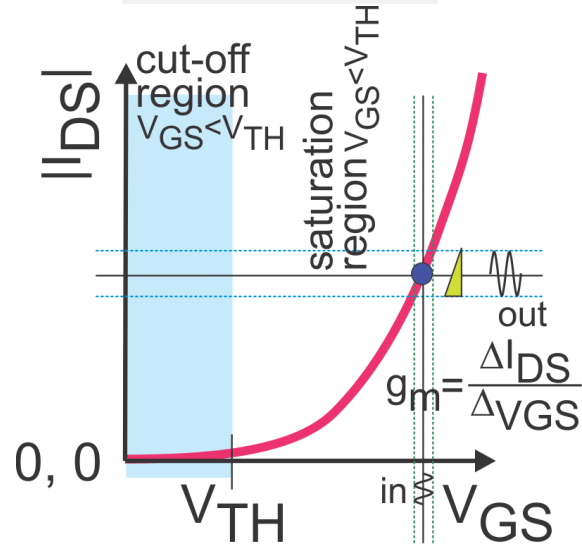

output characteristics

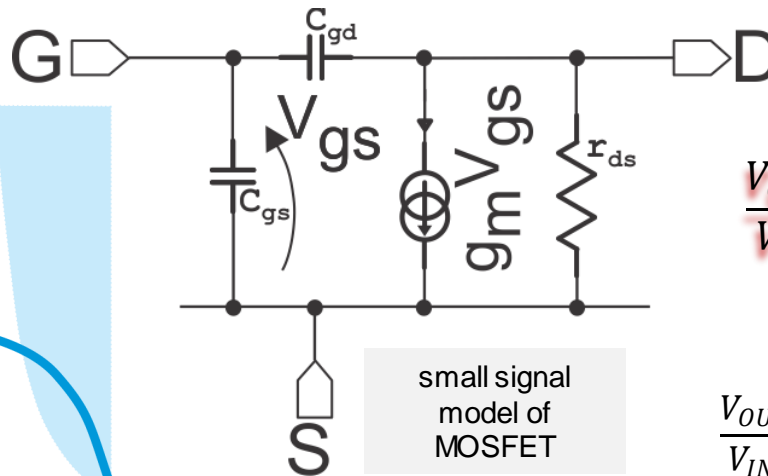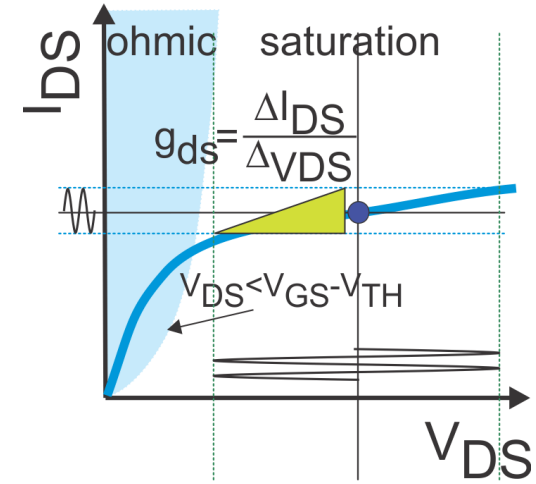

small signal model of MOSFET

$$\frac{V_{OUT}}{V_{IN}} = -\frac{g_m}{g_{dsn} || g_{dsp}}$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{g_m (r_{dsn} \cdot r_{dsp})}{r_{dsn} + r_{dsp}}$$

assume N and P identical

$$\rightarrow \frac{V_{OUT}}{V_{IN}} = -\frac{g_m r_{ds}}{2}$$


What to do with C\_load?

$$\frac{V_{OUT}(s)}{V_{IN}(s)} = -g_m \frac{r_{ds}}{2} || C_{load} = -g_m \frac{r_{ds}}{2(1 + sC_{load} \frac{r_{ds}}{2})}$$

bandwidth limitation
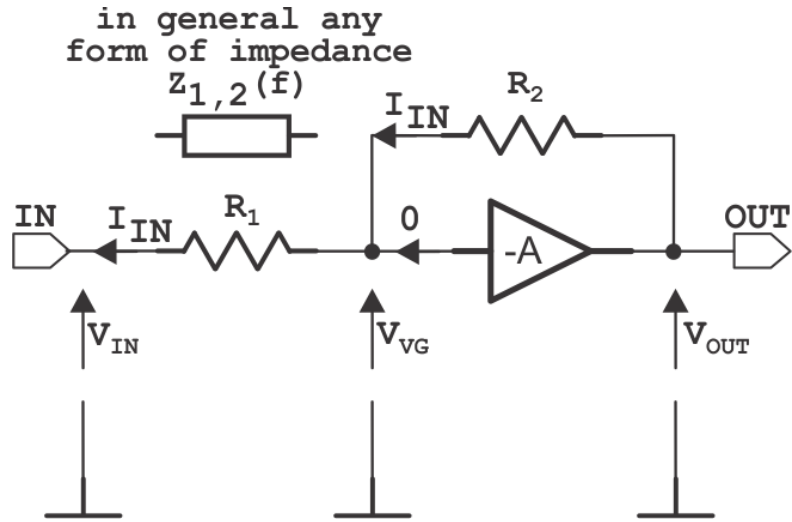
# Transistors and Amplifiers - 3

basic, inverting voltage amplifier with operational amplifier



writing down Kirchhoff's Voltage and Current Laws:

$$\left\{ \begin{array}{l} V_{IN} + IR_1 - V_{VG} = 0 \\ V_{VG} + IR_2 - V_{OUT} = 0 \\ V_{OUT} = -AV_{VG} \\ I_{IN} - 0 - I_{IN} = 0 \end{array} \right. \longrightarrow I_{IN} = \frac{V_{VG} - V_{IN}}{R_1}, I_{IN} = \frac{V_{OUT} - V_{VG}}{R_2}$$

$$\frac{V_{VG} - V_{IN}}{R_1} = \frac{V_{OUT} - V_{VG}}{R_2}$$

substituting for  $V_{VG} = -\frac{V_{OUT}}{A}$

$$\left( \frac{-\frac{V_{OUT}}{A} - V_{IN}}{R_1} \right) = \left( \frac{\frac{V_{OUT}}{A} + V_{OUT}}{R_2} \right)$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_2}{\frac{R_1 + R_2}{A} + R_1} \longrightarrow \lim_{A \rightarrow \infty} -\frac{R_2}{\frac{R_1 + R_2}{A} + R_1} = -\frac{R_2}{R_1}$$

$$H(j\omega) = \frac{V_{OUT}(j\omega)}{V_{IN}(j\omega)} = -\frac{Z_2(j\omega)}{Z_1(j\omega)} \quad \text{for } s = j\omega, H(s) = -\frac{Z_2(s)}{Z_1(s)}$$

if  $Z_2$  is capacitor  $C_2$ :  $H(s) = -\frac{1}{sC_2R_1}$  ideal integrator

if  $Z_2$  is resistor||capacitor:  $H(s) = -\frac{R_2}{R_1(1 + sC_2R_2)}$  lossy integrator

if  $Z_1$  is capacitor:  $H(s) = -sC_1R_2$  differentiator

## Operational amplifier:


- infinite input impedance  $\rightarrow$  no current flowing into input of amplifier;
- infinite voltage gain  $\rightarrow$  needs feedback circuit to operate, otherwise act as inverter/comparator ;
- infinite frequency bandwidth  $\rightarrow$  characteristics decided by feedback network;
- zero output impedance  $\rightarrow$  can act as voltage source;

Operational amplifier does not exist in nature, but it is well approximated by actual designs:


- input impedance  $\rightarrow$   $M\Omega$ - $G\Omega$  with dominating capacitive component;
- voltage gain  $\rightarrow$  100dB;  $M\Omega$ - $G\Omega$ ;
- frequency bandwidth  $\rightarrow$  low, kHz, but due to gain-bandwidth exchange sufficient;
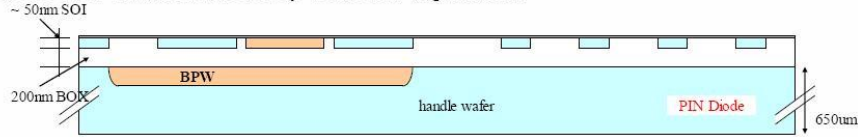
# Sensors and readout ICs


① Gate SiO<sub>2</sub> Oxidation followed by Well, BPW Implantation



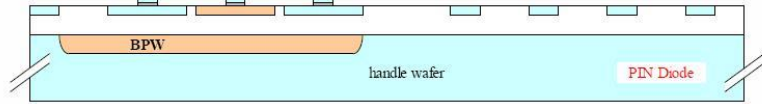
② After Gate stack formation ( with extension and sidewall formations )



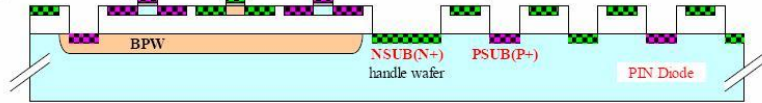
③ BW(NSUB,PSUB) photo/etching and S/D, NSUB, PSUB Implantation




④ S/D annealing and Salicidation

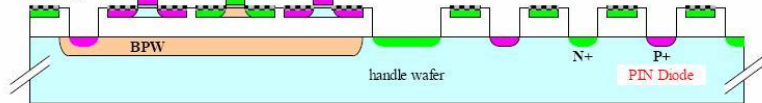

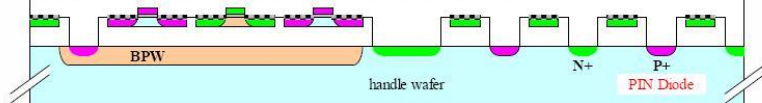
⑤ 1st ILD filling and CMP planarization ( after Salicide formation )



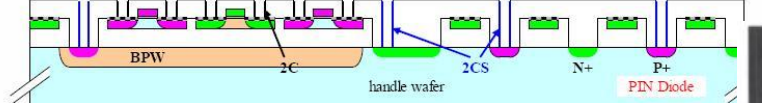⑥ Contact etching ( 2CS for substrate and 2C for S/D and gate of transistor )




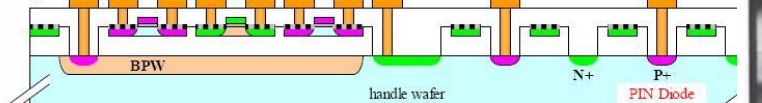⑦ Contact plug filling and 1st Metal formation




⑧ BEOL ( 2 ~ 4th Metal formation )

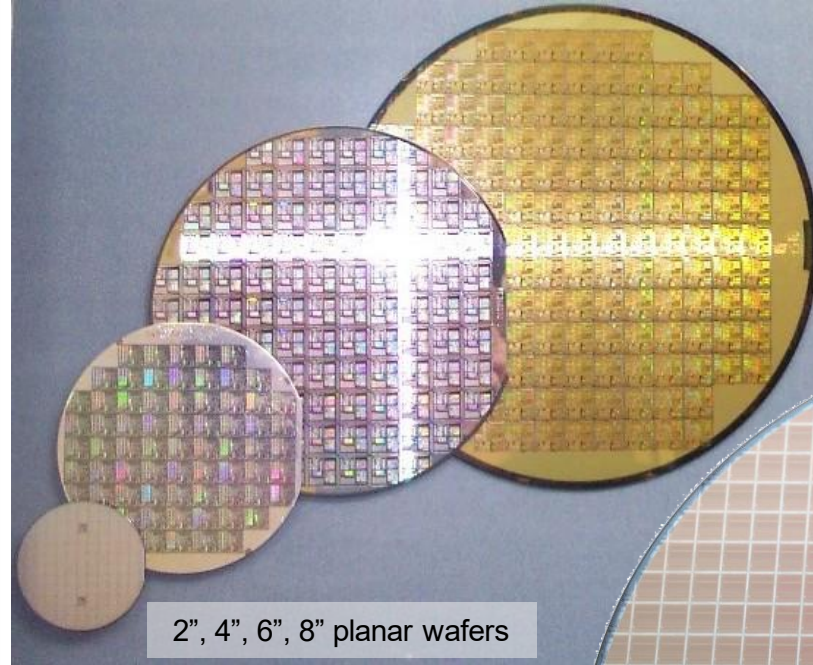followed by Backside polishing and Metal coating




2", 4", 6", 8" planar wafers

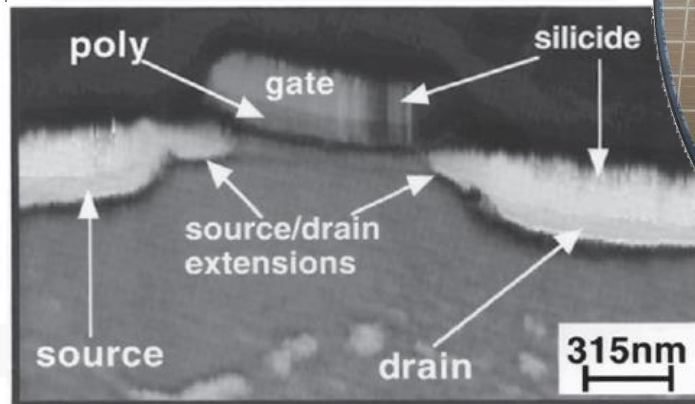X-section of NMOS transistor seen in Scanning Resistance Microscope



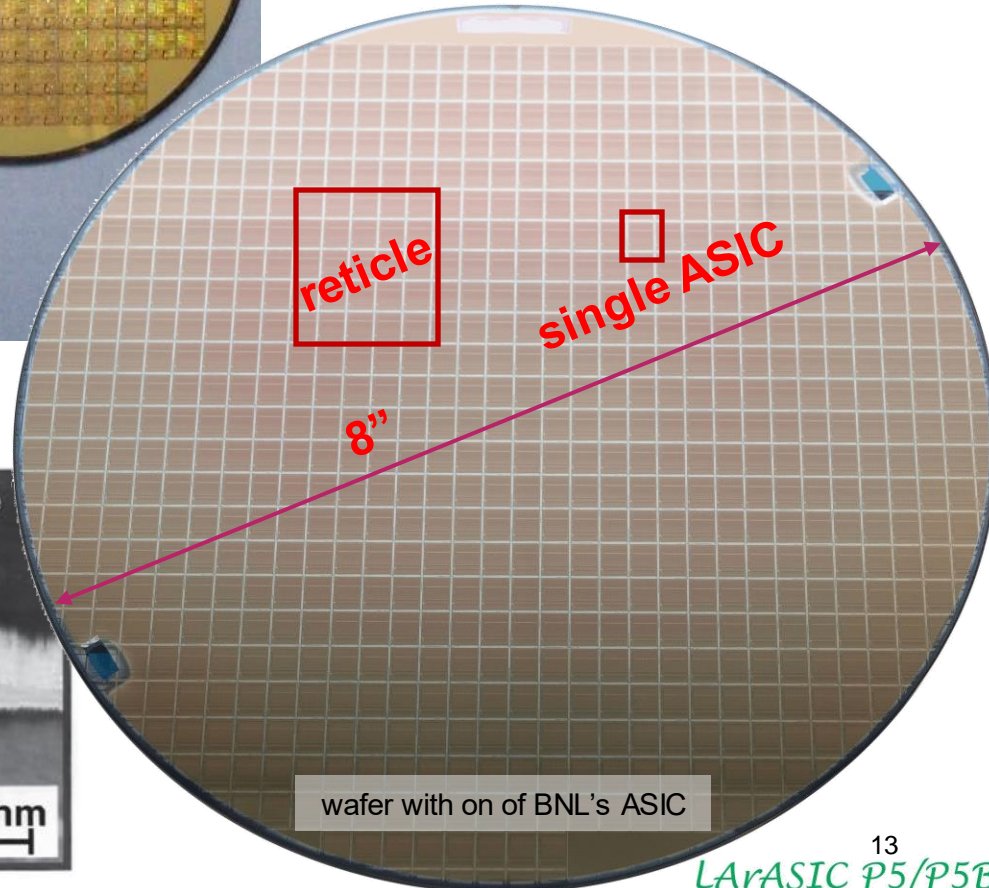- sensors and ICs are fabricated in similar way, using multiple steps of planar processing



wafer with on of BNL's ASIC



# Geometries of Solid-State Sensors

## STRIPS
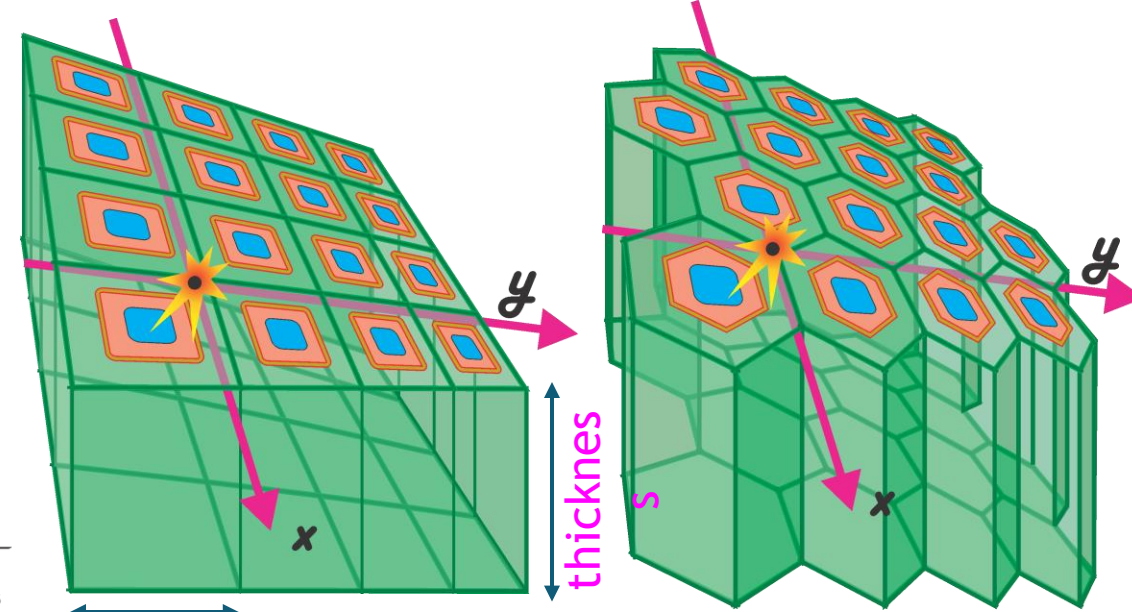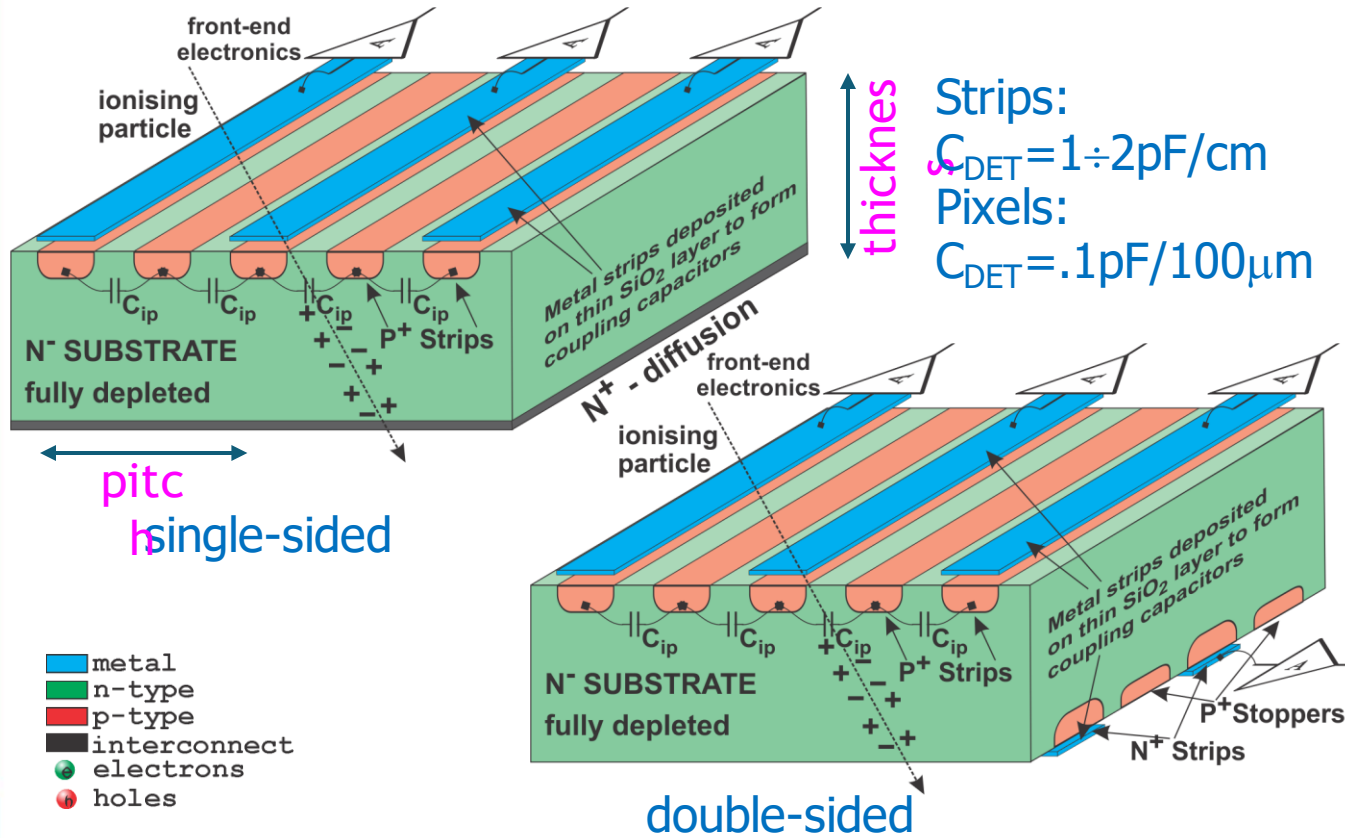
## PIXELS


Strips sensors deliver 1D - (sometimes 2D – but prone to ambiguity) aware information about incident radiation

Pixel sensors deliver 2D - (sometimes 3D) aware information about incident radiation



both types of sensors may be used to measure time of arrival


# Readout ICs

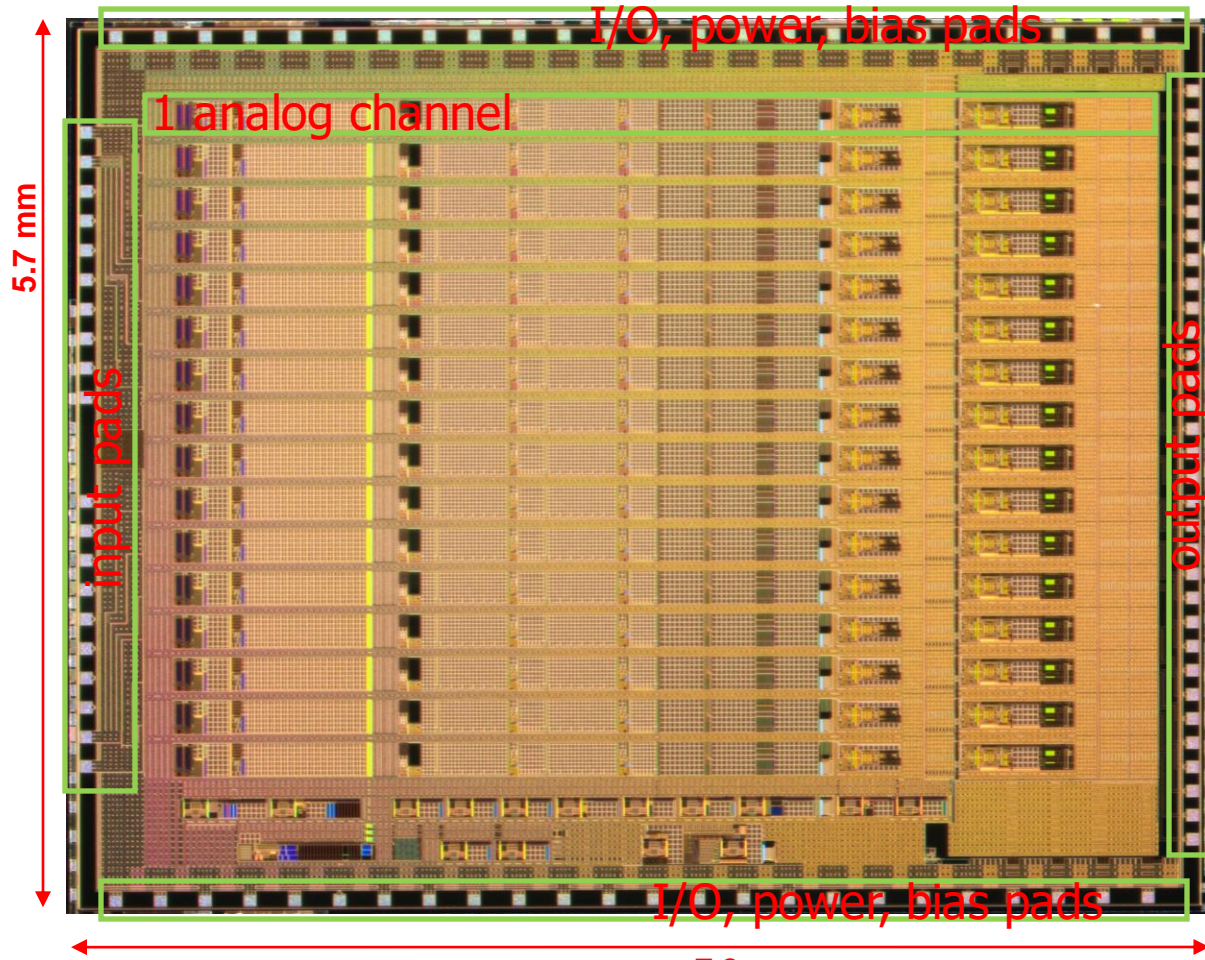

① LArASIC\_P4 180 nm CMOS

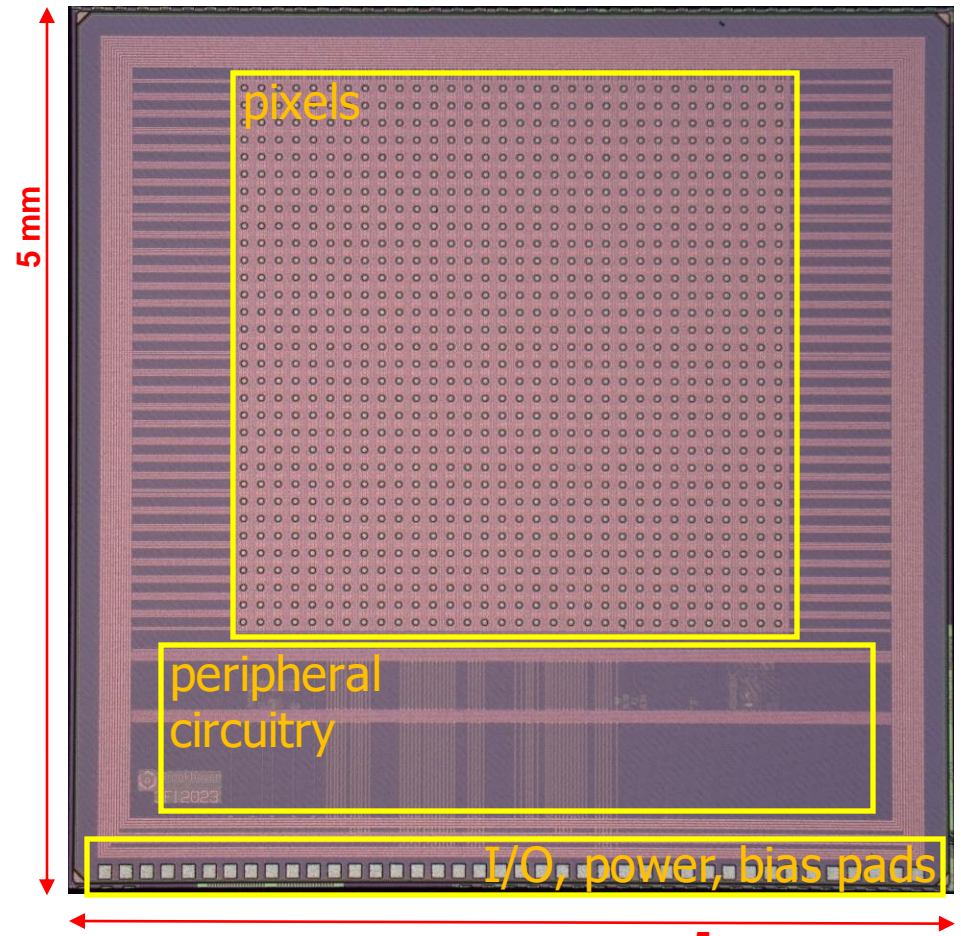7.2 mm

[16 channel Analog Front-End for liquid Ar TPC readout]



① 3FI65P1 65 nm CMOS

5 mm

[pixel readout IC 32x32 pixels @100  $\mu\text{m}$  sq pitch]

# Typical charge processing chain - 1

## Sensors read out by charge sensitive electronics:

- deliver at their output short current pulse, whenever ionizing radiation interacts with their sensitive regions;
- charge carried by output current pulse of sensor is linearly related to energy released by radiation in sensitive region of sensor (mean value);
- typically produce small portions of charge:
  - small energy released;
  - low sensor's sensitivity;

Noise of first amplification stages degrades accuracy in measurements

Accuracy may also be degraded when:

- sensor is exposed to relatively high radiation intensity → time separation between single events is short, leading to:
  - baseline fluctuations;
  - pulse-on-pulse pile-up effects;
- time which is available to perform charge measurements is reduced (e.g., beam crossing cadence);
- interferences, common modes, ground bouncing, etc. → baseline fluctuations ;

## Measurement of energy released by nuclear event in sensitive region of sensors must be considered performed:

- once analog quantity which carrier information of such energy, or charge delivered by sensors, is converted by Analog-to-Digital converter (ADC) or Time-to-Digital Converter (TDC) into number;
- and obtained number is stored in digital memory;


## To be suitable for ADC, current pulse delivered by sensor must undergo several operations:

- aiming at delivering to ADC signal with suitable characteristic to guarantee correct conversion (antialiasing);
- reducing accuracy degradation.




# Typical charge processing chain - 2

circuit diagram

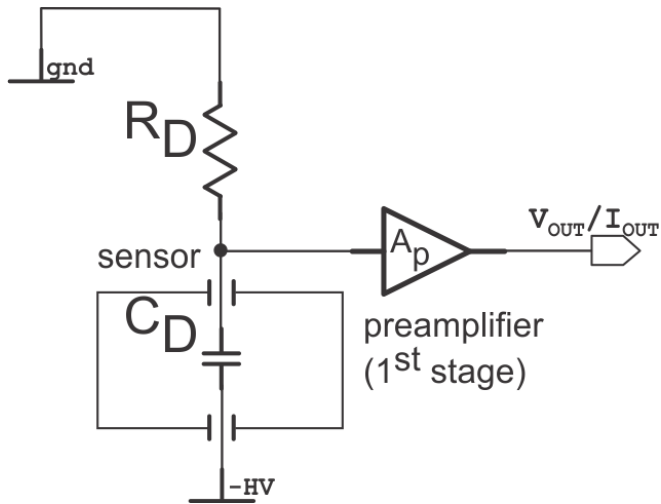

$A_p$  provides voltage gain – voltage mode processing

equivalent circuit

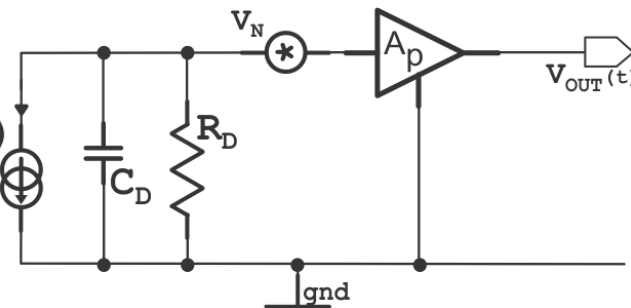


response to single charge pulse:

$$V_{OUT}(t) = -A_p \frac{Q}{C_D} e^{-t/R_D C_D} + A_p V_N(t)$$

response depends on  $C_D$  that may change with for example HV bias applied

waveform at output of preamplifier

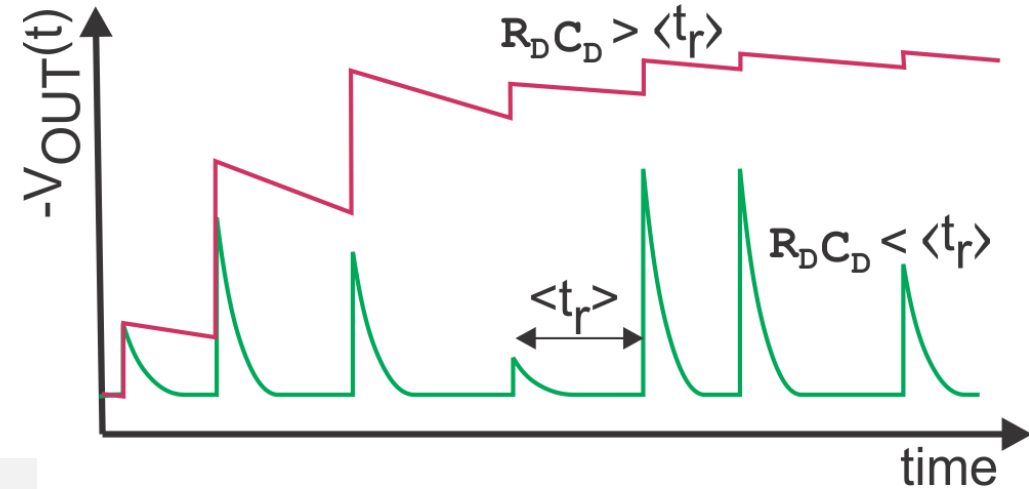


If  $C_D R_D$  too big output of AP saturates and becomes insensitive

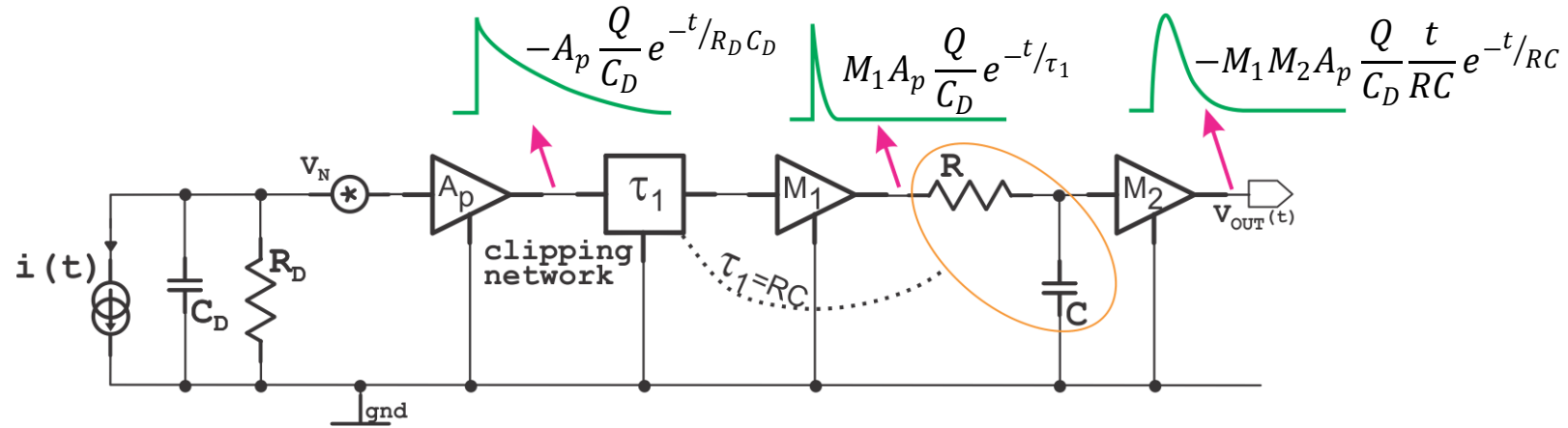
# Typical charge processing chain - 3

not rigorous in representing polarity

How to prevent saturation: clipping network aka pole-zero cancellation



two ways of achieving clipping

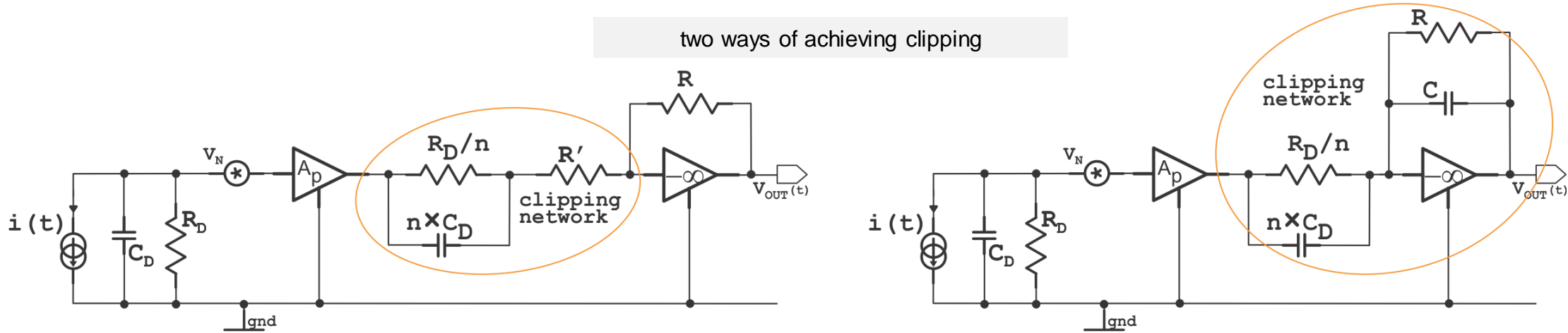


ratio  $R/R'$  allows adding voltage gain
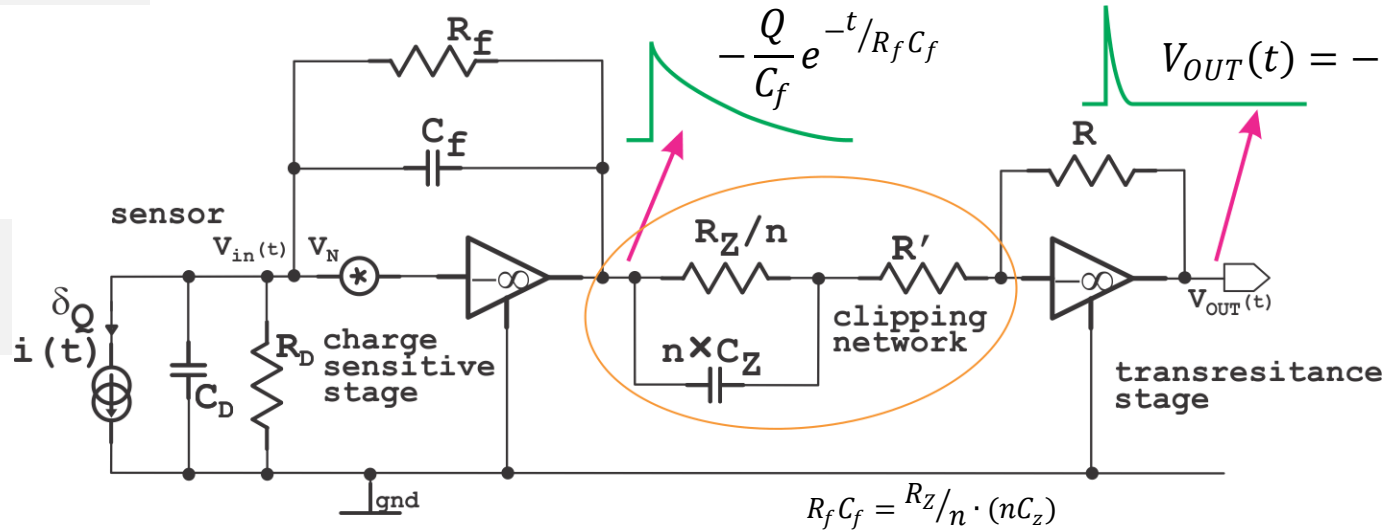
# Typical charge processing chain - 4

How to make response independent of  $C_D$ :

because of infinite gain of amplifier, there is no current flowing through  $C_D$  and  $R_D$





$$-\frac{Q}{C_f} e^{-t/R_f C_f}$$

$$V_{OUT}(t) = -\frac{R}{R+R'} Q \frac{R'(nC_f)}{C_f} e^{-t / \frac{R_f C_f}{1 + \frac{R'}{R}}}$$

not rigorous in representing polarity

signal amplitude is multiplied how many times  $nC_f$  is larger than  $C_f$   
charge gain

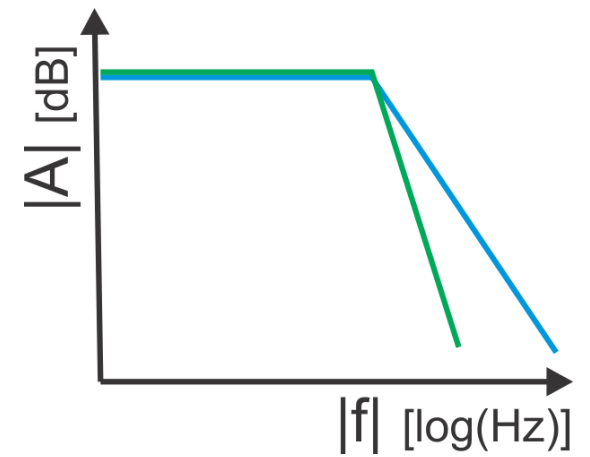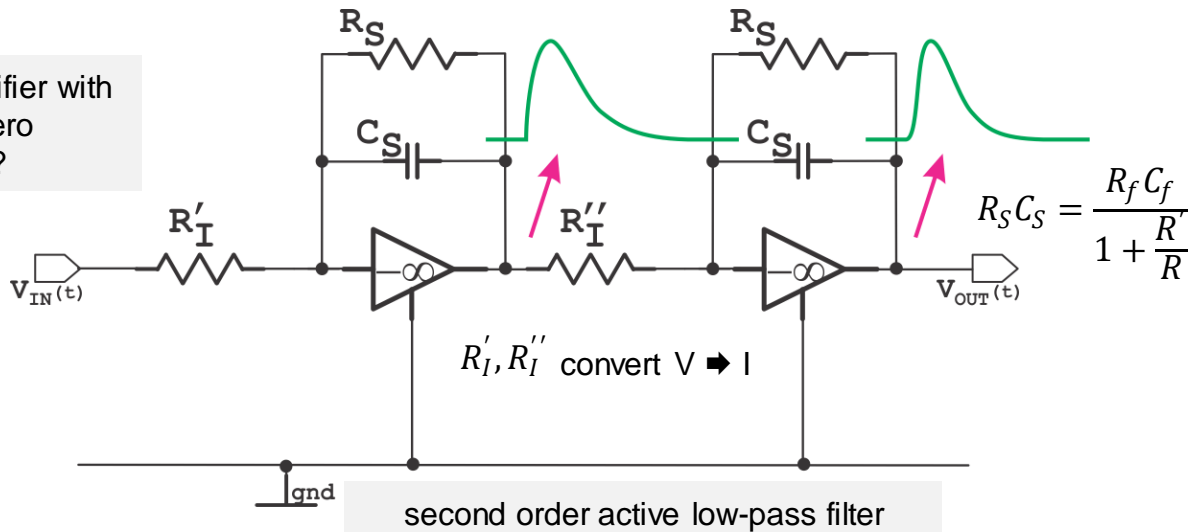
what follows preamplifier with clipping (pole-zero cancellation)?



# Typical charge processing chain - 6

ADVANCED

Other options of filters:

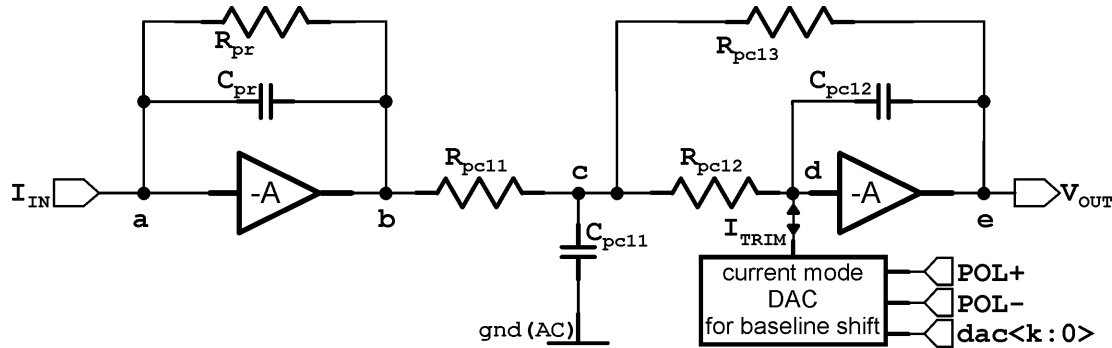

$$R_{pr} = 571.6 \text{ k}\Omega$$

$$C_{pr} = 304 \text{ fF}$$

$$R_{pc11} = 183.2 \text{ k}\Omega / 7 = 26.17 \text{ k}\Omega$$

$$C_{pc11} = 4.52 \text{ pF}$$

$$R_{pc12} = 183.2 \text{ k}\Omega$$

$$C_{pc12} = 304 \text{ pF} / 2 = 152 \text{ pF}$$


$$R_{pc13} = 183.2 \text{ k}\Omega$$

$$I_{\text{current DAC}} = \pm 250 \text{ nA (baseline)} + 1 \mu\text{A (polarity)}$$

- capacitance  $C_c$  is coupling capacitance for last stage of CSA

3<sup>rd</sup> order semi-gaussian shaping filter with one real pole and one pairs of complex conjugate poles
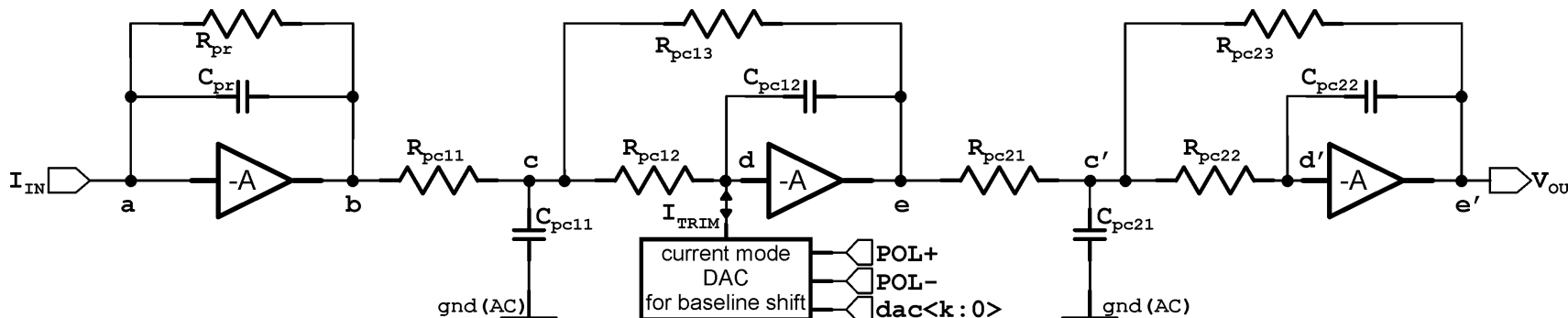
$$H_t(s) = \frac{1}{s} \frac{-sC_c R_{pr}}{sC_{pr}R_{pr} + 1} \frac{1}{s^2 C_{pc11} C_{pc12} R_{pc12} R_{pc13} + sC_{pc12} R_{pc12} \left(1 + \frac{R_{pc13}}{R_{pc11}} + \frac{R_{pc13}}{R_{pc12}}\right) + 1} = \frac{-sC_c R_{pr}}{sC_{pr}R_{pr} + 1} \frac{-A_v}{\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q} + 1}$$






- DAC current injected into node 'd' to avoid additional parallel noise that would be added in case of using the node 'a',
- relatively large value of  $R_{pc12}$  allows achieving efficient voltage shifts of baseline with low current of DAC that limits power consumption.
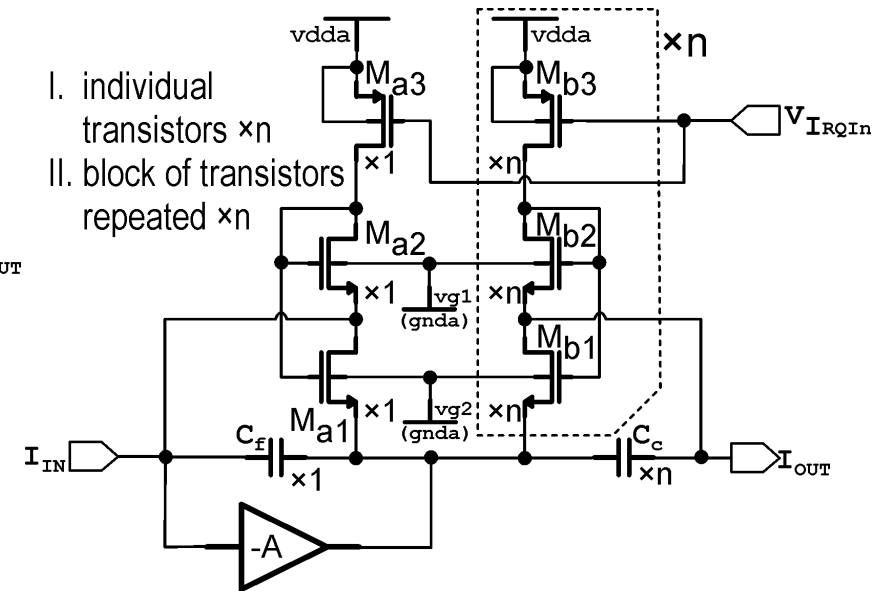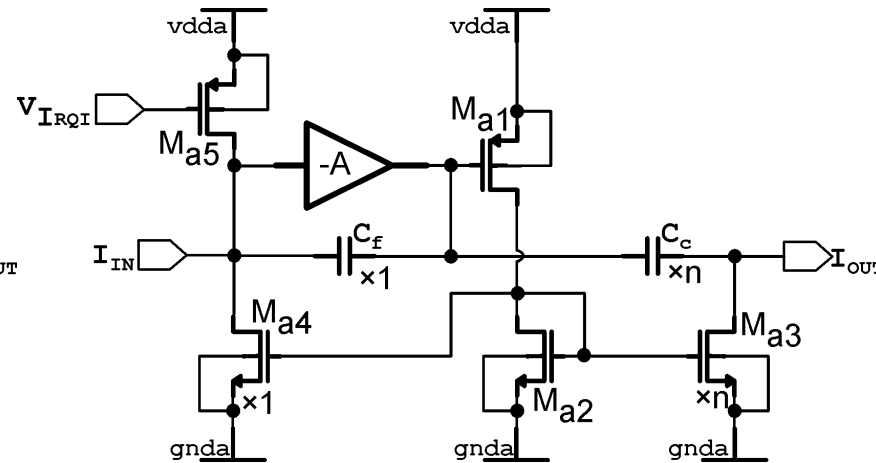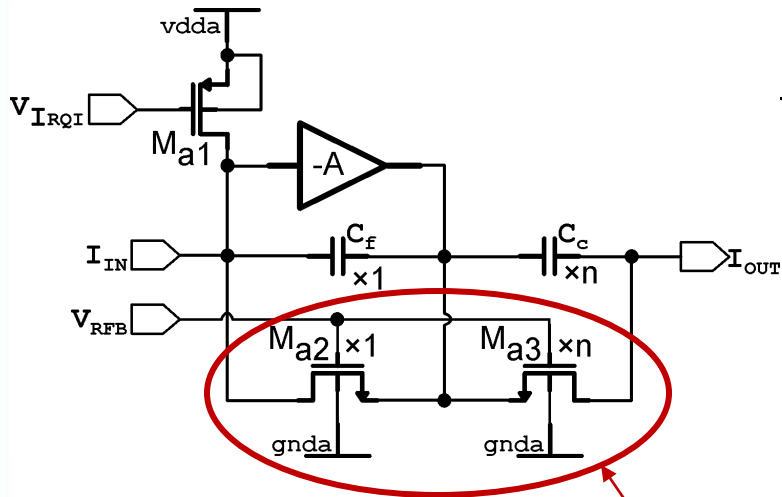
# Typical charge processing chain - 7

ADVANCED

How preamplifier is designed with no resistors:




[♦] G. De Geronimo et al, "A CMOS detector leakage current self-adaptable continuous reset system: theoretical analysis", Nucl. Instr. Meth. A 421 (1999) 322-333

[♥] G. De Geronimo et al, "Front-End ASIC for a GEM Based Time Projection Chamber", IEEE Trans. Nucl. Sci Vol. 51, No. 4, August 2004 1313-1317

[♣] G. W. Deptuch, P. Otfinowski, "Charge Sensitive Amplifier with Pole-Zero Cancellation", provisional patent application USPTO Serial No. 63/379,887

still one can see resistors !  
resistance of transistors' channels  
controlled by gate voltages

# Typical charge processing chain - 8

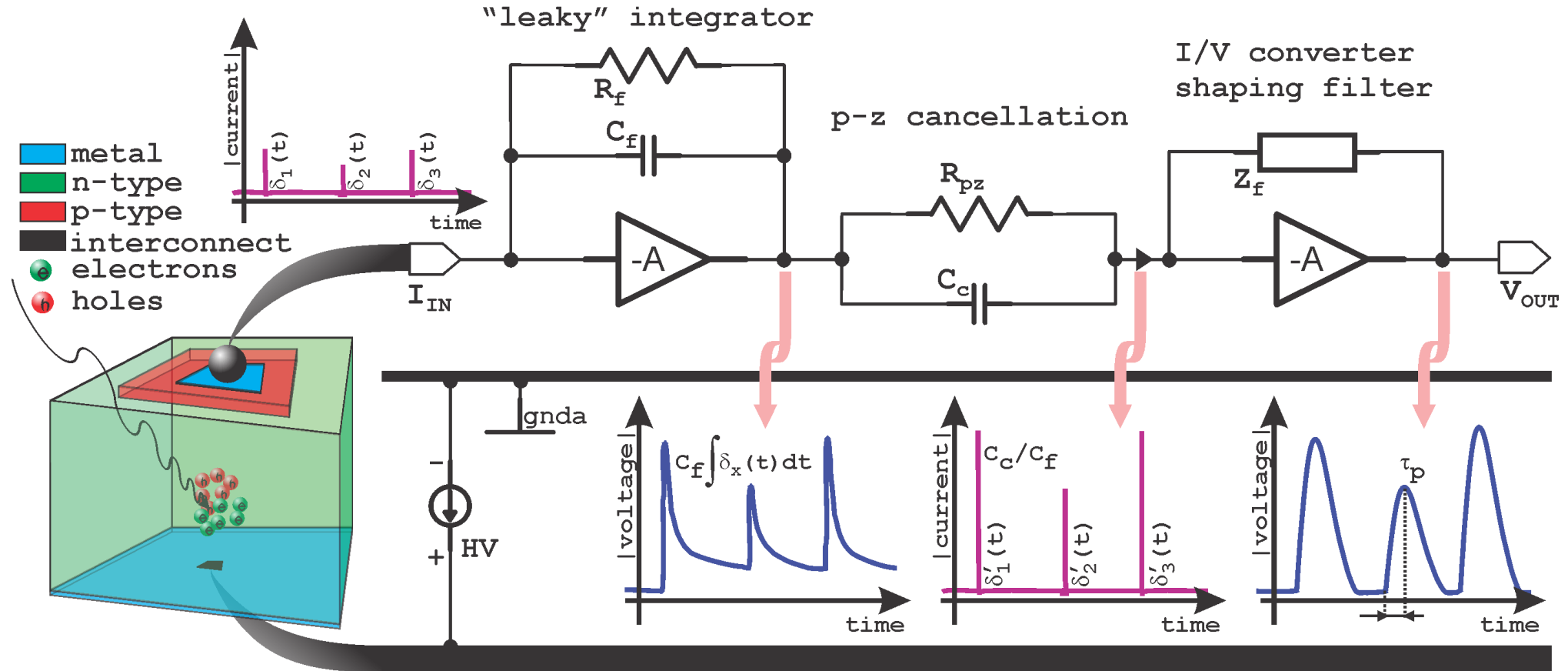

characteristic parameters of typical materials for semiconductor sensors

| quantity                                       | Si   | Ge   | GaAs | Diamond | CdTe | Cd <sub>0.9</sub> Zn <sub>0.1</sub> Te | TlBr | a-Si |
|--|------|------|------|---------|------|--|------|------|
| $E_g$ [eV]                                     | 1.12 | 0.67 | 1.43 | 5.50    | 1.44 | 1.57                                   | 2.68 | 1.90 |
| $W$ [eV]                                       | 3.60 | 2.96 | 4.20 | 13.00   | 4.43 | 4.64                                   | 6.50 | 6.00 |
| $\epsilon$                                     | 11.7 | 16.0 | 12.8 | 5.7     | 10.9 | 10.0                                   | 30.0 | 12   |
| $\mu_e$ [cm <sup>2</sup> /(Vs) <sup>-1</sup> ] | 1350 | 3900 | 8000 | 1800    | 1100 | 1000                                   | 30   | 1-4  |
| $\mu_h$ [cm <sup>2</sup> /(Vs) <sup>-1</sup> ] | 450  | 1900 | 400  | 1200    | 100  | 120                                    | 4    | 0.05 |
| $\rho$ [g/cm <sup>3</sup> ]                    | 2.33 | 5.33 | 5.32 | 3.52    | 5.85 | 5.78                                   | 7.56 | 2.30 |

- Other types of sensors:
- gas ionization chambers;
  - proportional counters;
  - scintillation sensors

# Noise - 1



noise gives rise to degradation of signal delivered by sensor → limited accuracy in information carried by such signal

noise terms directly related with detection mechanism: fluctuations in number of liberated e<sup>-</sup>h<sup>+</sup> pairs (Fano factor)

noise stochastic terms in circuit devices



noise terms resulting from electromagnetic disturbances, ground loop, ground bouncing, power supply ripple, etc.

shielding

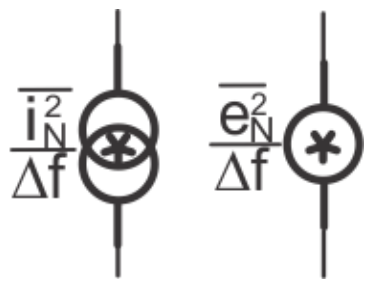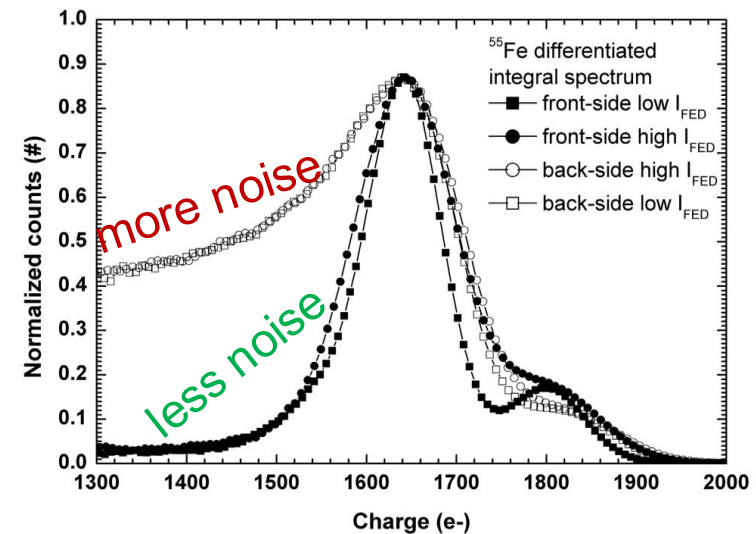

noise current and voltage sources

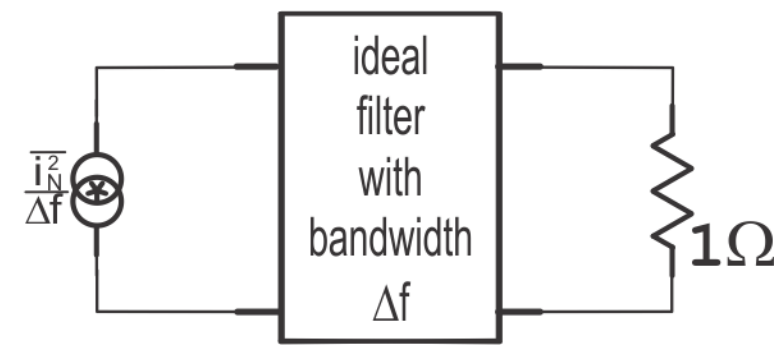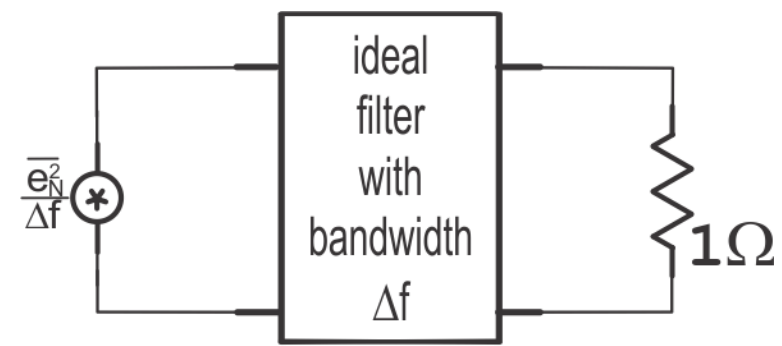meaning of both sources is average power delivered to 1Ω load in frequency interval Δf




resistor

capacitor

diode

MOSFET

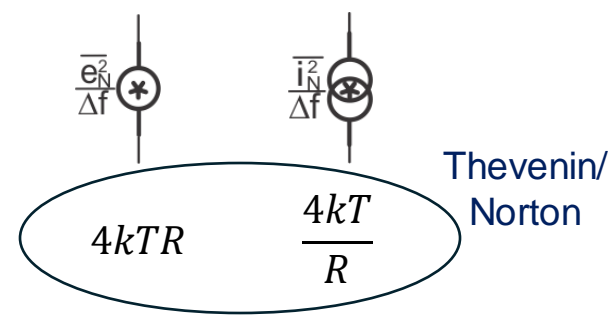


Thevenin/Norton


|     |                                      |         |
|-----|--------------------------------------|---------|
|     | $2qI_D$                              | $2qI_G$ |
| th. | $4kT \frac{0.7}{g_m}$                |         |
| 1/f | $\frac{K_f}{C_{ox}^2} \frac{1}{WLf}$ |         |

# Noise - 2

much simplified and brief analysis:

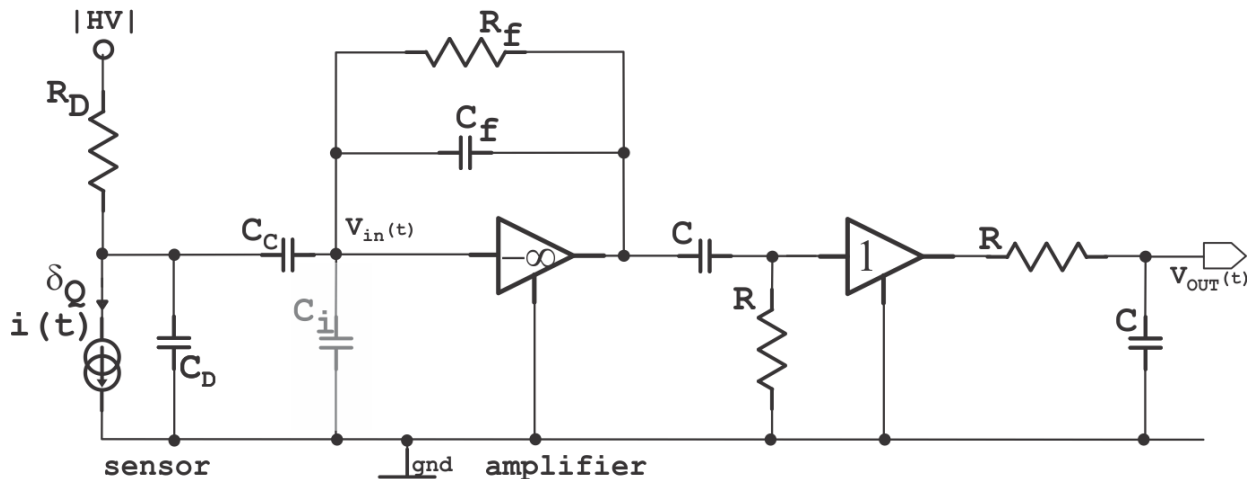

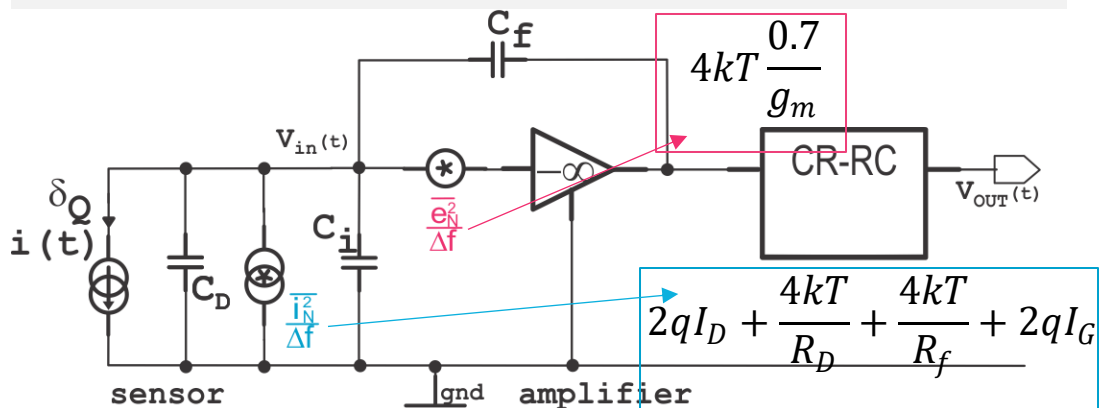- $C_C$  is large so it can be replaced by short
- $C_i$  is input capacitance of amplifier (1<sup>st</sup> transistor gate)
- $R_f, R_D$  are large, so consider as opens, but look at noise contribution!
- replace p-z by CR-RC cascade



noise power at output of integrator:

$$\text{currents} \quad \left( 2q(I_D + I_G) + 4kT \left( \frac{1}{R_D} + \frac{1}{R_f} \right) \right) \frac{1}{\omega^2 C_f^2}$$

$$\text{voltages} \quad 4kT \frac{(C_i + C_D + C_f)^2}{C_f^2} \frac{0.7}{g_m}$$

$$\text{CR-RC filter} \quad H(j\omega) = \frac{1}{1 + j\omega RC} \frac{j\omega RC}{1 + j\omega RC}$$

$$\left[ \frac{\text{power spectrum}}{\text{at output}} \right] = \left[ \frac{\text{power spectrum}}{\text{at input}} \right] |H(j\omega)|^2$$

$$|RMS\ NOISE|^2 = \int_0^\infty \left[ \frac{\text{power spectrum}}{\text{at output}} \right] df \quad \omega = 2\pi f$$

we know that peak amplitude is  $Q/C_f$ ,  
so ENC is at Room Temperature:

$$ENC = 17.36 \left[ 1.45 \frac{(C_i + C_D + C_f)^2}{g_m} \frac{1}{\tau_p} + \left\{ 40(I_D + I_G) + 2070 \left( \frac{1}{R_D} + \frac{1}{R_f} \right) \right\} \tau_p \right]^{1/2}$$

let's design detecting system so that parallel noise is negligible and knowing that  $C_f$  is small:

$$ENC = 21(C_D + C_i) \left[ \frac{1}{g_m \tau_p} \right]^{1/2}$$

so, for  $C_D$  and  $C_i$  in pF,  $g_m$  in mS and  $\tau_p$  in  $\mu s$ , for  $\tau_p=1$  and  $g_m=10$   
 $\Rightarrow ENC \approx 6e/pF$

because  $g_m \propto \sqrt{\frac{C_{ox} W I_{DS}}{L}}$

It is possible to find relation between  $C_D$  and  $C_i$  minimizing ENC



# Noise (summary) - 3



$$ENC^2 = \underbrace{A_1(C_D + C_i + C_f)^2 \frac{1}{\tau_p}}_{\text{series white noise}} + \underbrace{A_2(C_D + C_i + C_f)^2 \frac{2\ln 2}{\pi}}_{\text{1/f noise}} + \underbrace{\frac{1}{3}A_3\tau_p}_{\text{parallel noise}}$$

for triangular shaping and MOS

$$A_1 = 4kT \frac{0.7}{g_m}$$


$$A_2 = 10^{-11} - 10^{-9} V^2$$
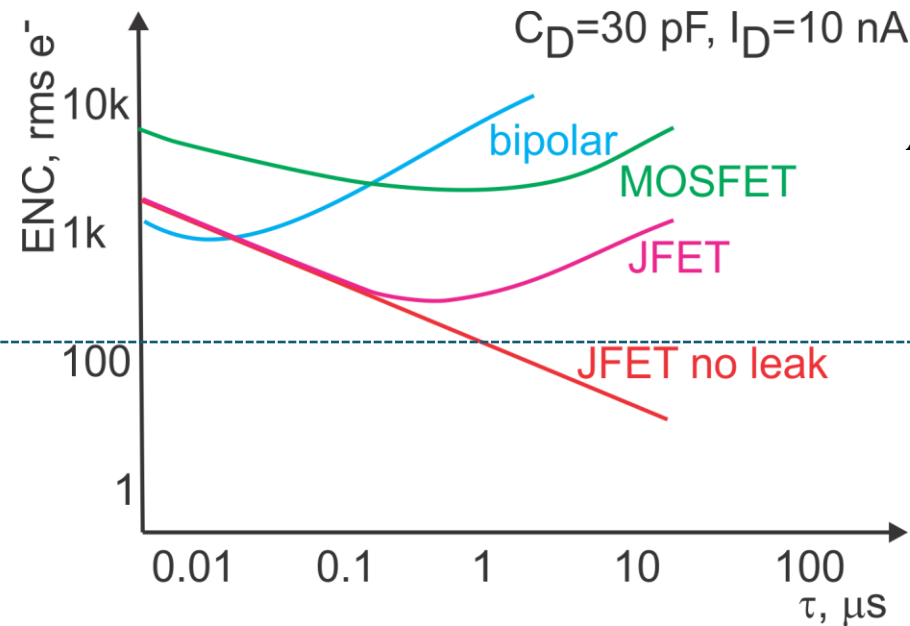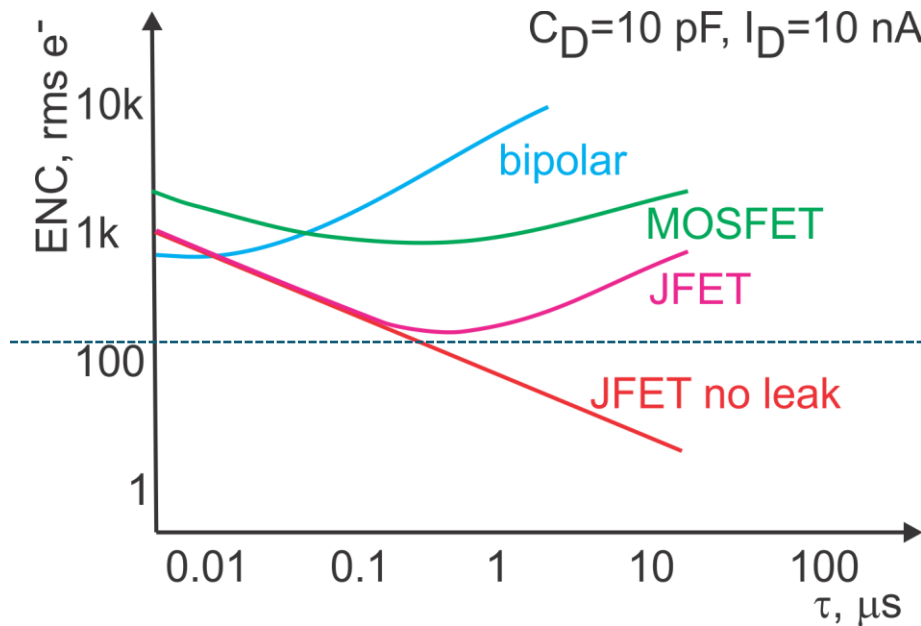
$$A_3 = 2qI_D + 4kT \left( \frac{1}{R_f} + \frac{1}{R_D} \right)$$




1/f

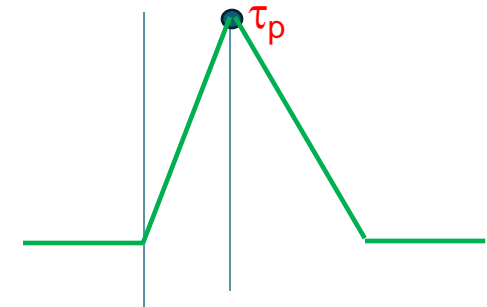- series white noise → inversely proportional to  $\tau_p$  and is important for short shaping times
- 1/f noise → independent of  $\tau_p$  and not too much can be done (except not deep in saturation and not small WL)
- parallel noise → proportional to  $\tau_p$  and is important for long shaping times





# Measurements - 1

## AMPLITUDE MEASUREMENT

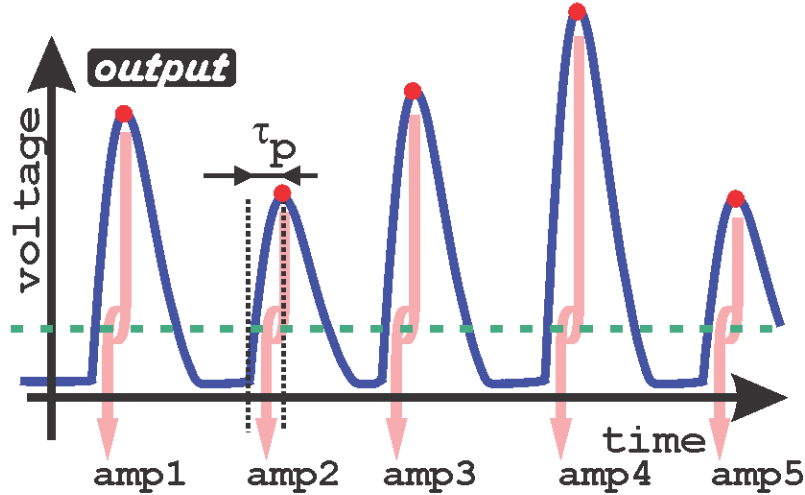

peak - detection

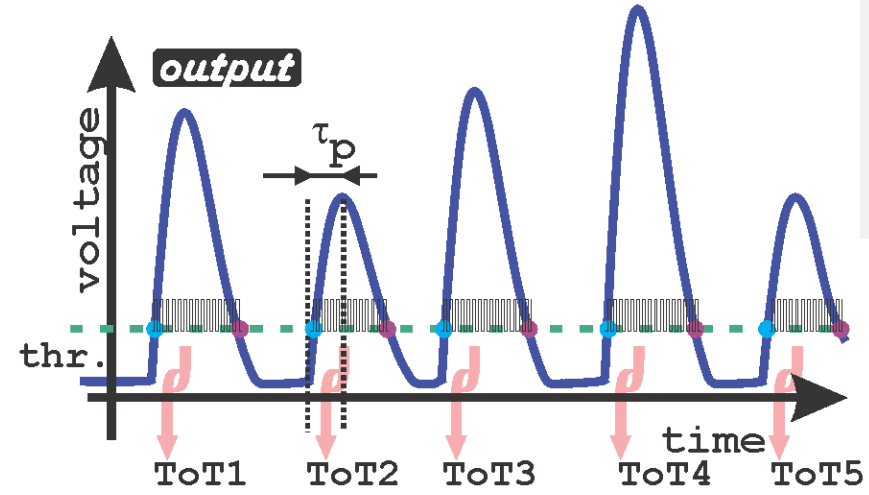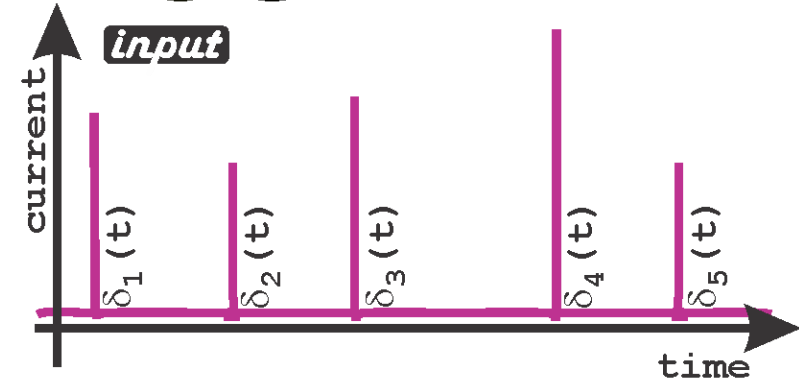amplitude measured as the maximum (minimum) excursion of a pulse above the baseline



ToT measurement

amplitude measured as time a pulse stays above a threshold


We are interested to know how:

- much charge was liberated
- proportions of charge between channels

Precision of amplitude measurement is affected by indeterministic errors (stochastic), depending on noise contained in signal  
➔ S/N

# Measurements - 2

## noise superimposes on signal

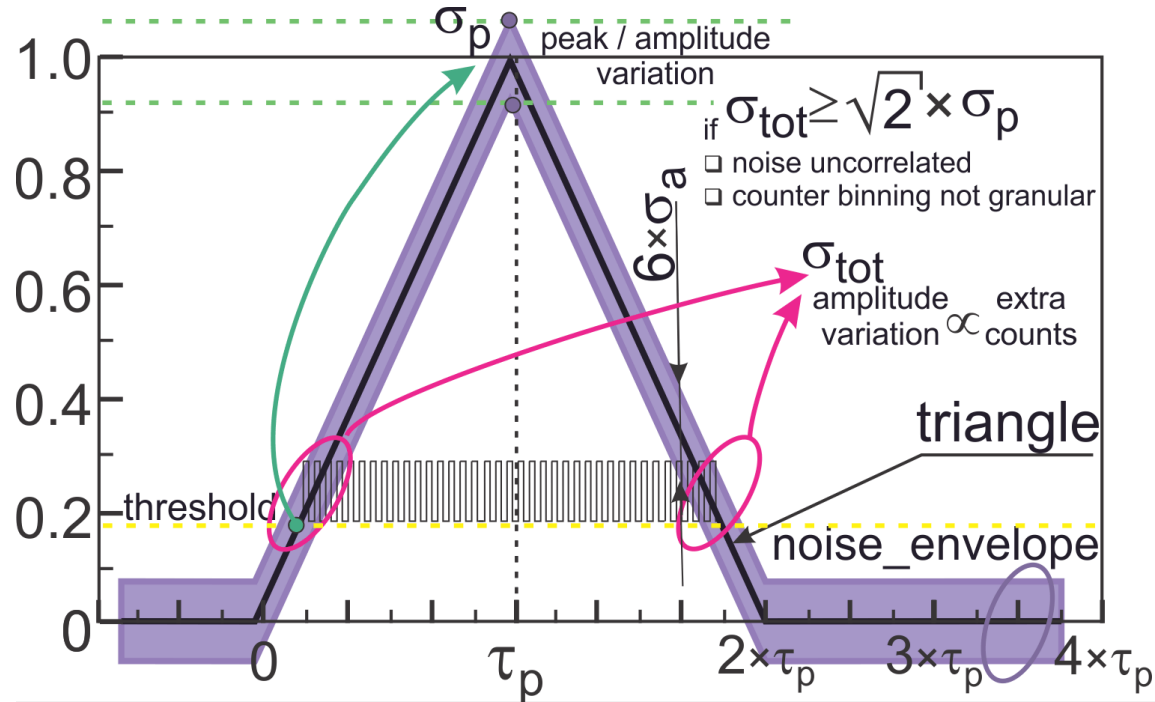


### Major sources of noise:

- electronic noise generated inside amplifiers processing signals → optimize design;
- noise generated in power supplies (most of sensors are operated in single ended configuration) → optimize system and design;
- interferences: capacitive, inductive that penetrate:
  - individually to each channel, or
  - generate common mode fluctuations → all channels 'jump' or drift;
- resulting from temperature drifts, light penetration, cross-talks, etc.
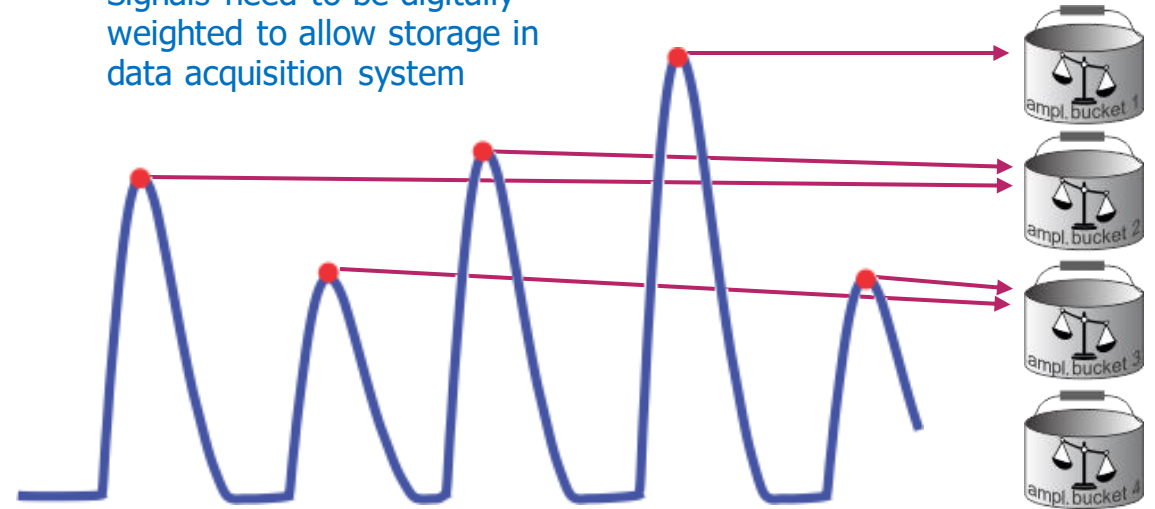
## digitization

Signals need to be digitally weighted to allow storage in data acquisition system






additional effect of binning (quantization) affects resolution (it adds noise) of amplitude measurement

use of triangular shaping is arbitrary




for practical reasons, width of noise envelope =  $6 \times \sigma$  (Gaussian distribution)
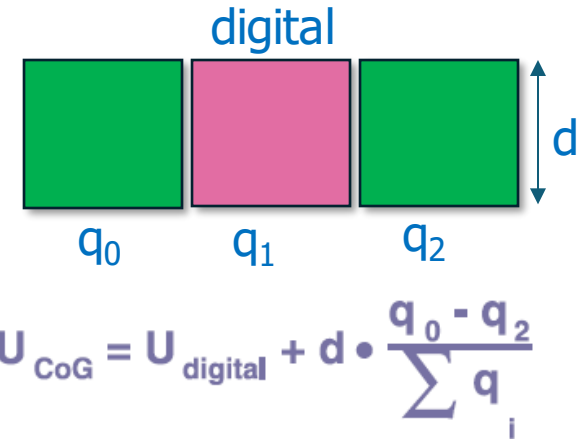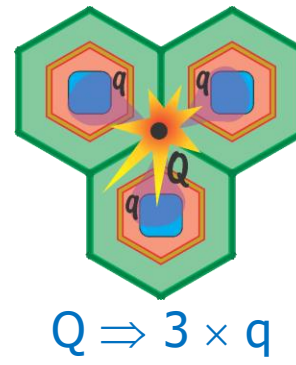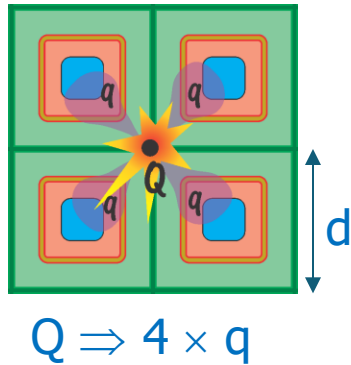
# Meas. - 3

more segmentation seems to be better but ...  
initial charge  $Q$  is shared among neighbors



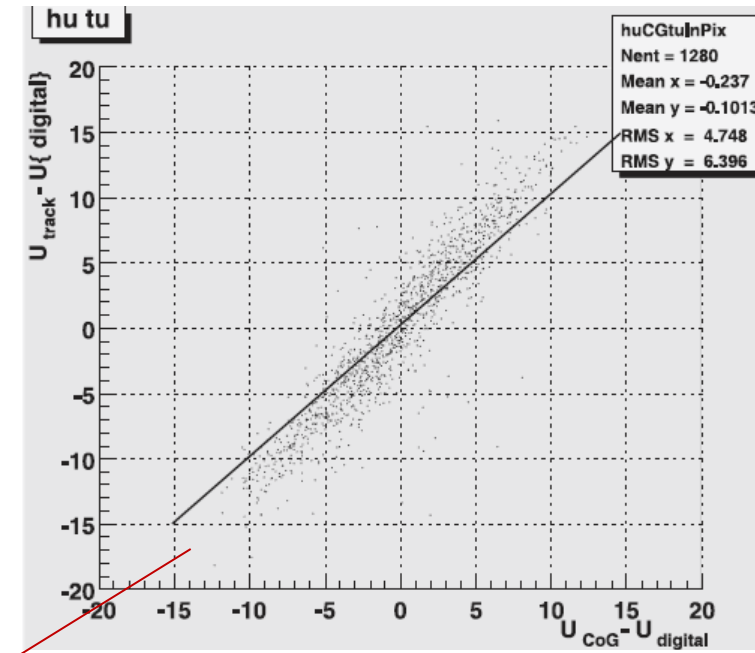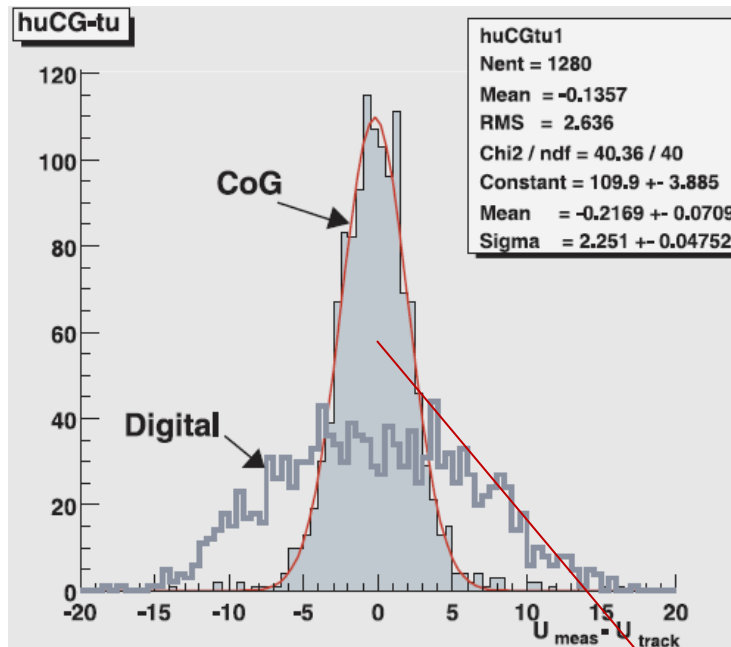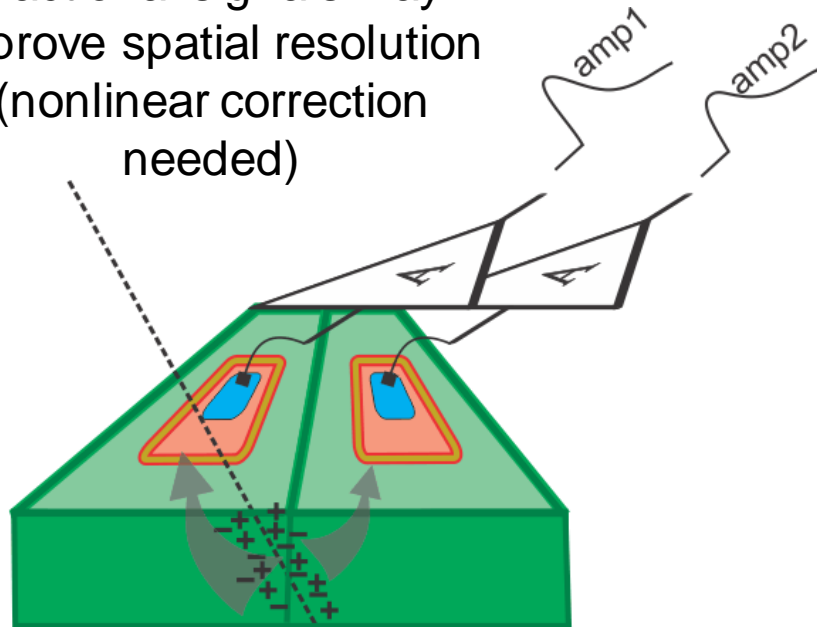measuring amplitudes of fractional signals may improve spatial resolution (nonlinear correction needed)



$\sigma_s = 2.636 \mu\text{m} \Rightarrow 2.417 \mu\text{m}$


# Meas. - 4

## TIME MEASUREMENT

importance of slope


We are interested to know how:

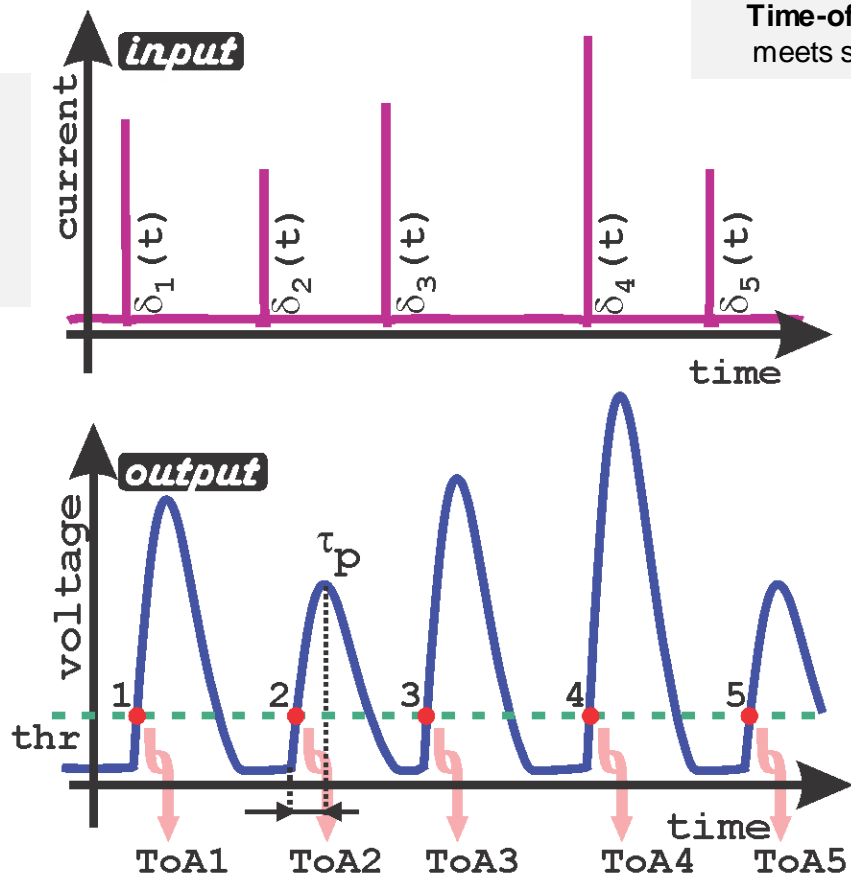- when radiation arrived to or crossed sensor



Time-of-Arrival measured as time when pulse meets some criteria, e.g., crosses a threshold

ToA measurement

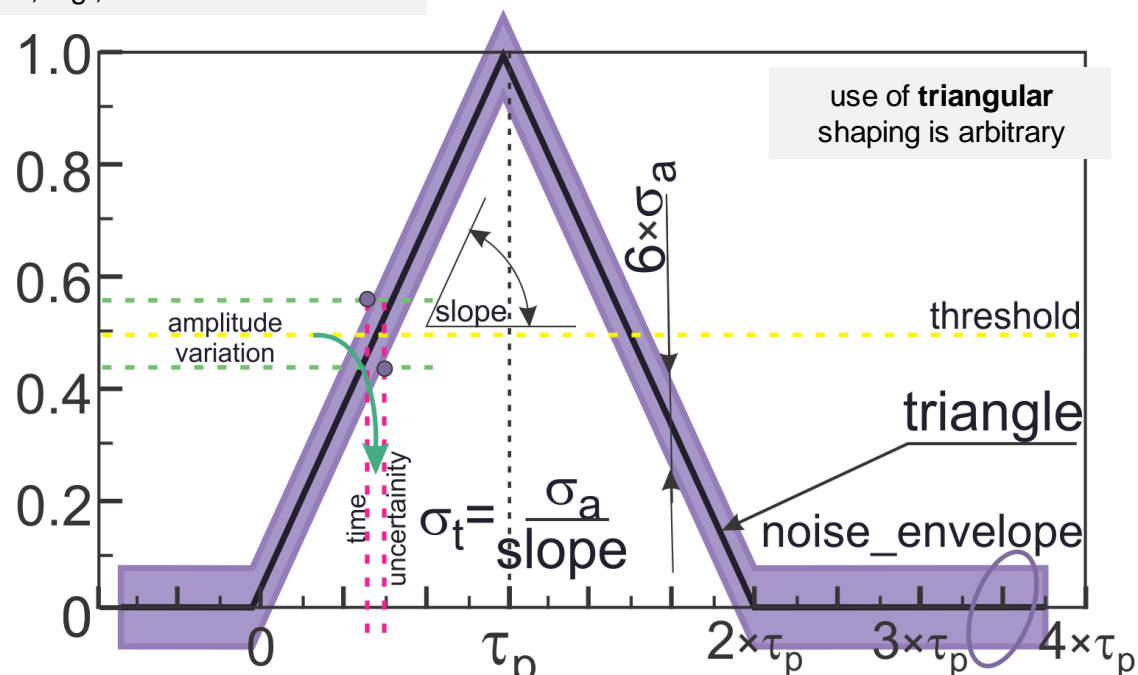

use of triangular shaping is arbitrary

Methods of measuring Time-of-Arrival:


- Leading Edge Discrimination (LED);
- Constant Fraction Discrimination (CFD);
- First Derivative Zero-Crossing (Peak Detection);
- Centroid Finding;

Essential in Time-of-Arrival:

- Change must be fast  $\rightarrow$  slope of observed signal must be maximized;
- Steeper slope  $\rightarrow$  larger bandwidth, so noise need to be watched too:

# Meas. - 5

## choice of threshold level

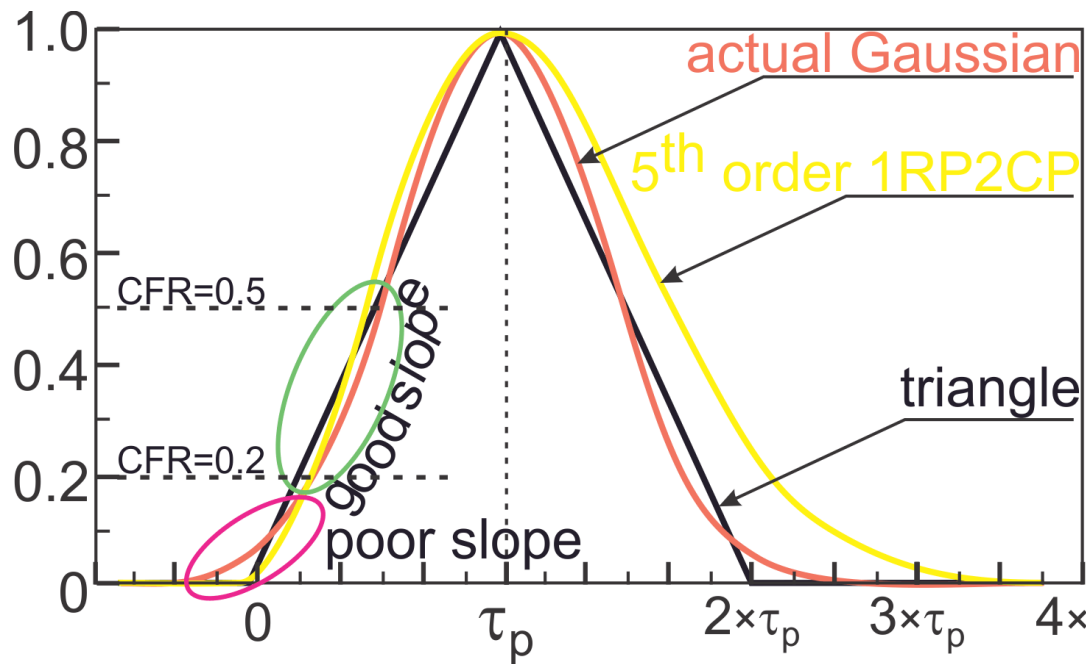


Shaping filters used in practical realizations are not triangular but approximate Gaussian form:

- Semi-Gaussian CR-RC<sup>(n)</sup> with Real Poles;
- Synthesized semi-Gaussian with pairs of Complex Conjugate Poles;
- Bessel, etc.;


Threshold needs to be set:

- where changes are fastest;
- typically, good slope  $\in (0.2, 0.5)$  of normalized amplitude  $\rightarrow$  CFR;

## precision timing in details

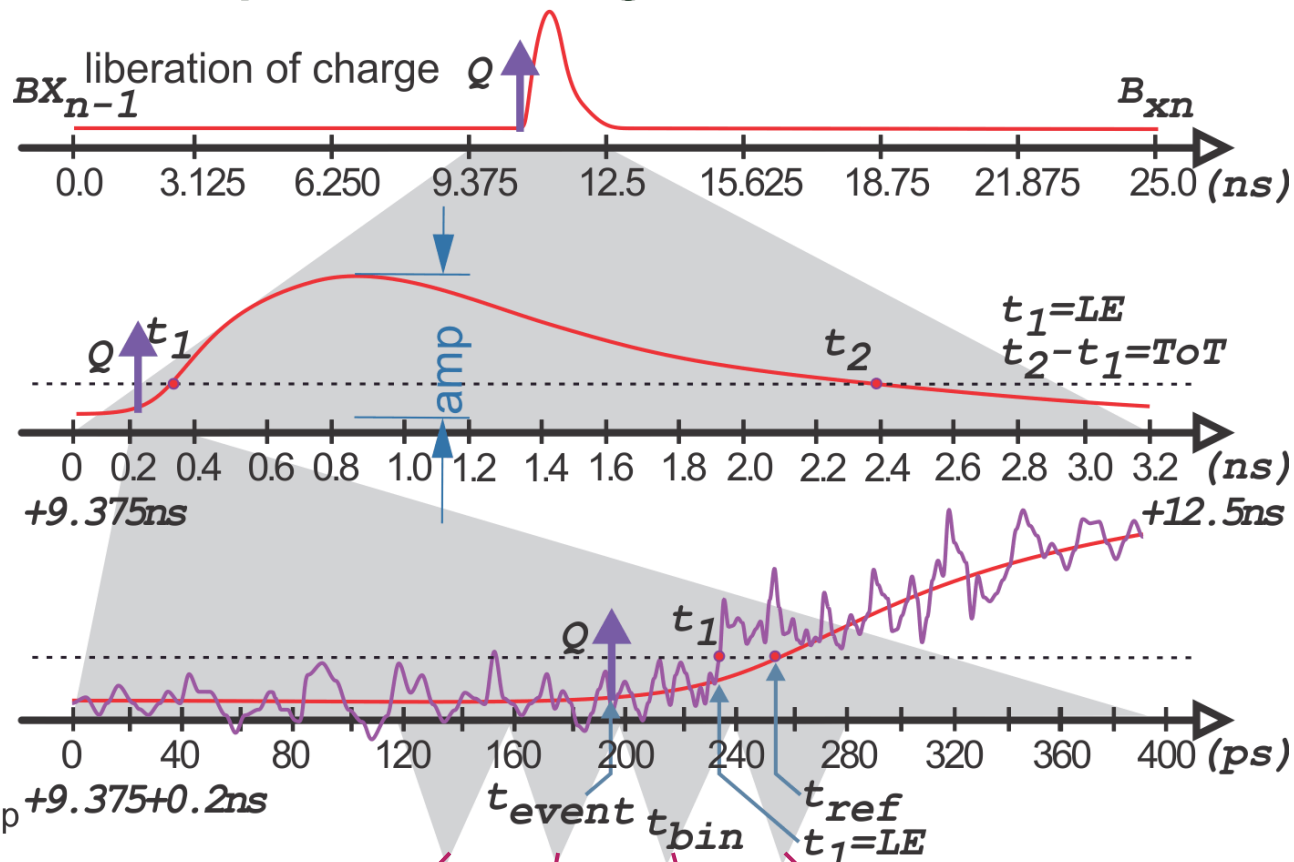

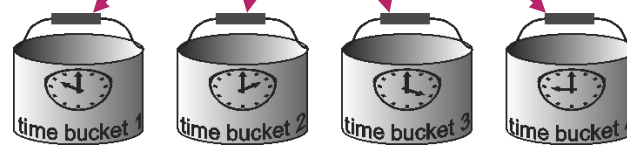binning is important as it may decide about final resolution



presented case is example

example


$$\begin{aligned}
 t_{event} &= 196ps & t_1(LE) &= 234ps & \epsilon_{t_1(LE)} &= t_{bin} - t_{ref} = 34ps \\
 t_{ref} &= 254ps & t_{bin} &= 220ps & & \\
 & & & & \text{error dominated by binning} & t_{ref} - t_1(LE) = 20ps
 \end{aligned}$$

# Meas. - 6


ToA measurement is not easy, and it requires:

- correction resulting from simultaneous amplitude measurement
- insensitive measurement to amplitude

## real discriminator

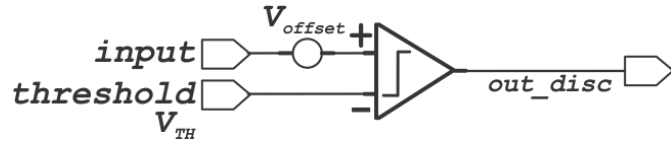

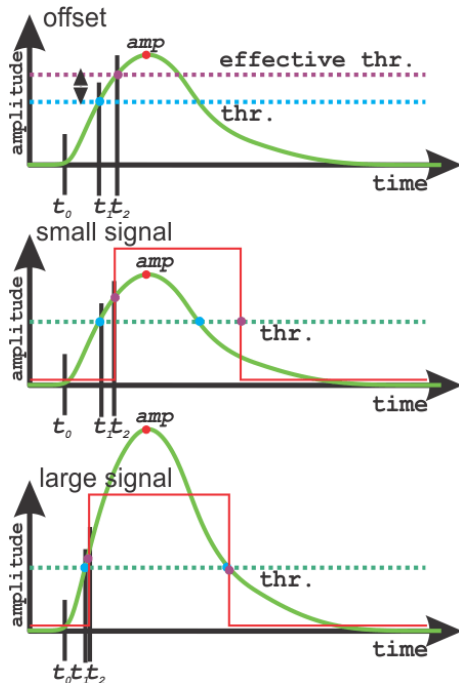
offset may be signal, radiation dose absorbed, temperature, aging, etc. dependent



delay dependent on overdrive may lead to additional errors, and may not be correctable


(overdrive insensitive discriminators)
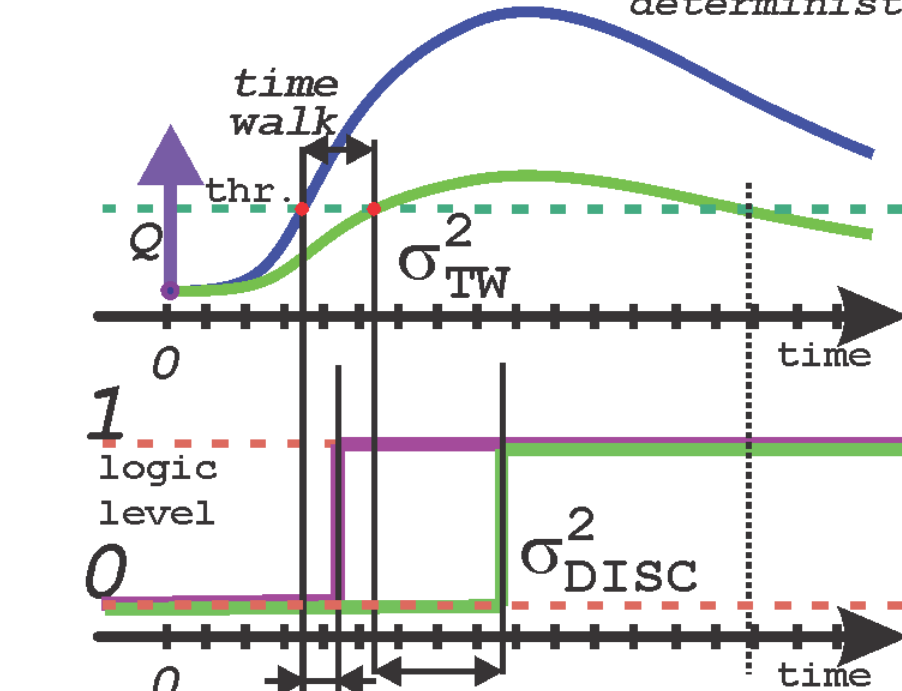
$$\sigma_{ToA} = \sqrt{\left(\alpha_f \frac{\tau_p}{S/N}\right)^2 + \underbrace{\sigma_{TW}^2 + \sigma_{DISC}^2}_{deterministic}}$$



Precision of ToA measurement is affected by errors:



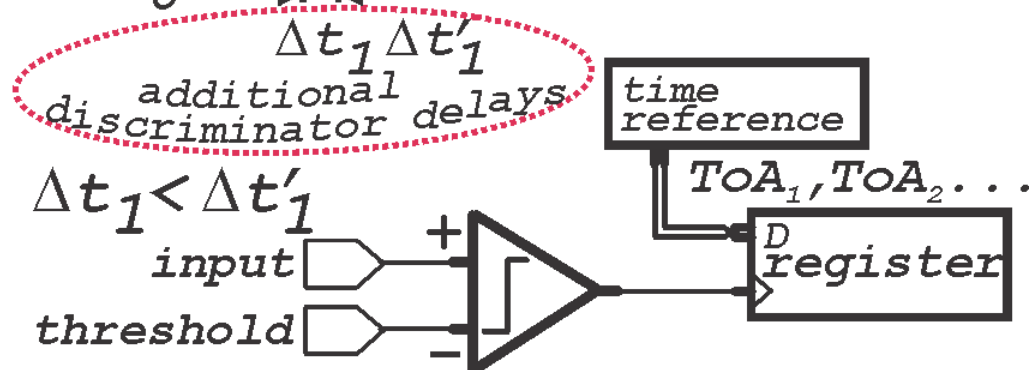
- indeterministic (stochastic), depending on noise contained in signal  $\rightarrow$  S/N and slope of a pulse ( $\alpha_f \tau_p$ )
- and deterministic:
  - $\rightarrow$  time-walk  $\sigma_{TW}$
  - $\rightarrow$  discriminator overdrive  $\sigma_{DISC}$



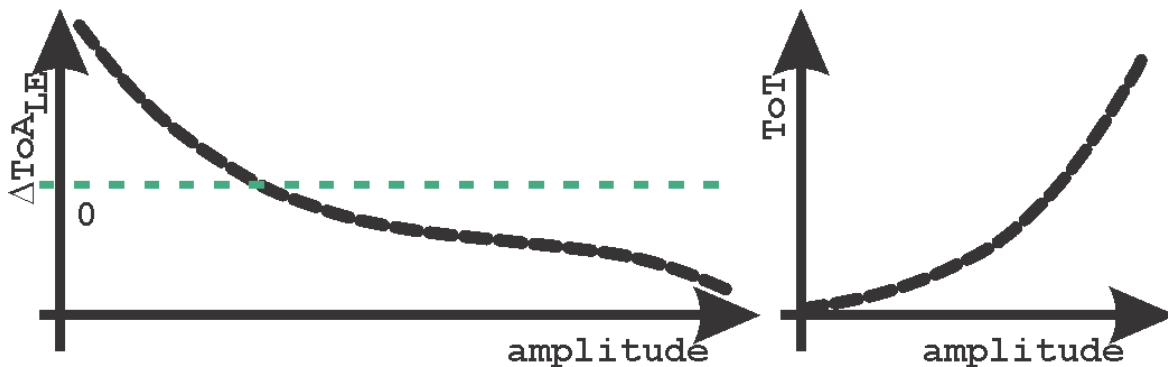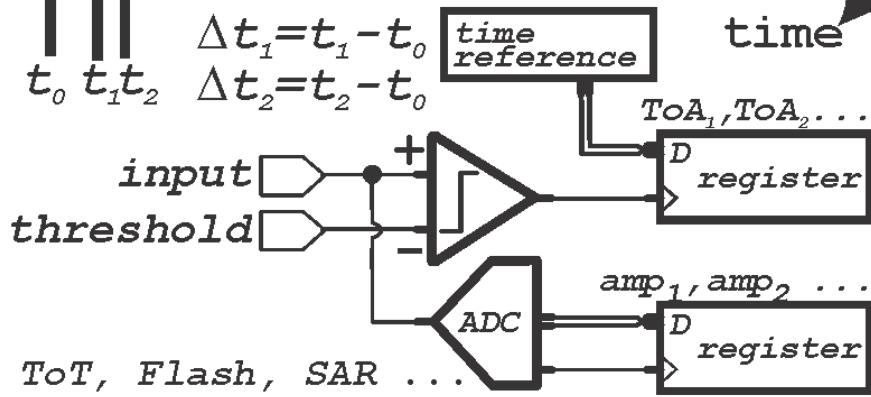
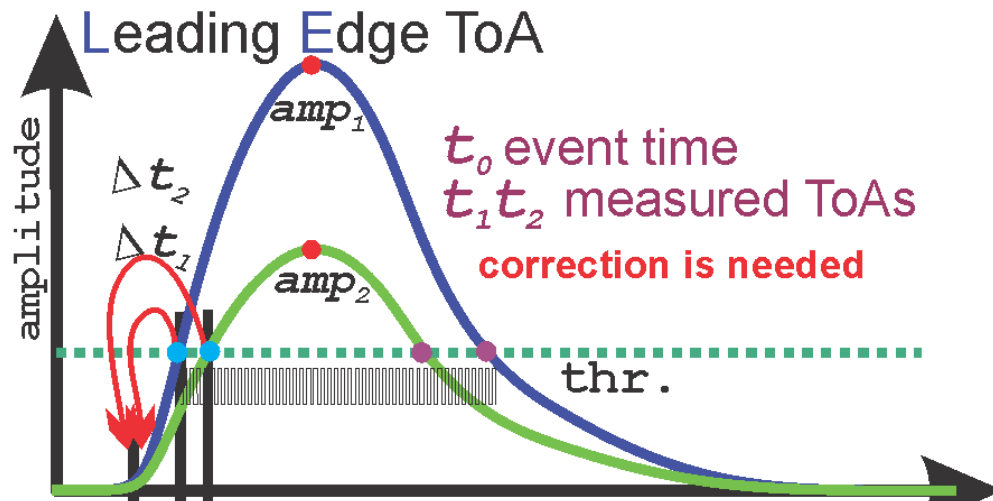
# Meas. - 7

LE is simple but requires additional steps of correction (not easy in circuits as it requires look-up tables, etc.)

$t_0$  – actual time of event  
 $t_1$  time of crossing threshold of large amplitude signal  
 $t_2$  time of crossing threshold of small amplitude signal



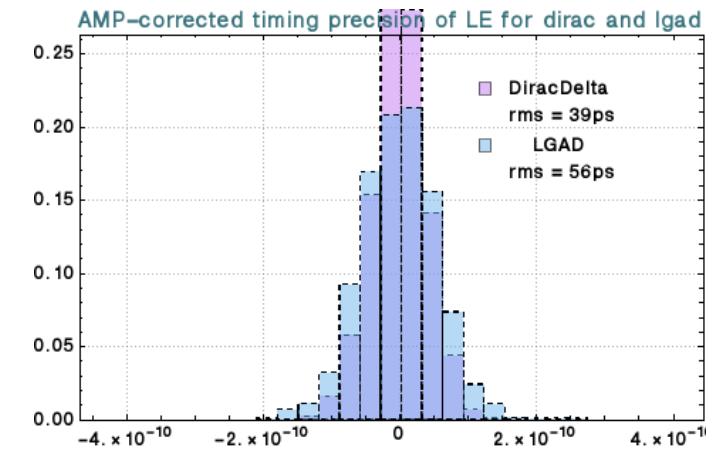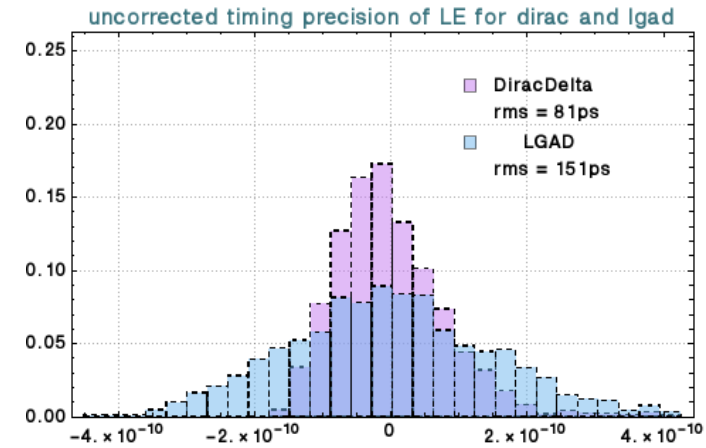Examples of ToA for SNR=30 with signals represented as  $\delta(t)$  and realistic finite time duration




3-fold improvement achieved (equivalent to CFD)




# Meas. - 8
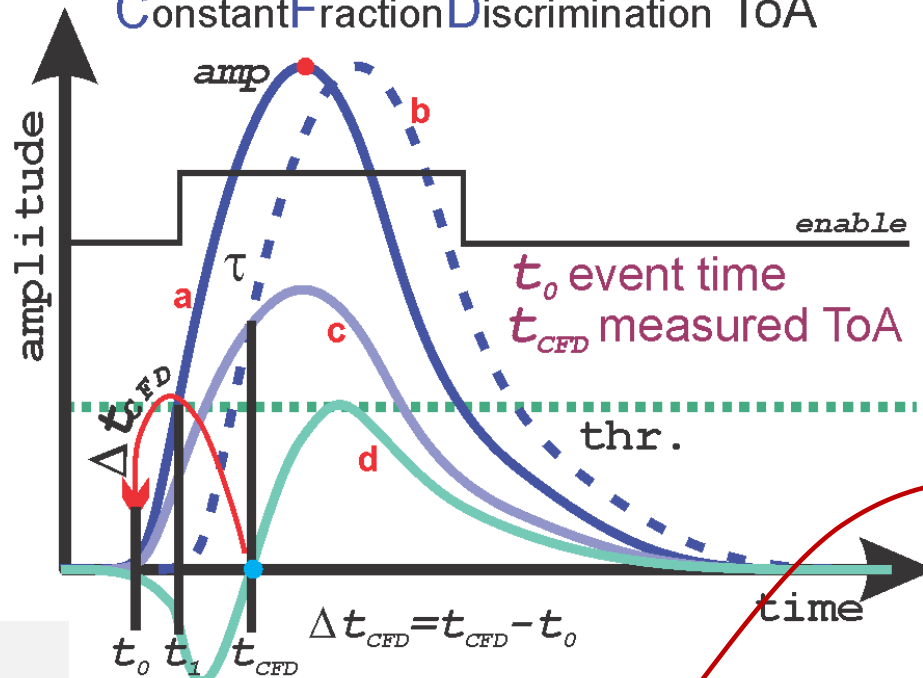
## Constant Fraction Discrimination ToA

CFD is attractive as it perform automate 'correction' of TW by circuit




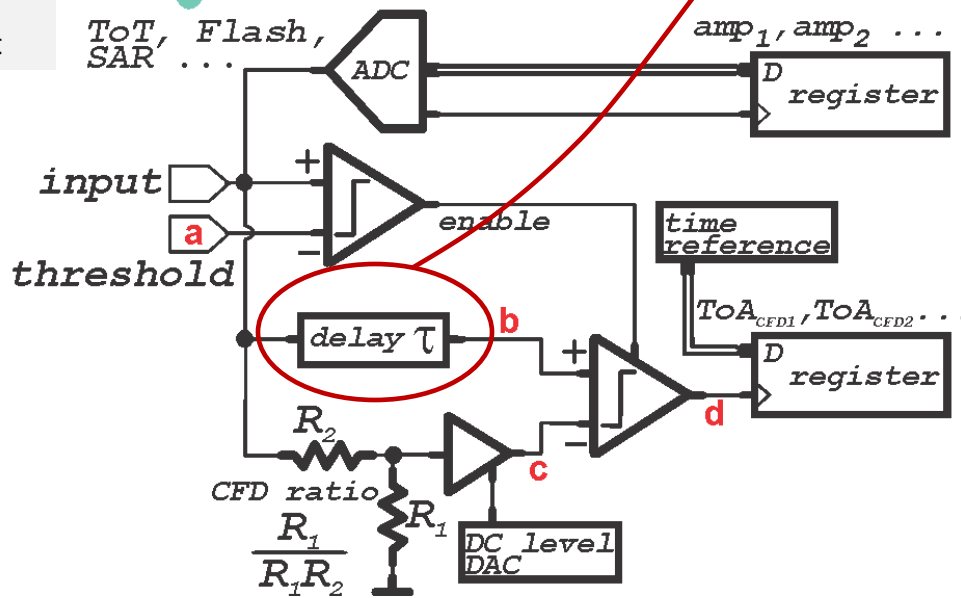
$t_0$  – actual time of event  
 $t_1$  time of crossing threshold  
 $t_{CFD}$  time yielded by measurement


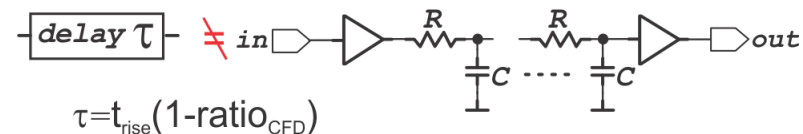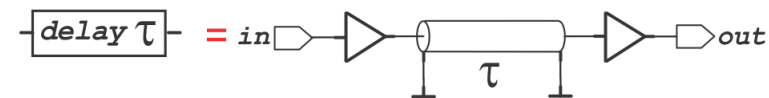
## challenges in practical CFD


Practical issues with CFD in IC:

- needed delay:  $H(s) = e^{-s\tau}$ , but practically achievable is  $H(s) \propto \frac{1}{s + \tau}$ ;
- lack of actual delay causes errors in „zero-crossing” position measurements when waveform shape changes due to:
  - amplitude dependence
  - varied charge collection timing




solution could be discrete time analog delay line:

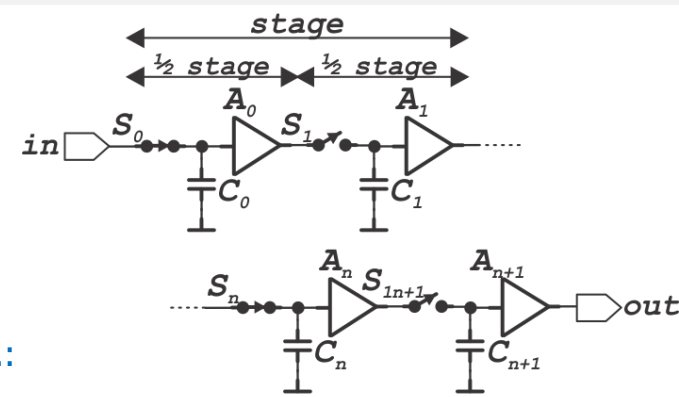- shifts processing in discrete analog domain;





ex.:

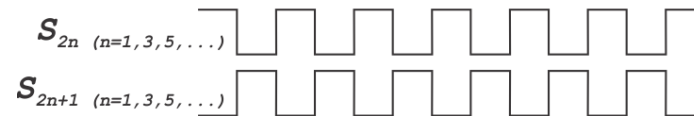

# Meas. - 9
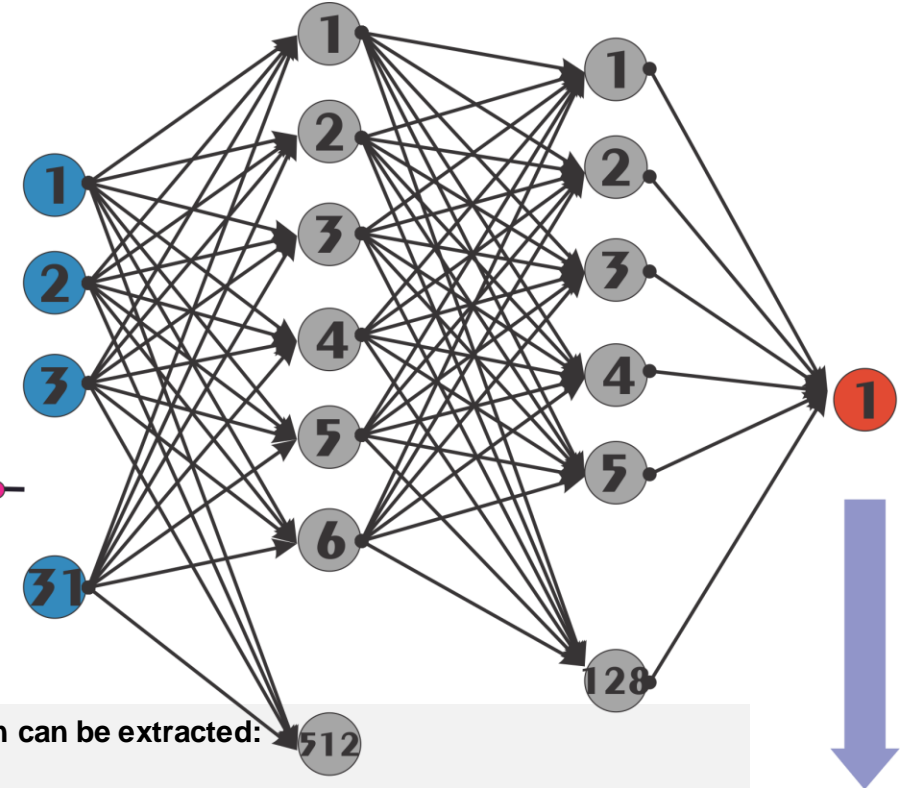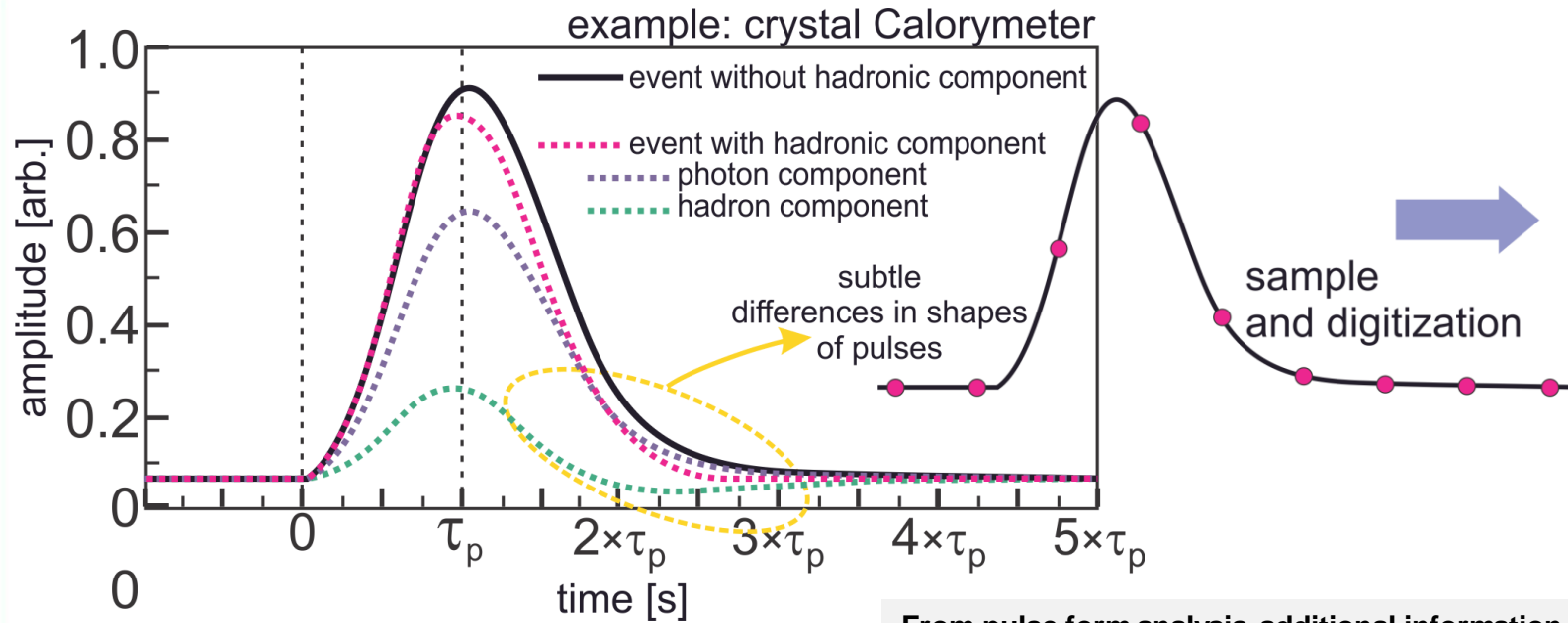
## PULSE SHAPE ANALYSIS

We are interested to know what type of particle interacted with sensor



### Forms of pulses depend on:

- how charge liberation occurs:
  - electromagnetic shower (photon production);
  - hadronic shower (secondary particles);
  - photoelectric effect vs. linear energy transfer
- how liberated charge is collected
  - drift in E field;
  - diffusion

### From pulse form analysis additional information can be extracted:

- particle trajectory (Time Projection Chamber);
- total energy deposited;
- type of interacting particles;
- composition of events;


### Ex. In Belle II (SuperKEKB e<sup>+</sup>e<sup>-</sup>):

- pulse shape analysis is used to distinguish electromagnetically and hadronically interacting particles within CsI(Tl) electromagnetic calorimeter;
- pulse shapes from particle-dependent scintillation response are analyzed with multi-template offline fit to measure fraction of scintillation emission produced by hadrons;
- particularly attractive are Artificial Neuron Network (ANN) techniques.

Energy deposited  
Hadron Intensity






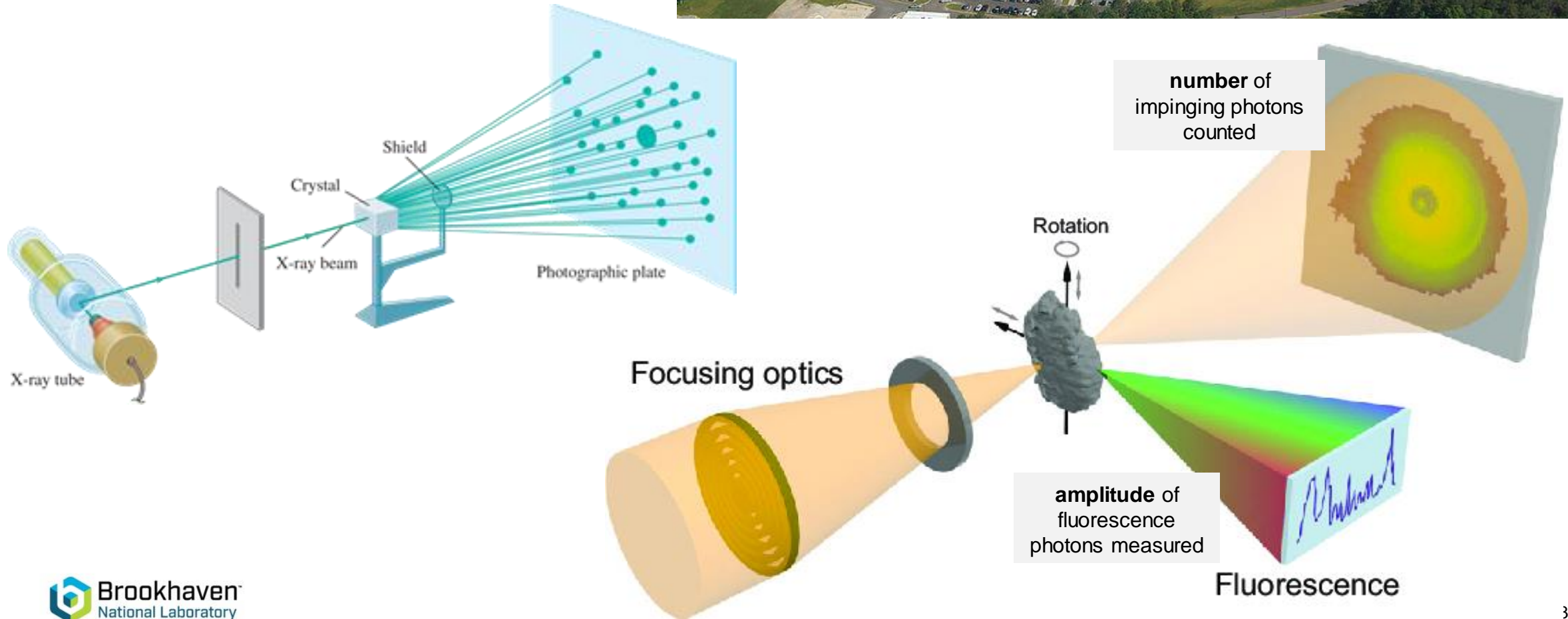
# Meas. - 10

from simple diffraction imaging to imaging using synchrotron radiation



# Meas. - 11



## COUNTING

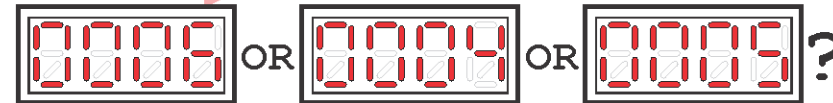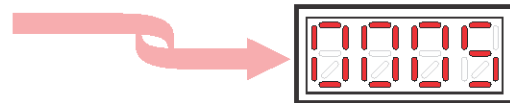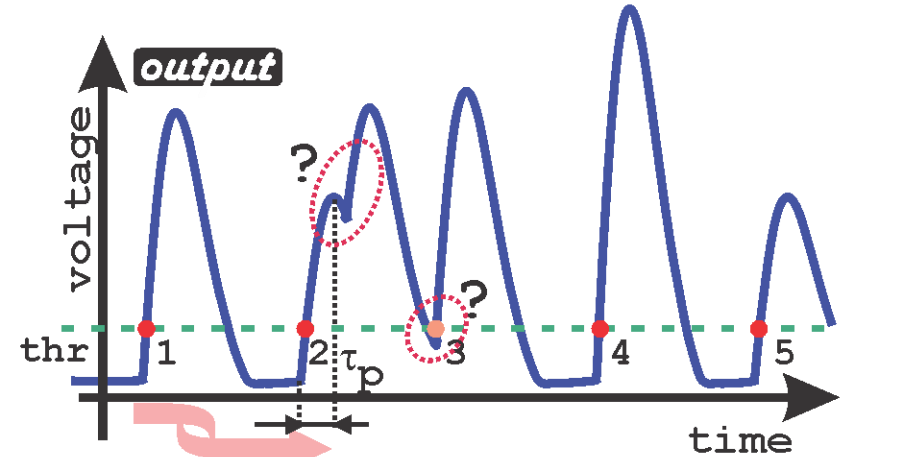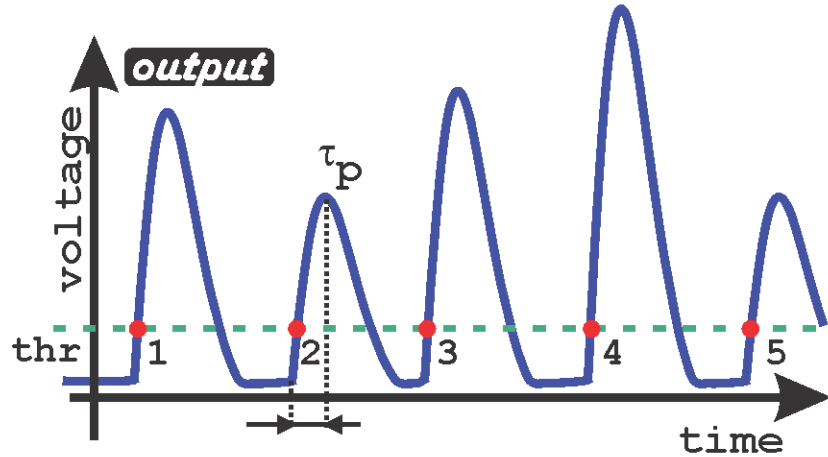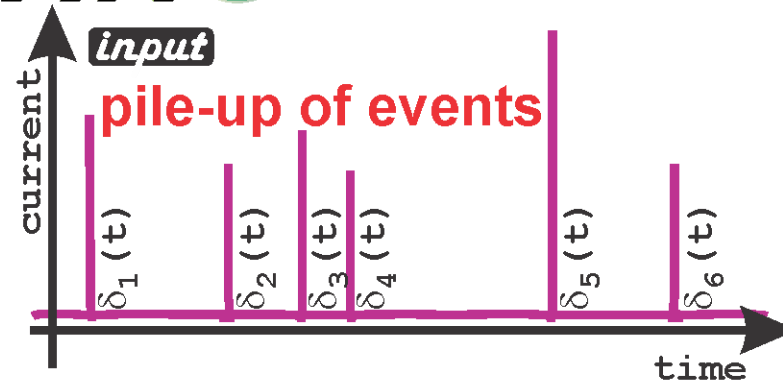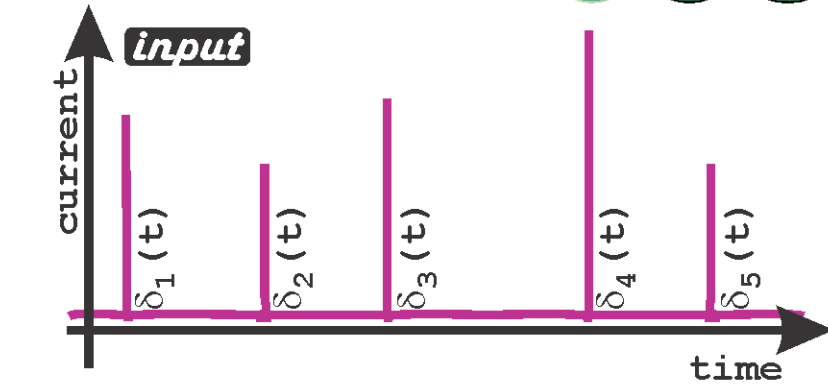




# Meas. - 12
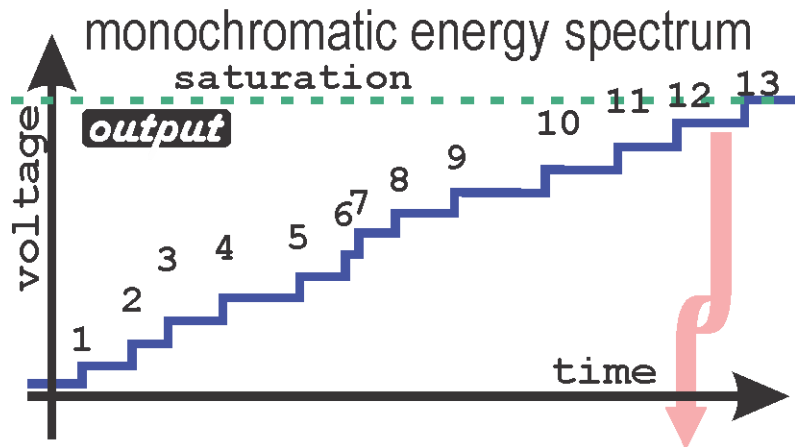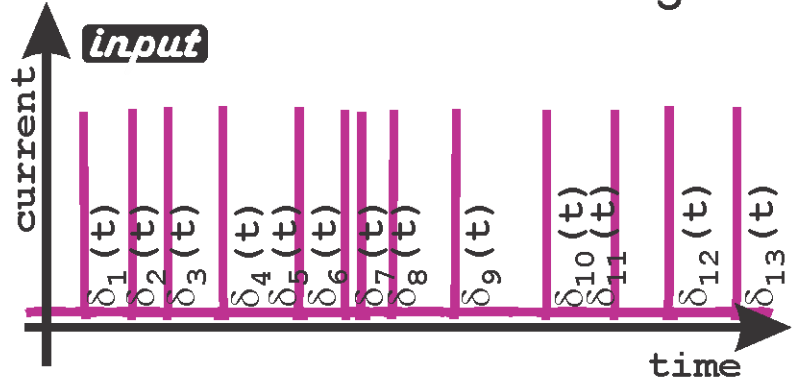
## INTEGRATING

event rate is too high for handling individual pulses



low noise  $\Rightarrow$

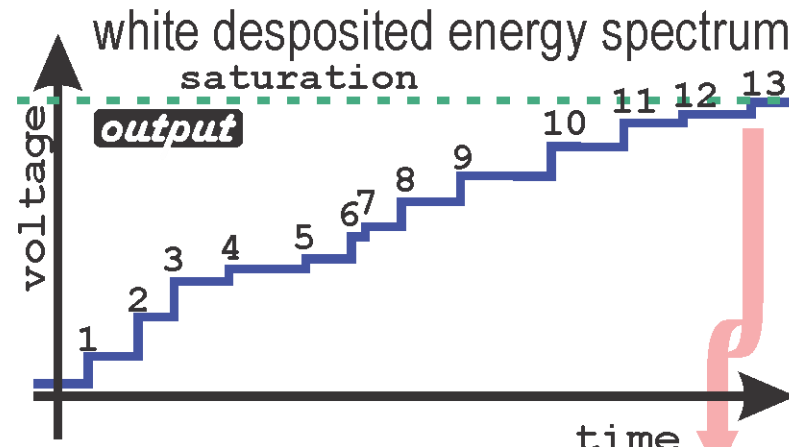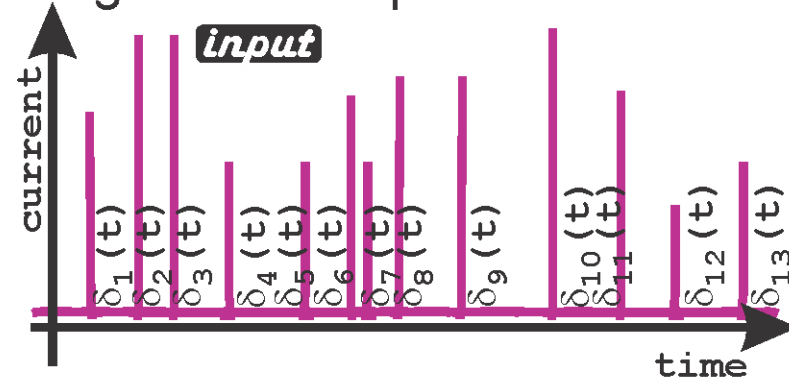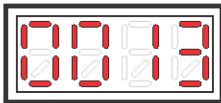

$$V_{\text{OUT}} = \sum_{x=1}^{13} C_f \int \delta_x(t) dt$$

# Useful Literature Items

old but spring-like

International Atomic Energy Agency:

- “Selected Topics in Nuclear Electronics”, IAEA-TECDOC-363, Vienna 1986
- “Nuclear Electronics Laboratory Manual”, IAEA-TECDOC-530, Vienna 1989

V. Radeka, “Optimum Signal-Processing for Pulse-Amplitude Spectrometry in the Presence of High-Rate Effects and Noise, in IEEE Transactions on Nuclear Science, vol. 15, no. 3, pp. 455-470, June 1968

V. Radeka, “State of the Art of Low Noise amplifiers for Semiconductor Radiation Detectors”, BNL-222986-2022-COPA, 1968

E. Nygard, et al. “CMOS Low Noise Amplifier for Microstrip Readout Design and Results” CERN-PPE/90-142, 1990

more recent

W.E. Cleland, E.G. Stern, “Signal Processing considerations for Liquid Ionization Calorimeters in a High-Rate Environment, Nucl. Instr. and Meth. A 338 (1994)

V. Radeka, “Signal Processing for Particle Detectors” In: Fabjan, C., Schopper, H. (eds) Particle Physics Reference Library. Springer, Cham. 2020

A. Rivetti, “MOS: Front-End Electronics for Radiation Sensors (Devices, Circuits, and Systems)” CRC Press 2015

# Summary

Application Specific Integrated Circuits with sensors form semiconductor eyes to detect radiation

- application {
- They allow measurements of numerous features of incident radiation:
  - Impact position (direction)
  - Energy and type
  - Intensity
  - Time of arrival
  - Spatiotemporal correlations, etc.
  - Etc.

Readout ASICs are large scale, mixed-mode... data generating circuits machines, designed with CAD/EDA tools

- R&D {
- They are candidates for:
  - AI/ML processing reducing raw data and extracting higher-order information
  - 3D-Integration for increased granularity and more transistors/channel

Careful optimization of Front-End amplification stages is needed to perform measurements accurately and allow further processing in digital