

Shunt-LDO Regulator

RD53B Features

23-January-2020


Michael Karagounis

Talk Outline


- changes and improvements of RD53B with respect to RD53A SLDO version
- focus on user perspective and expected regulator behavior
 - limited information on implementation details
- modifications to core design
 - minor issues like layout and connectivity
- protection features
 - overvoltage
 - overload
- new power mode

Design Concept

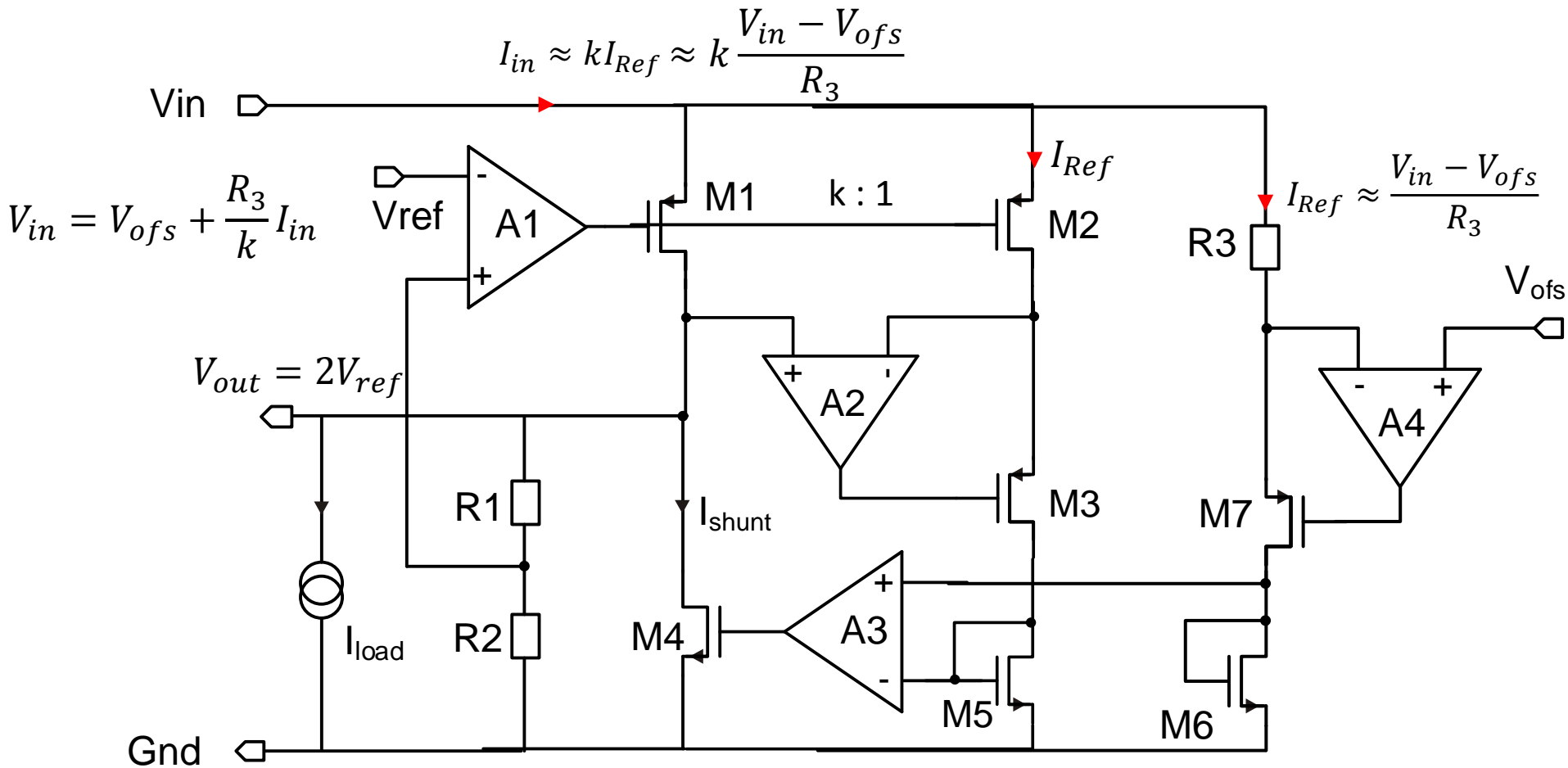
- The Shunt-LDO regulator combines the functionality of an LDO voltage regulator with the capability of a shunt regulator to drain a constant current
- Two control loops: 1) constant output voltage 2) constant current flow through the regulator



V/I Characteristic

 

 
$$V_{in} = V_{ofs} + \frac{R_3}{k} I_{in}$$




Modifications to Core Regulator Design

- reference resistor R3 defining the input impedance is only available as external component
 - integrated resistors show too large temperature and production variations
- common VDD_SHUNT pad for analog and digital regulator
 - regulators cannot be configured independent between Shunt/LDO mode
- Vofs terminal connected to biasing circuit off-chip
 - two additional pads Vofs_IN and Vofs_OUT available
 - Can be used for common Vofs voltage on module level to improve current distribution

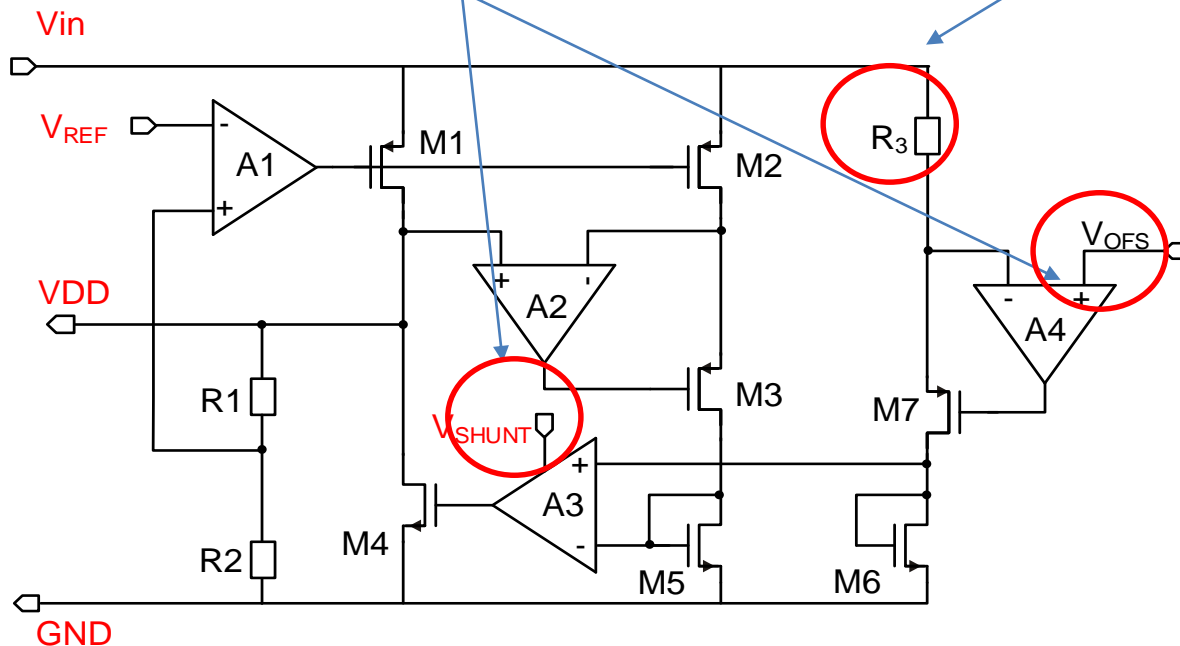


Modifications to Core Regulator Design

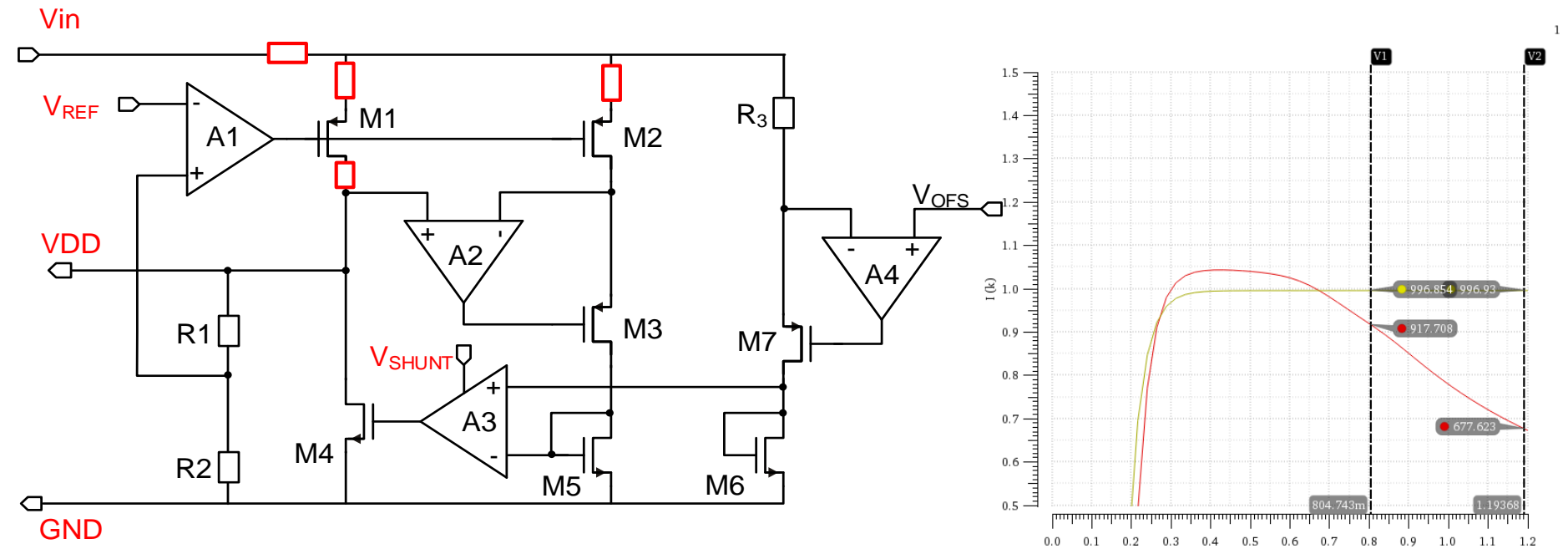- new layout of the power transistors to reduce influence of parasitic resistors
 - measured input impedance (V_{in} slope) was larger than expected
 - parasitic resistors influenced M1/M2 current mirror ratio




Improvements to Startup Behavior


- RD53A used two independent bandgaps for the digital and analog regulator
 - different startup timing of the digital and analog regulator
- RD53B uses single bandgap for both the digital and analog regulator
 - regulators should startup at the same time
- Startup is supported by an newly introduced startup circuit
 - Vofs is drawn to high value close to Vin to increase regulator impedance
 - injection of additional current into the Rofs resistor
 - switch-off current injection after start-up

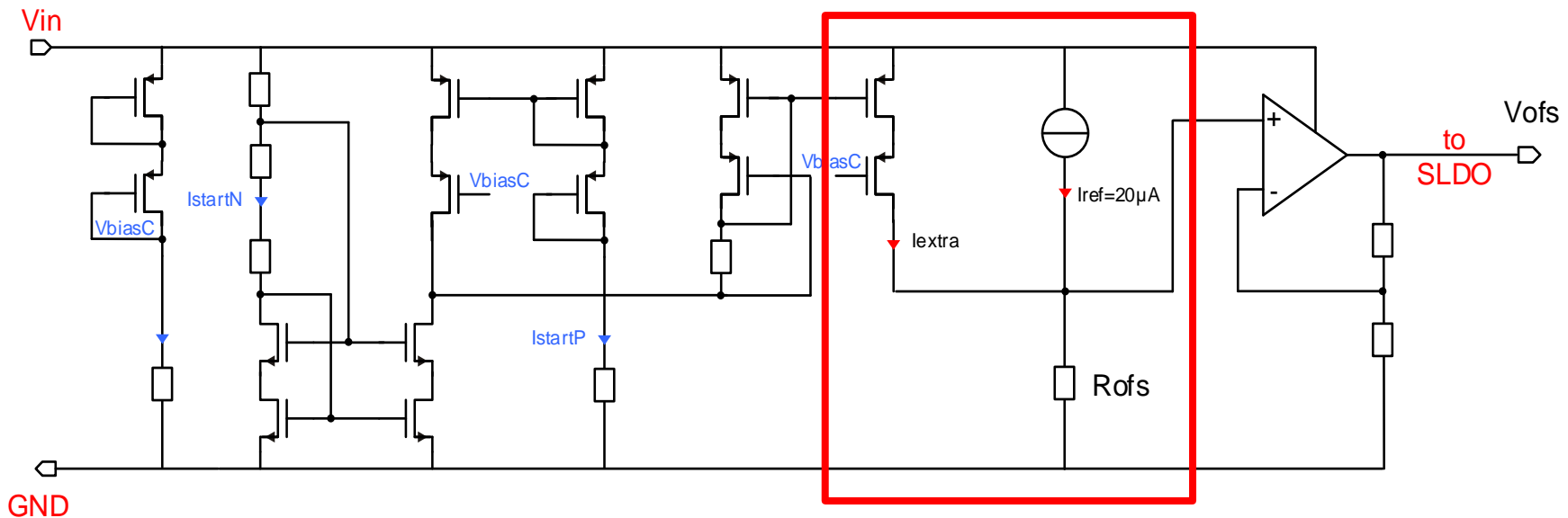

Simulation at 1A/1s start-up ramp


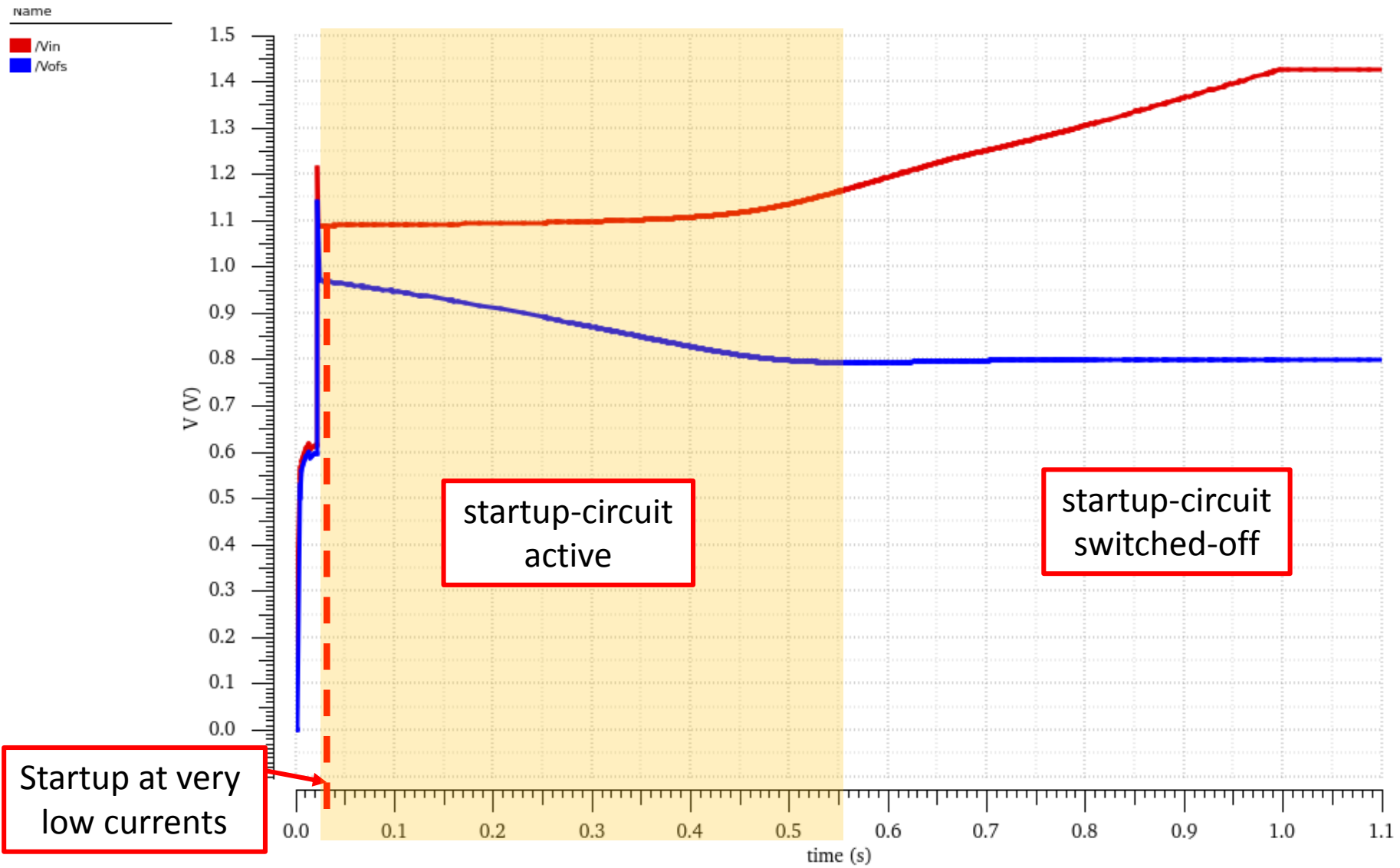


Protection Feature: Overload Protection

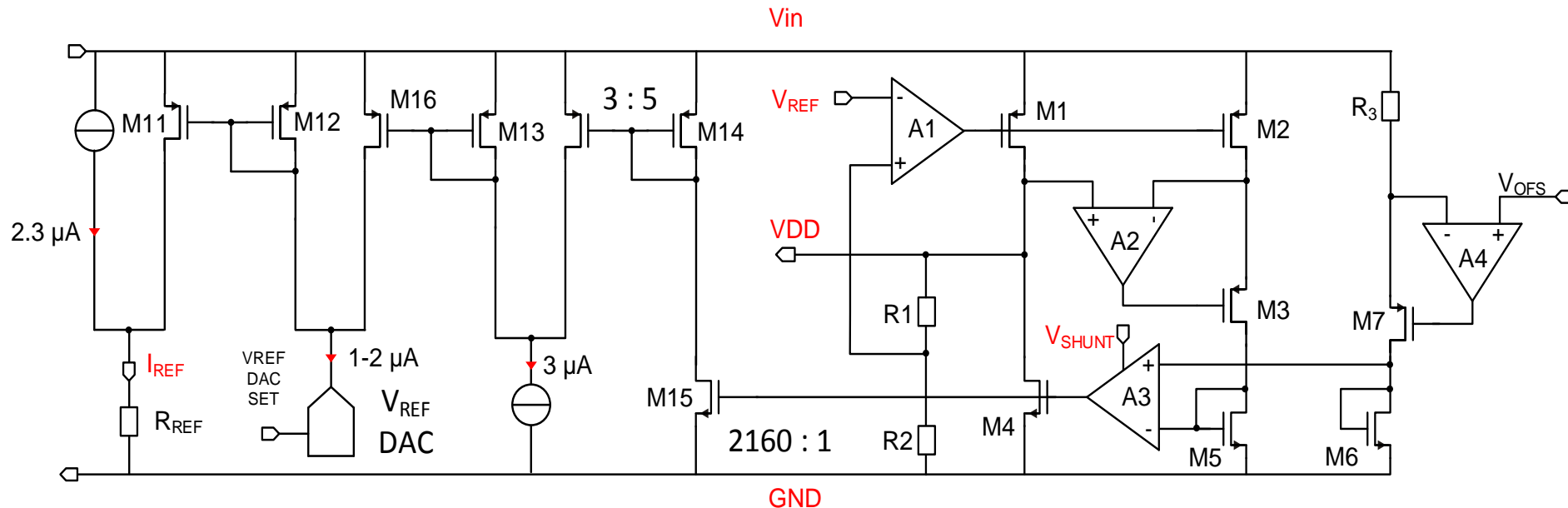


- With RD53A overload currents lead to collapse of regulator input voltage
 - This lead to overvoltages at other modules in the serial chain
- RD53B protects against overloads which are considered as undershunt current scenarios
 - high load current reduces shunt current
- In undershunt current case V_{out} is reduced
 - V_{out} is lowered by lowering V_{ref}
- Activation Threshold $I_{shunt} < 10 \text{ mA}$
- V_{out} minimum value 700mV \rightarrow V_{ref} minimum value 350 mV

  
Measurement of Overload/Undershoot Protection



 Protection Feature: Overvoltage Protection Voltage Clamp




 - voltage clamp implemented as shunt regulator
 - operated in parallel to SLDO
- takes all excess current in case $V_{in} \Rightarrow 2V$
- limits the voltage to 2V
- can absorb up to 2A additional current per chip
- OVP threshold defined by untrimmed bandgap
 - voltage limit can vary +/- 5%




Low Power Mode

- during installation the detector will be operated without active cooling
 - to test connectivity
- detector operation mode at lower power consumption required
- SLDO has to reach the nominal operating point $V_{in}=1.4V$ at lower input current
- configurable offset-voltage V_{ofs} required
 - low V_{ofs} for high power mode
 - high V_{ofs} for low power mode
- switch introduce to enable/disable additional resistor in V_{ofs} generation circuit
- switch is controlled by rectified AC signal

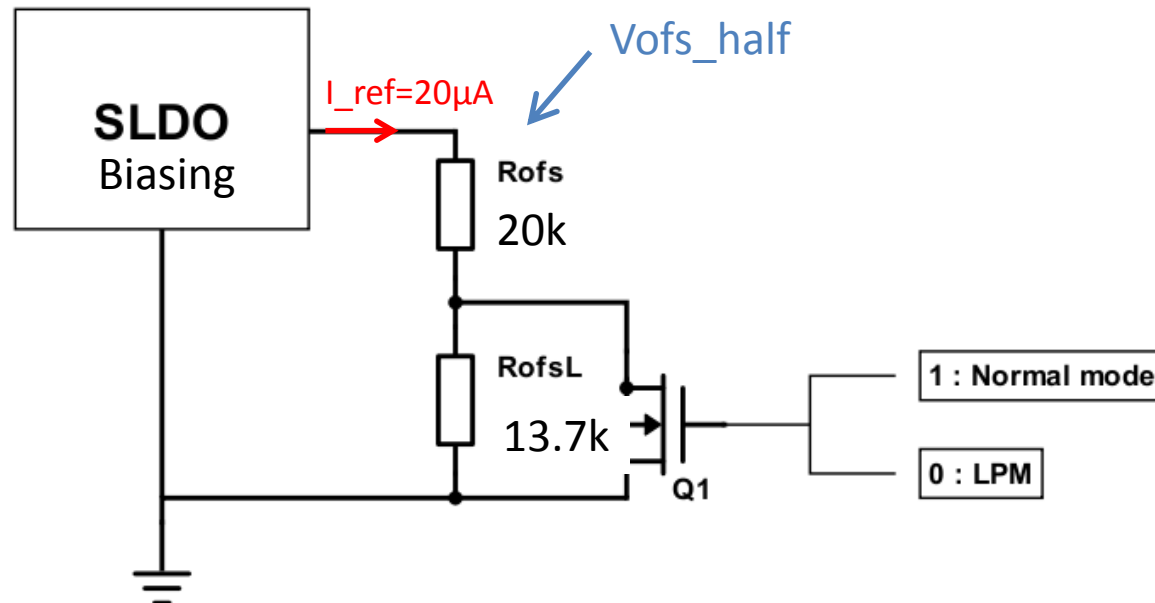


Rectification Circuit and Low Power Mode Interface

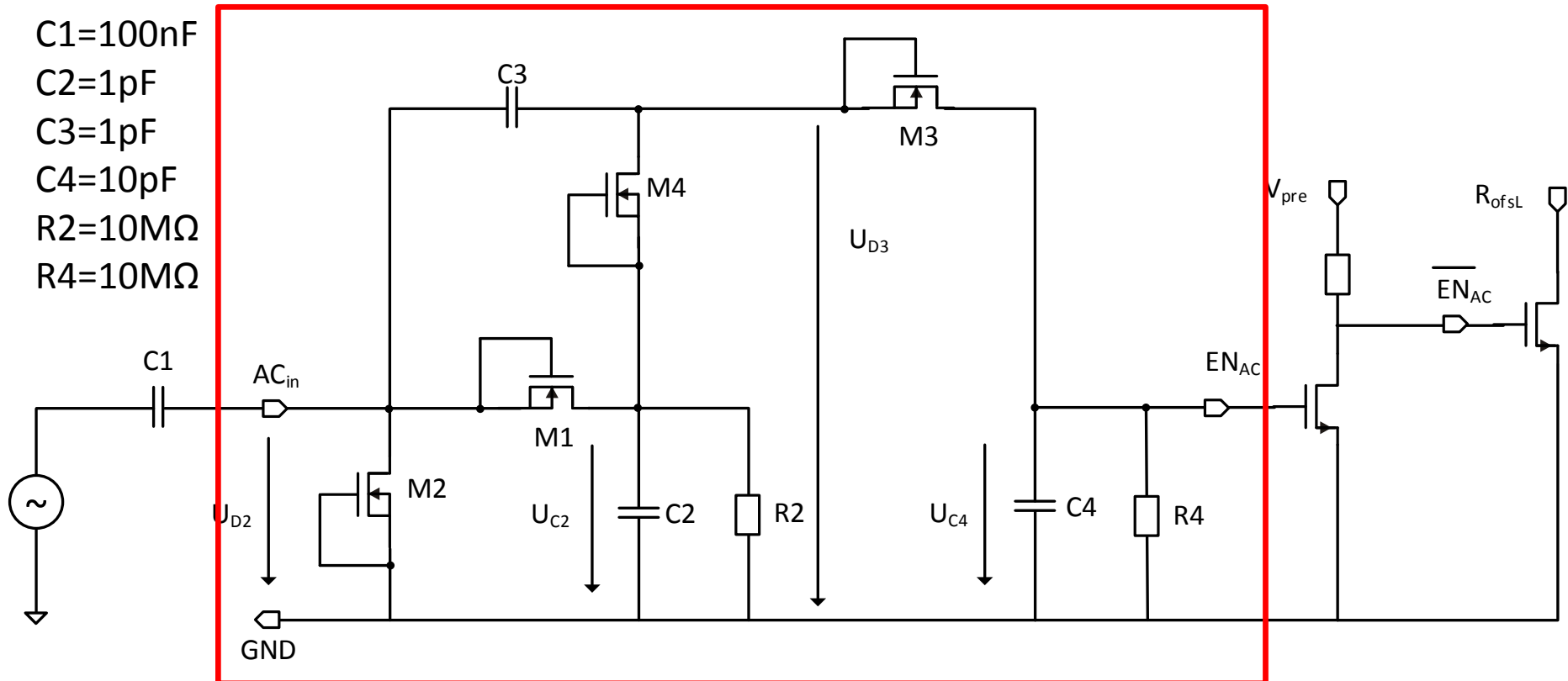$C1=100\text{nF}$
 $C2=1\text{pF}$
 $C3=1\text{pF}$
 $C4=10\text{pF}$
 $R2=10\text{M}\Omega$
 $R4=10\text{M}\Omega$



- rectification circuit with 2x multiplication
- AC signal is inverted and applied to a transistor in parallel two one of the Rofs resistors
 - Inverter is supply by V_{pre} using a resistor instead of PMOS to avoid SEU issues

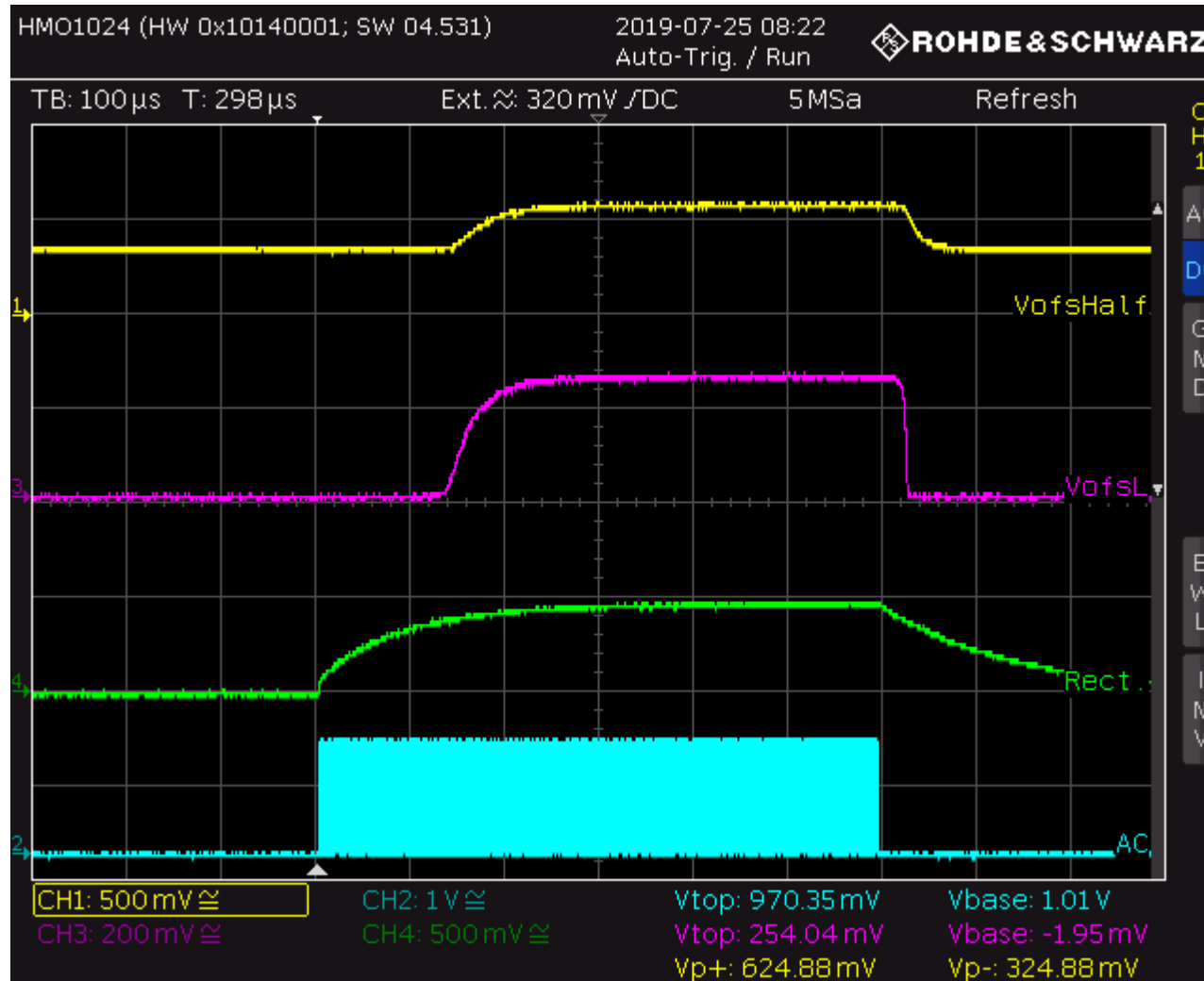Measurement AC Rectifier interaction with Vofs



Summary and Conclusion

- SLDO core design is almost the same
 - layout optimization and wiring modifications
- startup-behavior should become more deterministic
 - less bandgaps involved
 - startup-circuited integrated
- higher robustness and reliability aimed by protection features
 - overvoltage protection
 - overload/undershunt current protection
- Low Power mode initialization by Vofs configurability
 - AC rectification circuit integrated